

BJT
(Bipolar Junction Transistor)


Elektronika
(TKE 4012)

Eka Maulana


Pokok Bahasan


- Dasar Transistor
- Arus transistor
- Koneksi rangkaian
- Kurva transistor
- Pendekatan transistor
- Datasheet
- Load Line
- Titik Kerja

BJT terdiri dari 3 bagian (dopping)

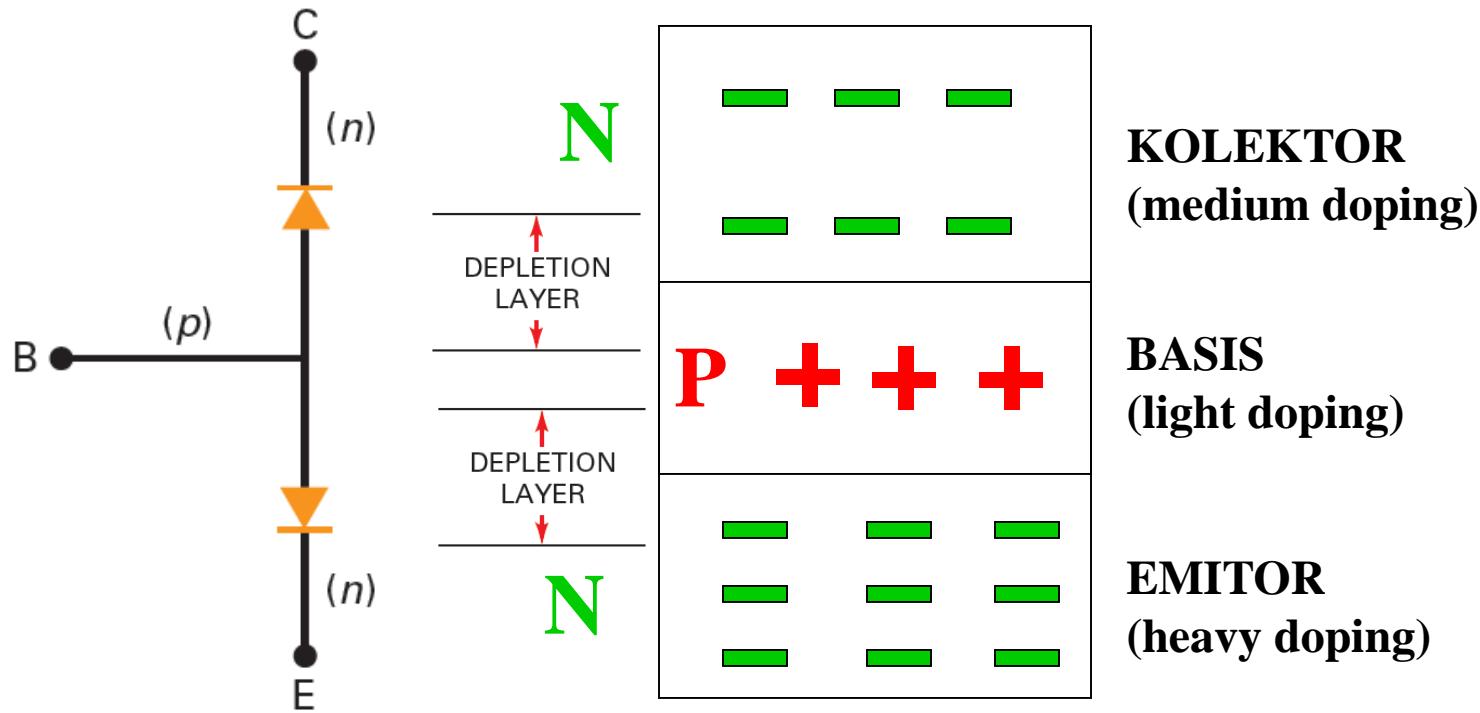

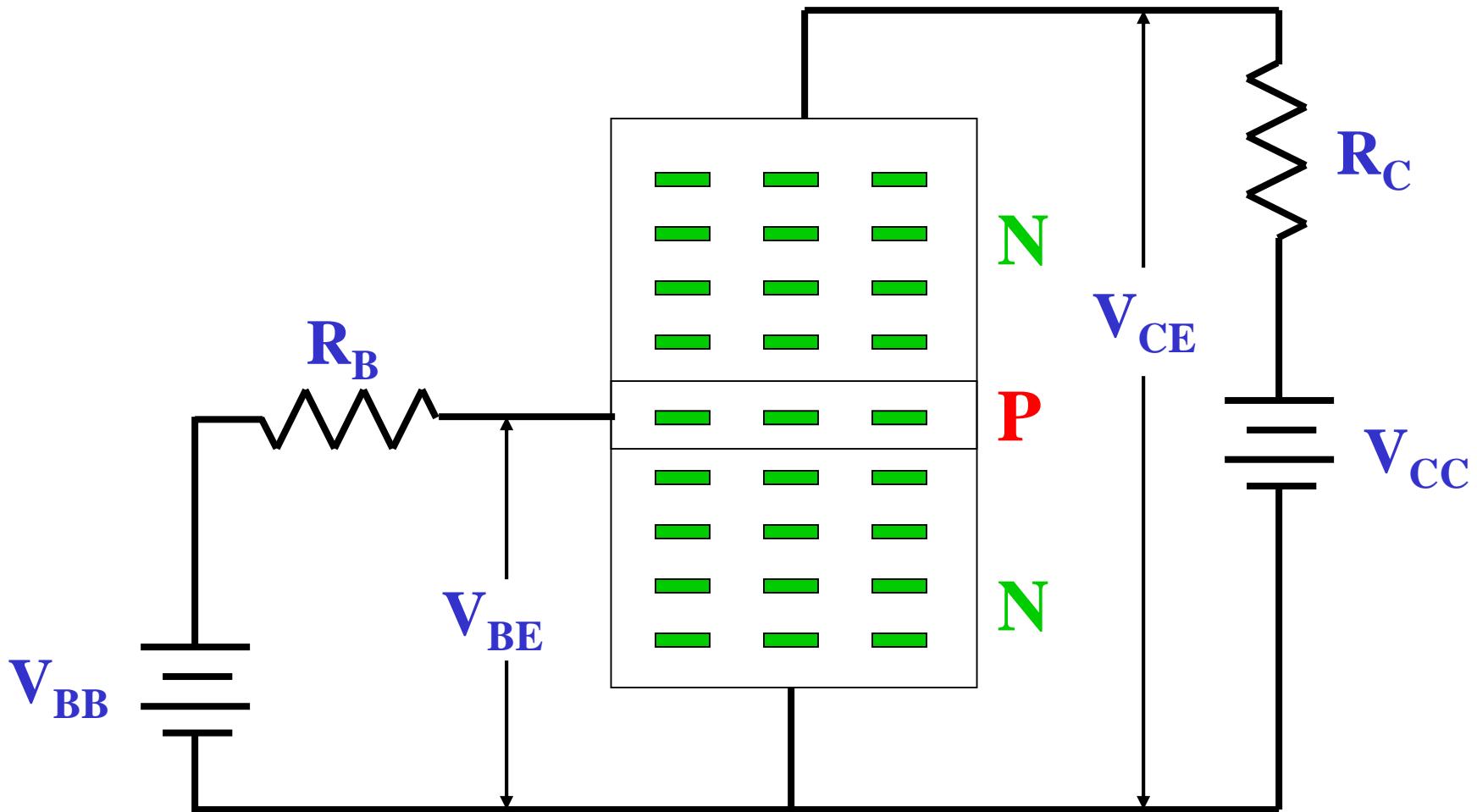
Saat transistor NPN dibias maju,
electron emiter menyebar ke basis dan kolektor



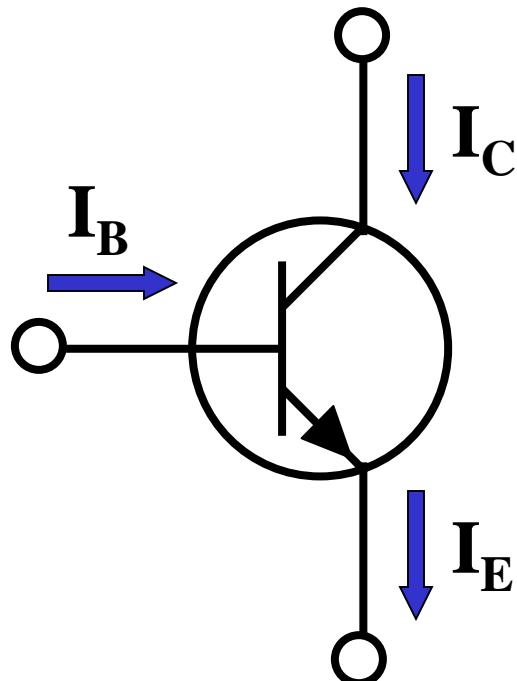

Aliran Arus

$$I_E = I_C + I_B$$

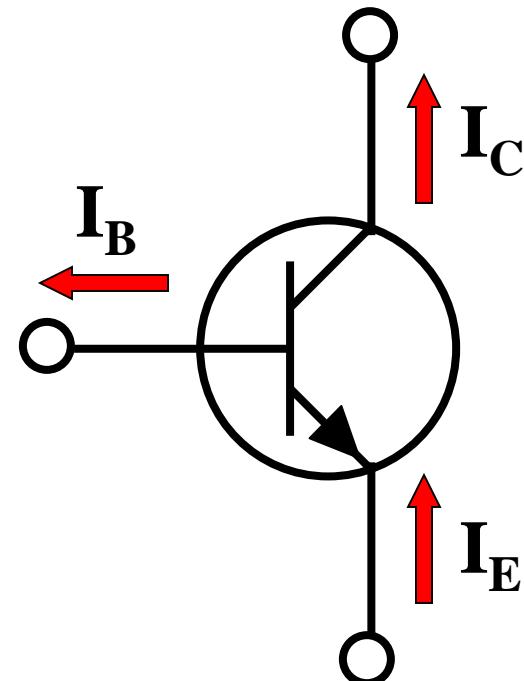

Aliran Elektron

$$I_C \approx I_E$$


$$I_B \ll I_C$$

$$\alpha_{dc} = \frac{I_C}{I_E}$$

$$\beta_{dc} = \frac{I_C}{I_B}$$

Common Emitter memiliki dua loop:

Loop Basis dan Loop Kolektor

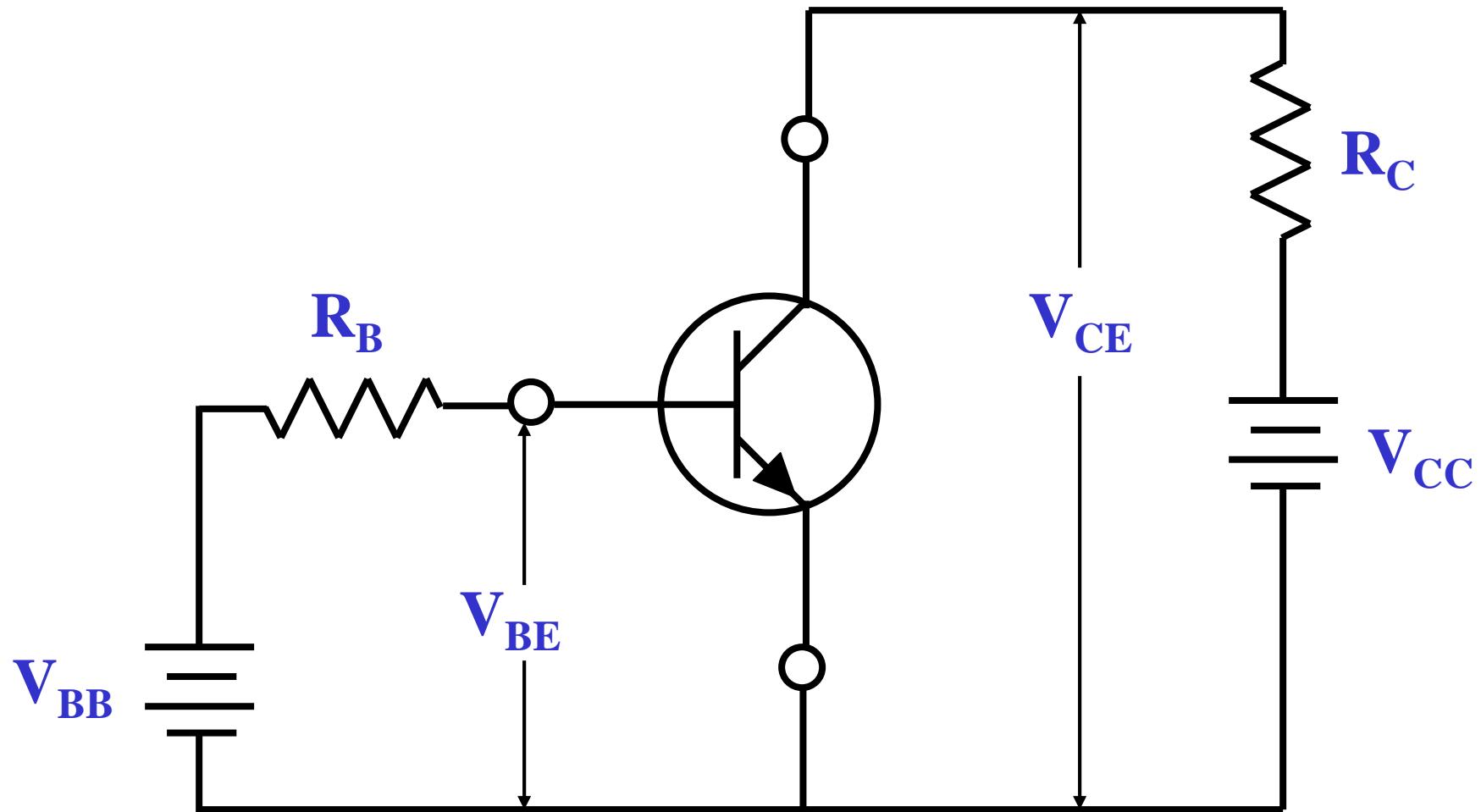


Notasi Subscript


- Ketika notasi subscript sama, maka menyatakan sumber tegangan (V_{CC}).
- Ketika notasi subscript sama, menyatakan tegangan dua titik (V_{CE}).
- Notasi single digunakan untuk menyatakan tegangan node dengan ground sebagai referensi (V_C).

Rangkaian pada BASIS biasanya dianalisis dengan pendekatan yang sama seperti digunakan pada dioda.

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

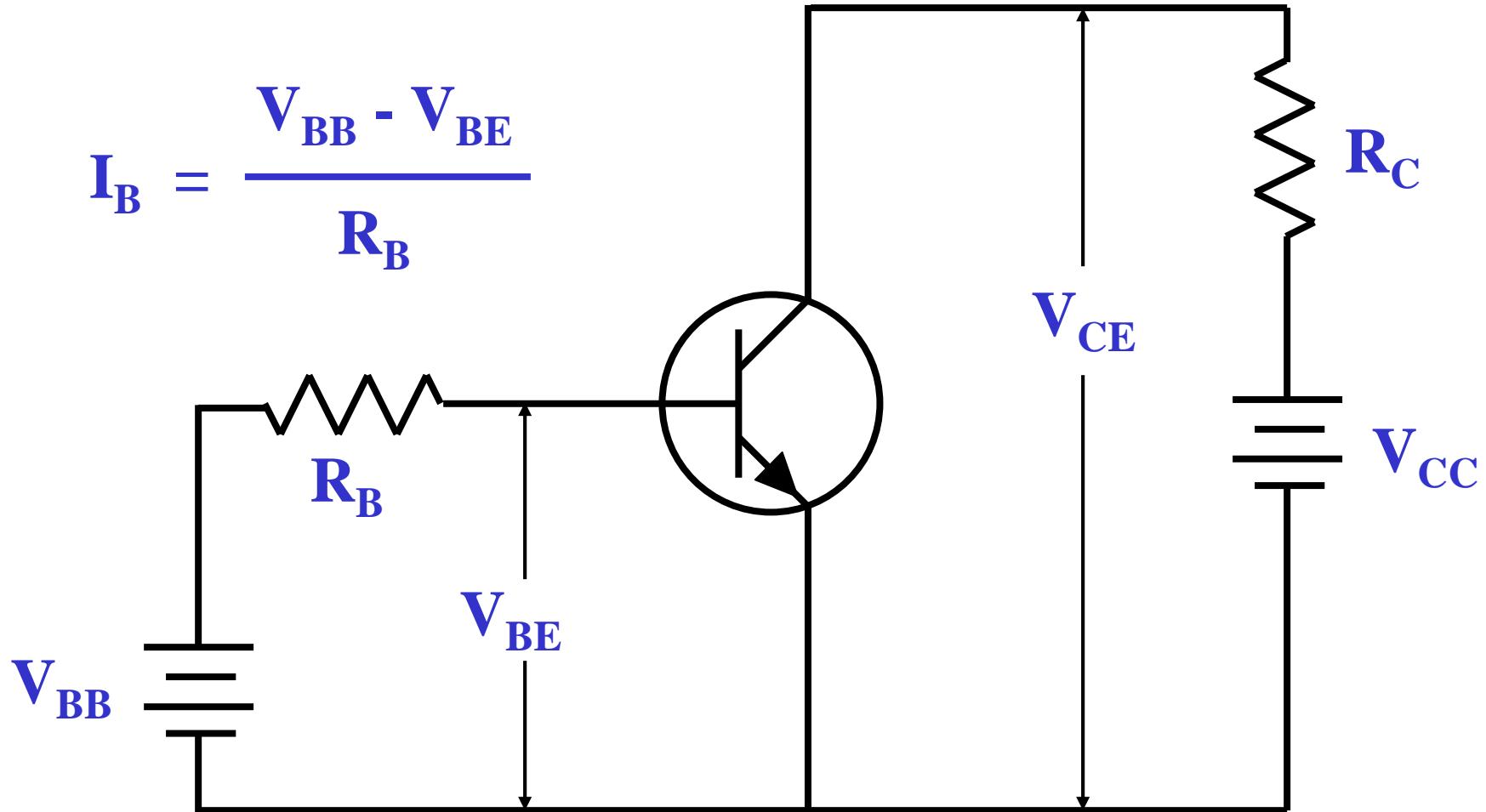

Grafik I_C versus V_{CE}

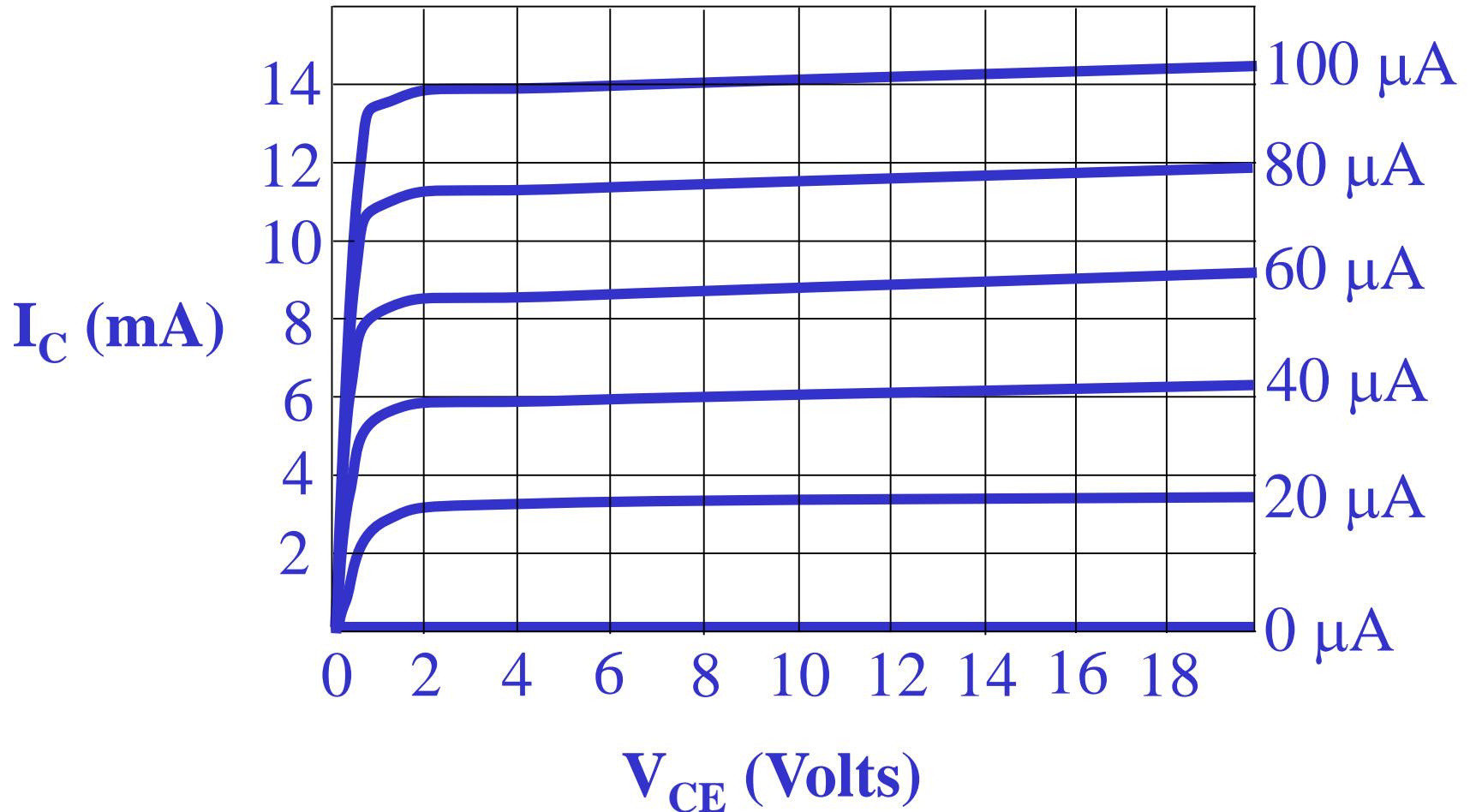

(nilai I_B baru merepresentasikan kurva baru)


Daerah Kerja Transistor

- **Cutoff** - digunakan untuk aplikasi switching
- **Active** - digunakan untuk penguatan linear
- **Saturation** - digunakan untuk aplikasi switching
- **Breakdown** - dapat merusak transistor

Pendekatan Rangkaian Transistor


- **First:** dioda ideal pada basis-emitor dan menggunakan βI_B untuk menentukan I_C .
- **Second:** menggunakan V_{BE} dan βI_B untuk menentukan I_C .
- **Third (and higher):** menggunakan perhitungan resistansi bulk dan pengaruh lain. Biasanya diselesaikan dengan simulasi komputer.

Pendekatan Kedua:

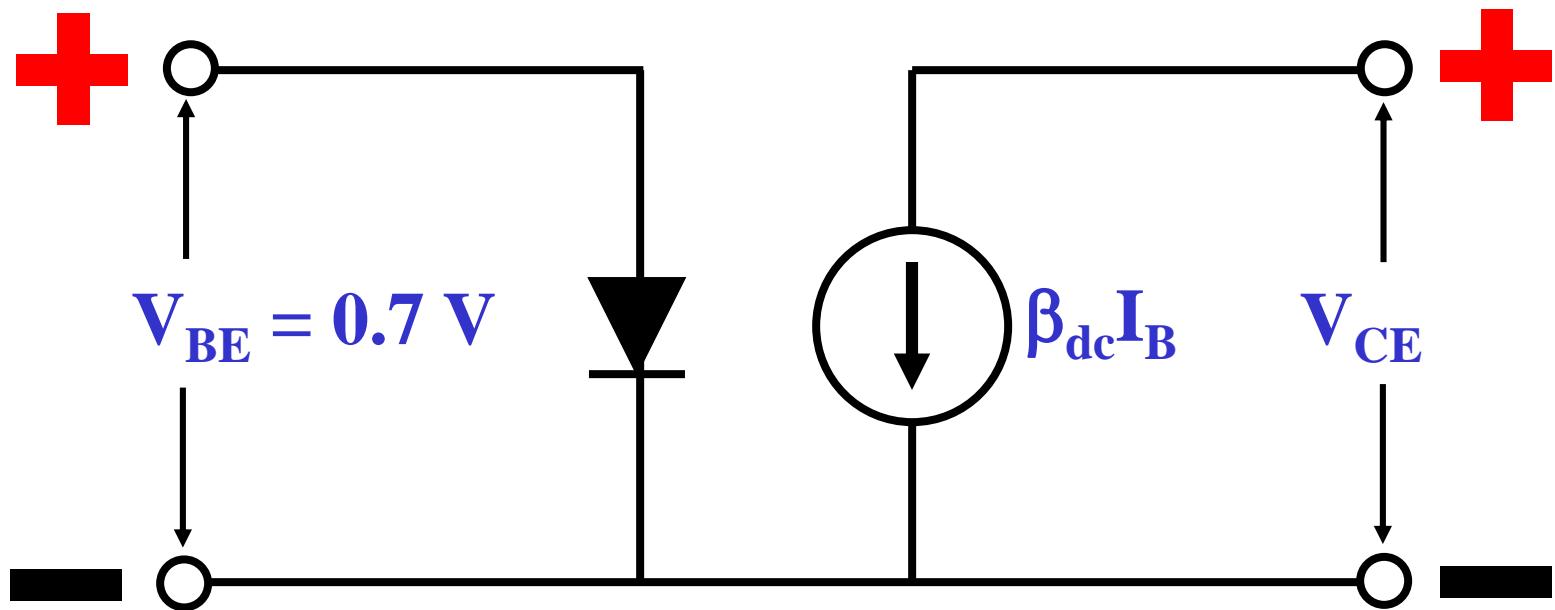


$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$
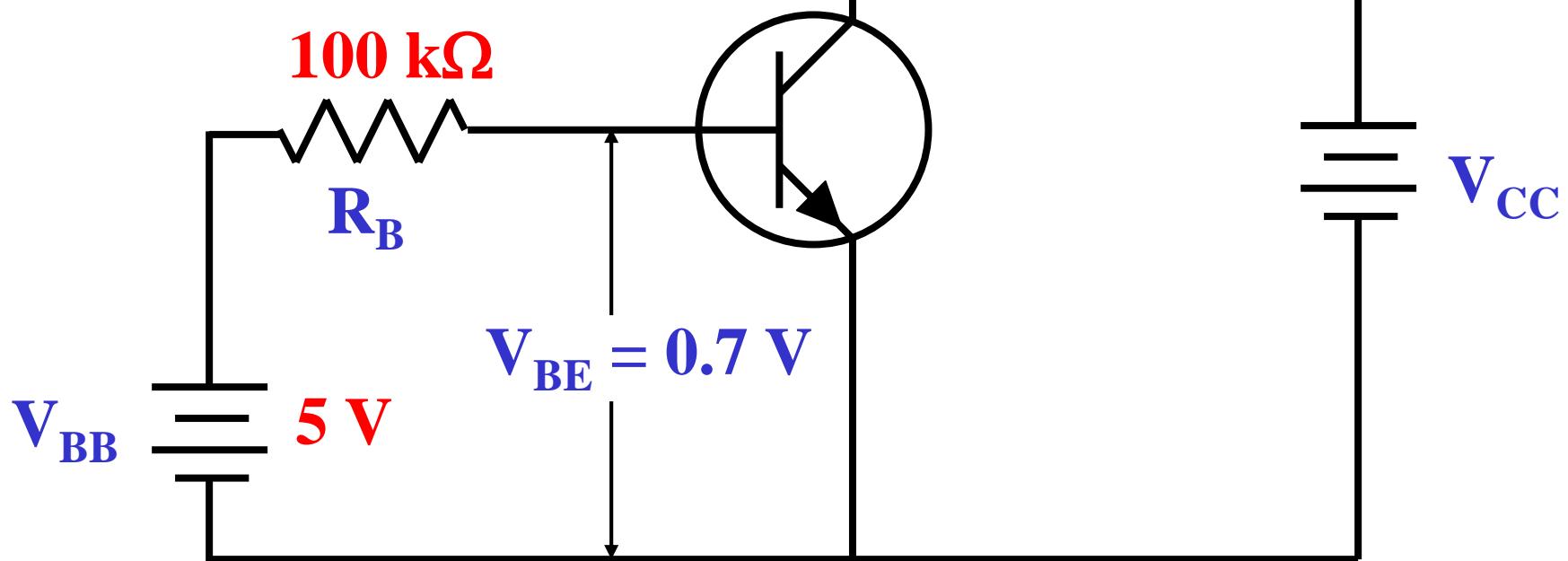
$$I_B = \frac{5 \text{ V} - 0.7 \text{ V}}{100 \text{ k}\Omega} = 43 \mu\text{A}$$




$$I_C = \beta_{dc} I_B$$
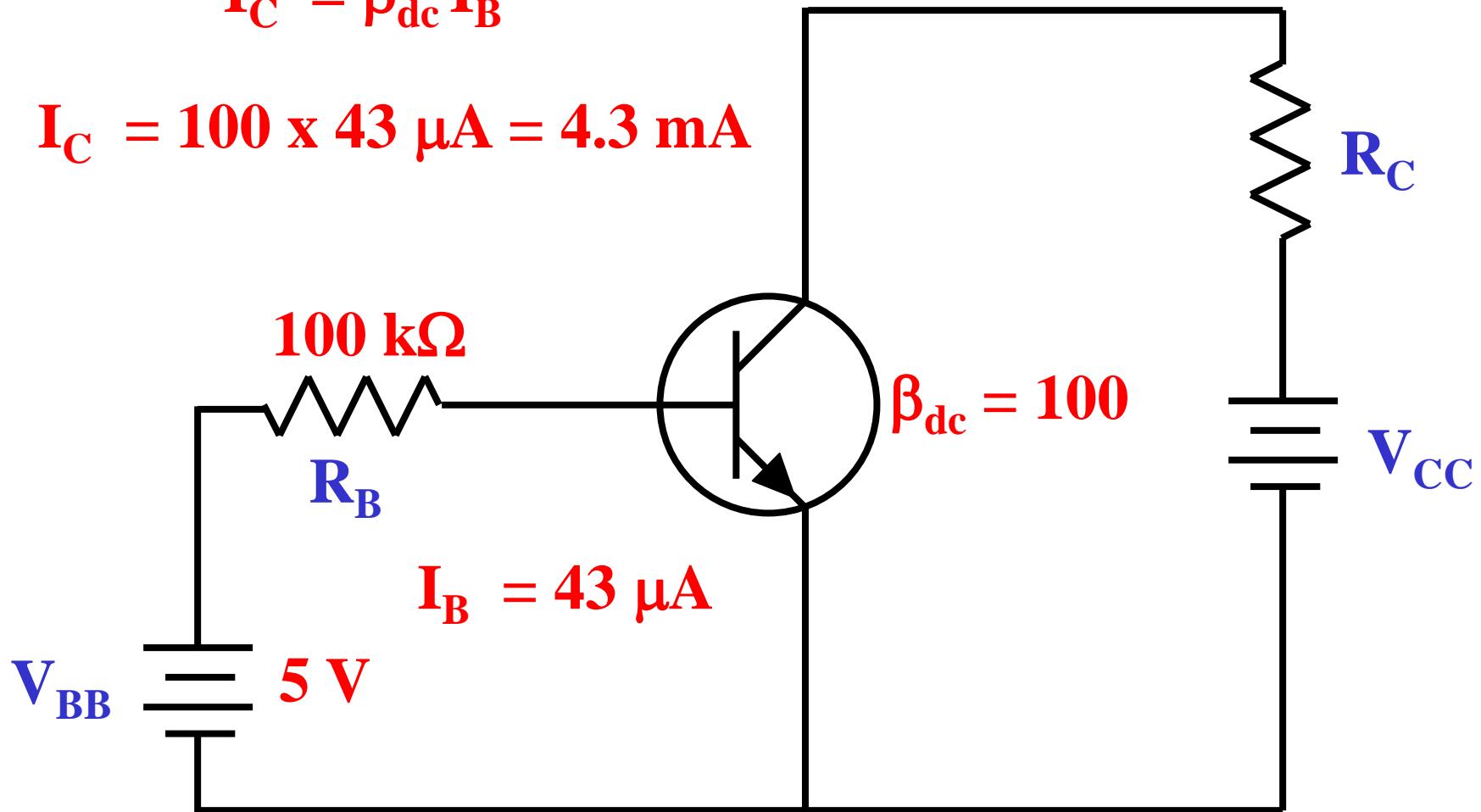
$$I_C = 100 \times 43 \mu A = 4.3 \text{ mA}$$



$$V_{R_C} = I_C \times R_C$$

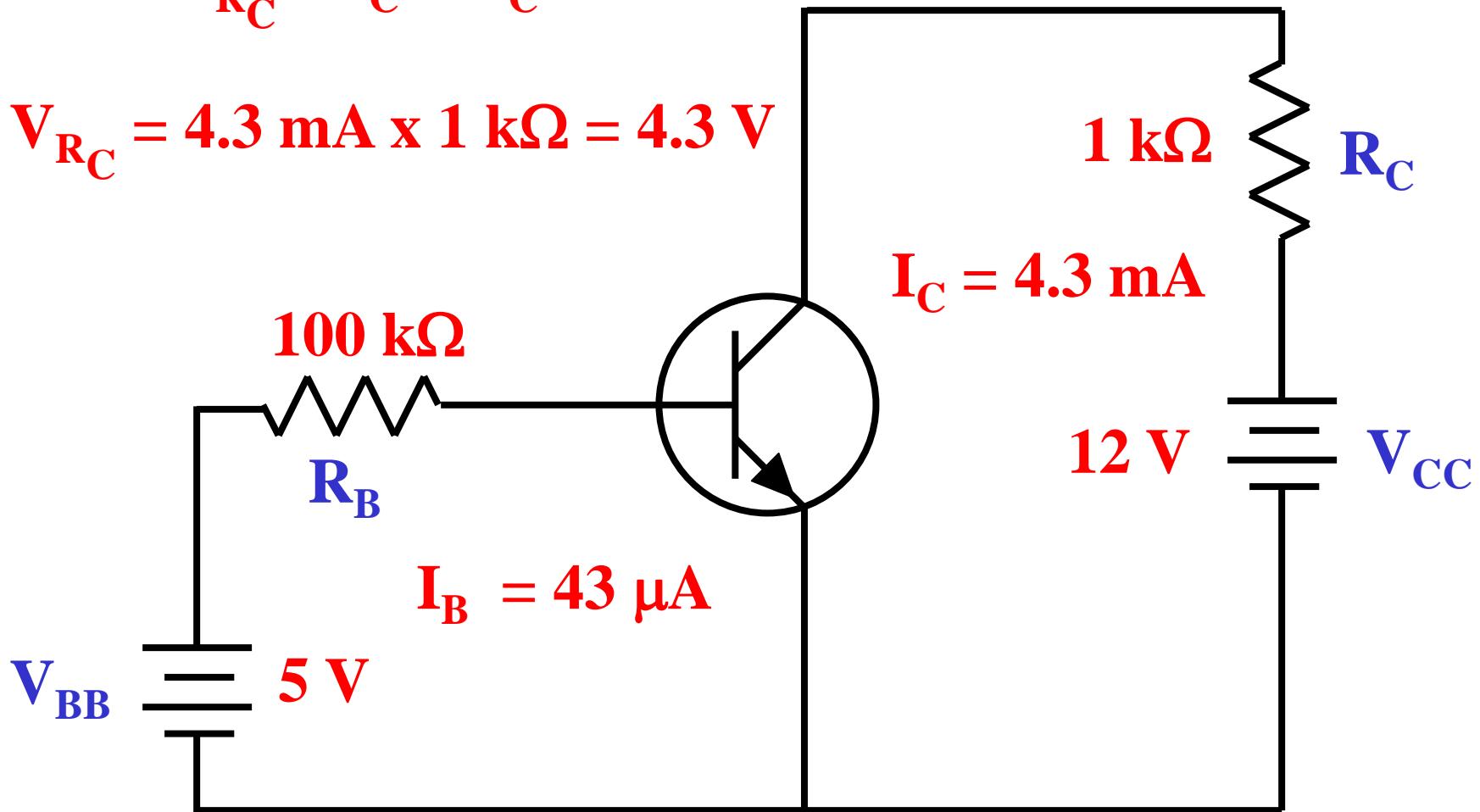
$$V_{R_C} = 4.3 \text{ mA} \times 1 \text{ k}\Omega = 4.3 \text{ V}$$



$$V_{CE} = V_{CC} - V_{R_C}$$

$$I_C = 4.3 \text{ mA}$$

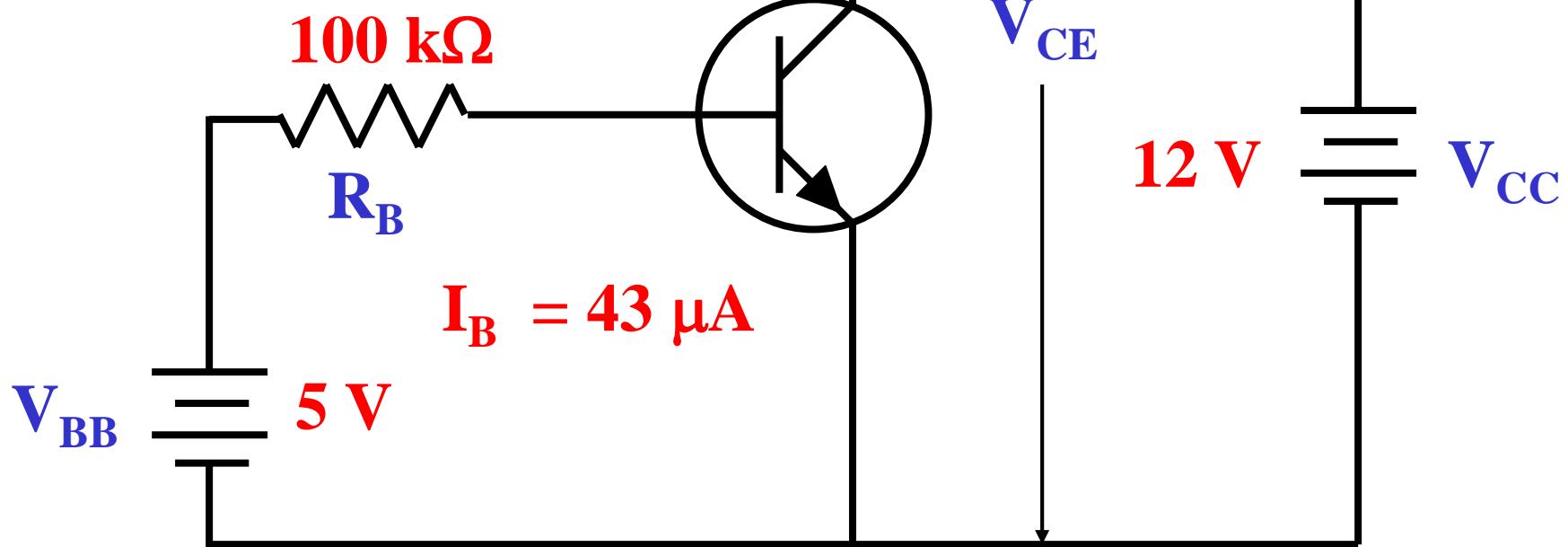
$$V_{CE} = 12 \text{ V} - 4.3 \text{ V} = 7.7 \text{ V}$$



Typical Breakdown Ratings

- $V_{CBO} = 60\text{ V}$
- $V_{CEO} = 40\text{ V}$
- $V_{EBO} = 6\text{ V}$
- Note: these are reverse breakdown ratings

Grafik breakdown Colector

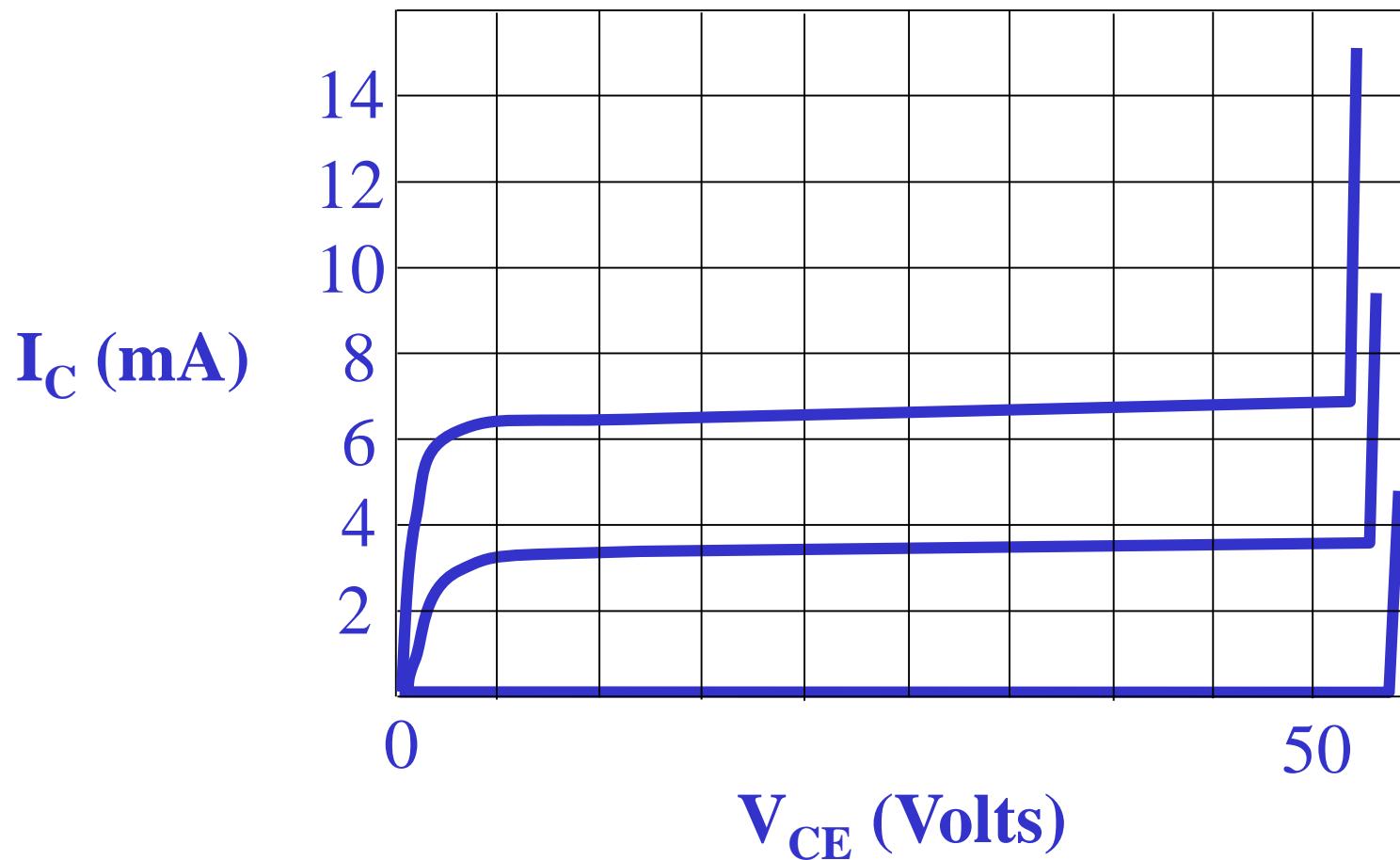

Typical Maximum Ratings


- $I_C = 200 \text{ mA dc}$
- $P_D = 250 \text{ mW}$ (for $T_A = 60 \text{ }^\circ\text{C}$)
- $P_D = 350 \text{ mW}$ (for $T_A = 25 \text{ }^\circ\text{C}$)
- $P_D = 1 \text{ W}$ (for $T_C = 60 \text{ }^\circ\text{C}$)

Pembiasan BJT (Bipolar Junction Transistor)

Elektronika (TKE 4012)

Eka Maulana


$$V_{CE} = V_{CC} - I_C R_C$$

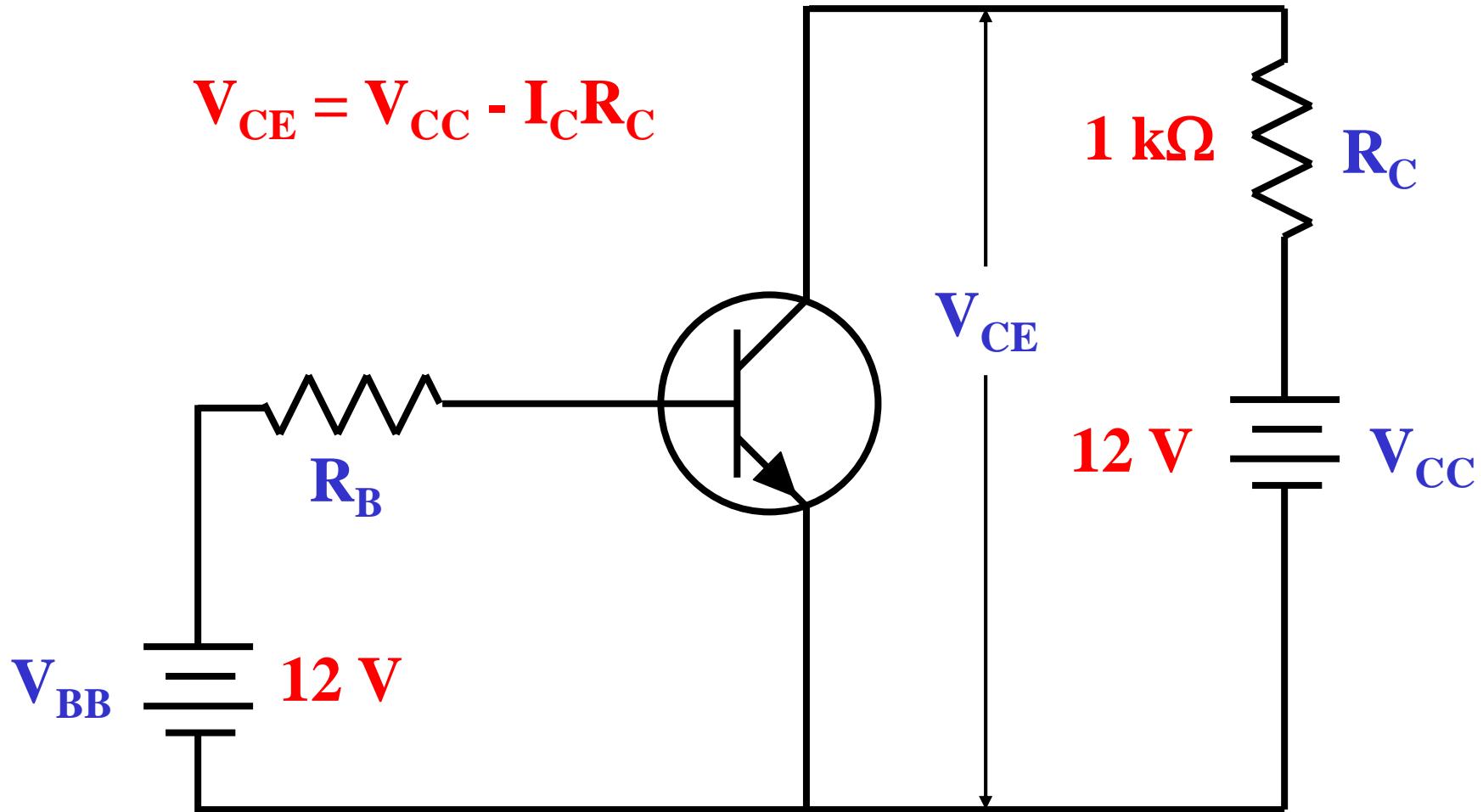


$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$




Persaman ini menghasilkan load line.

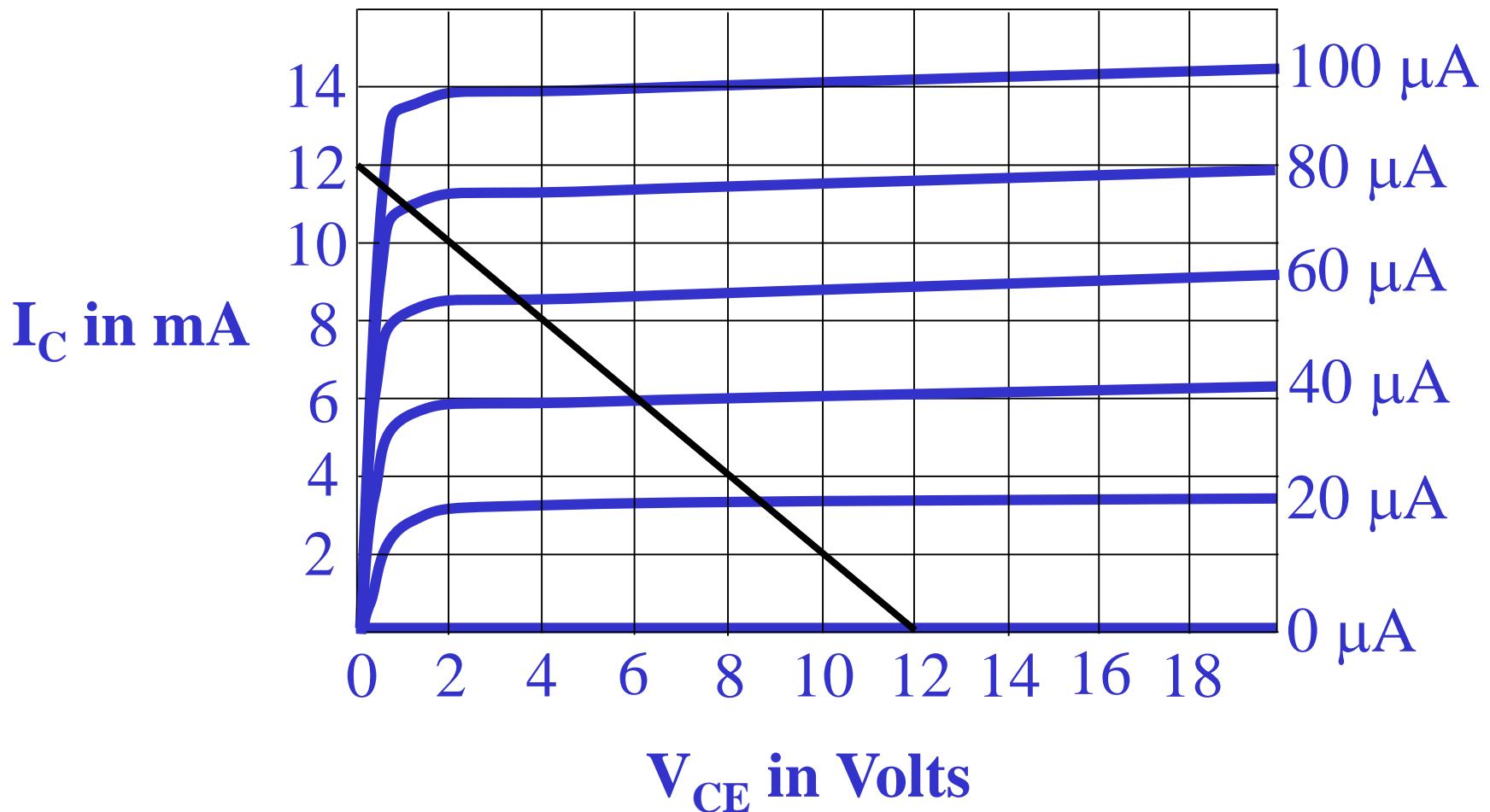

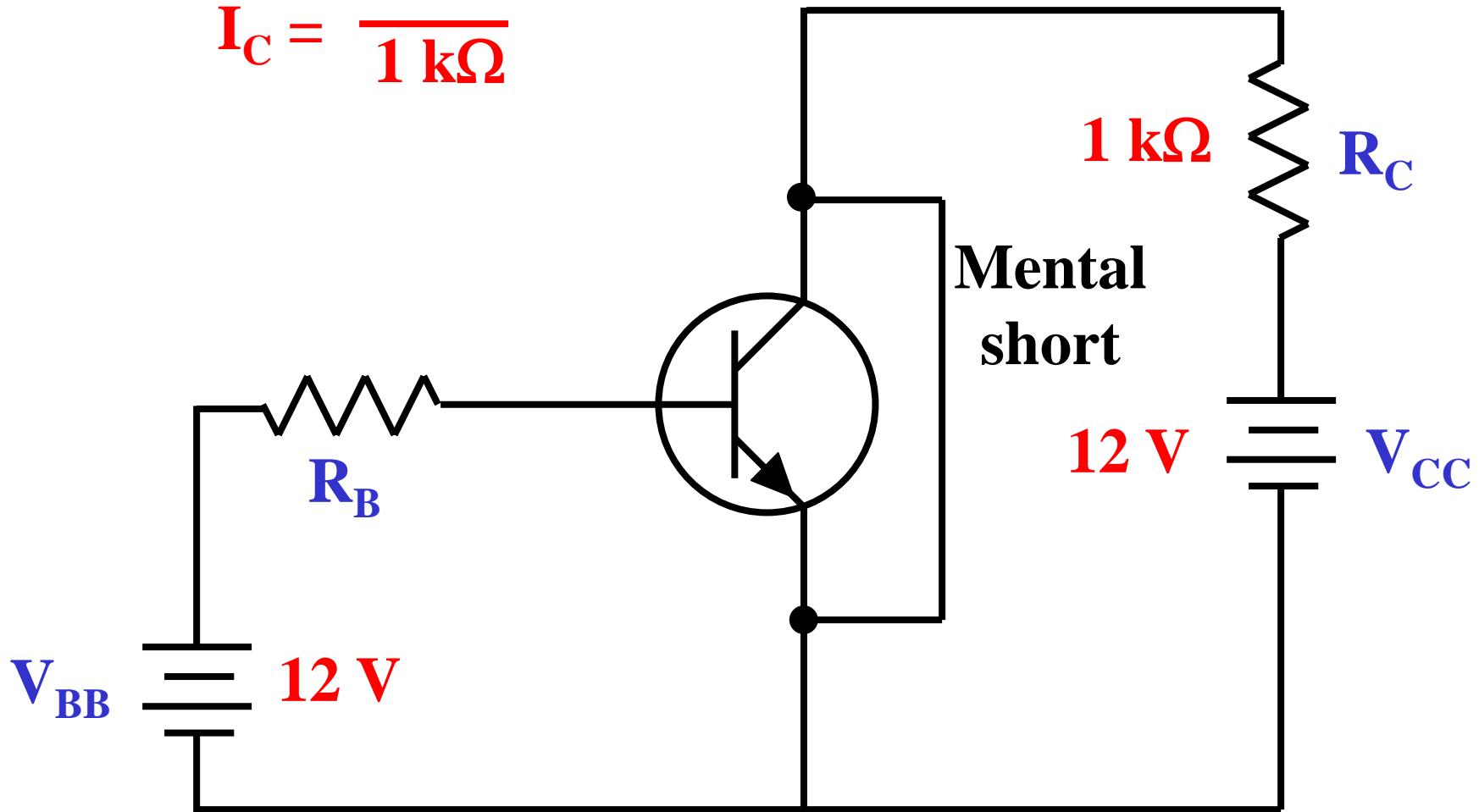
$$I_C = \frac{12 \text{ V}}{1 \text{ k}\Omega}$$



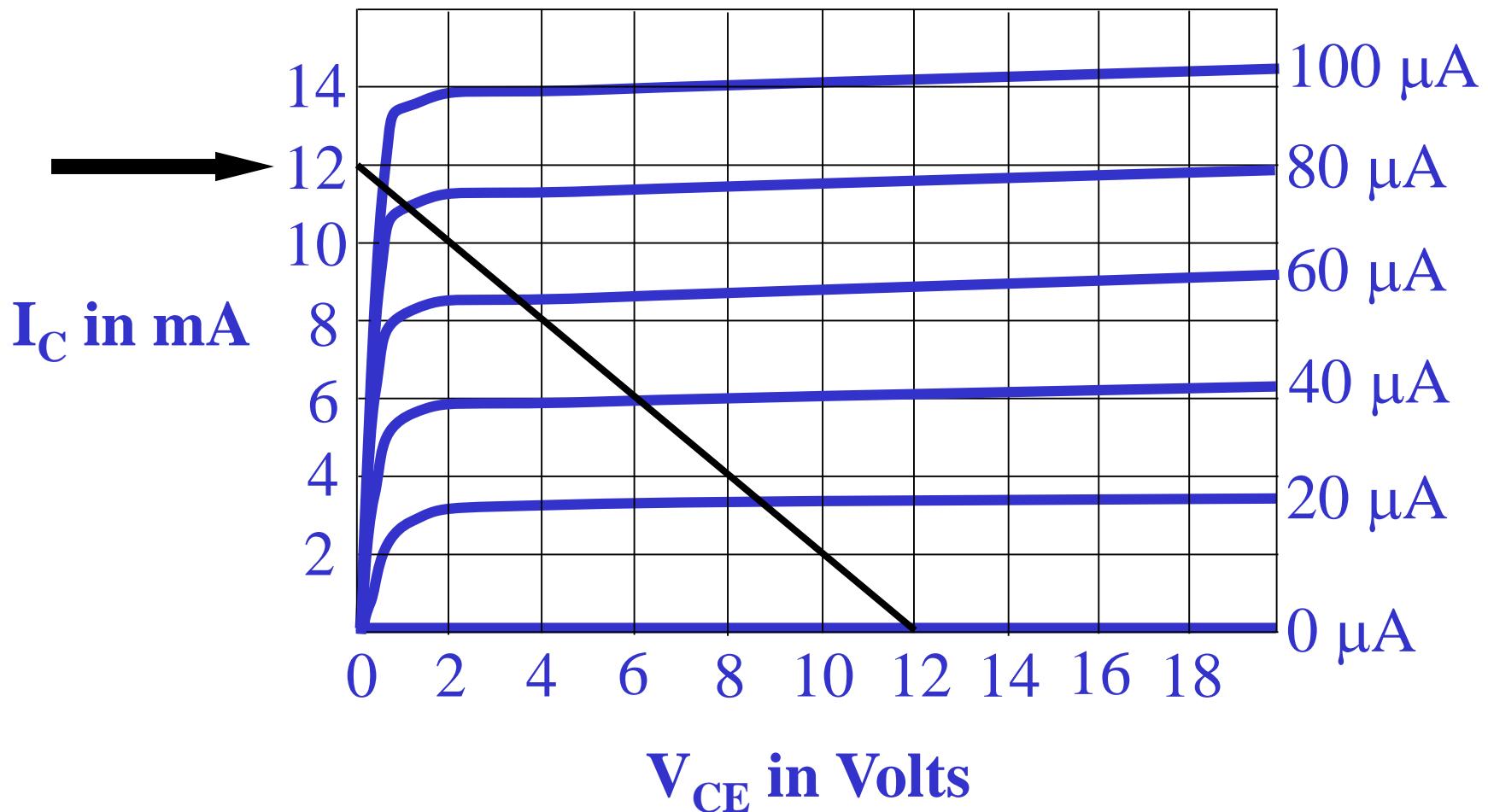
$$I_C = \frac{12 \text{ V}}{1 \text{ k}\Omega} = 12 \text{ mA} \quad \text{← Arus satutasi}$$




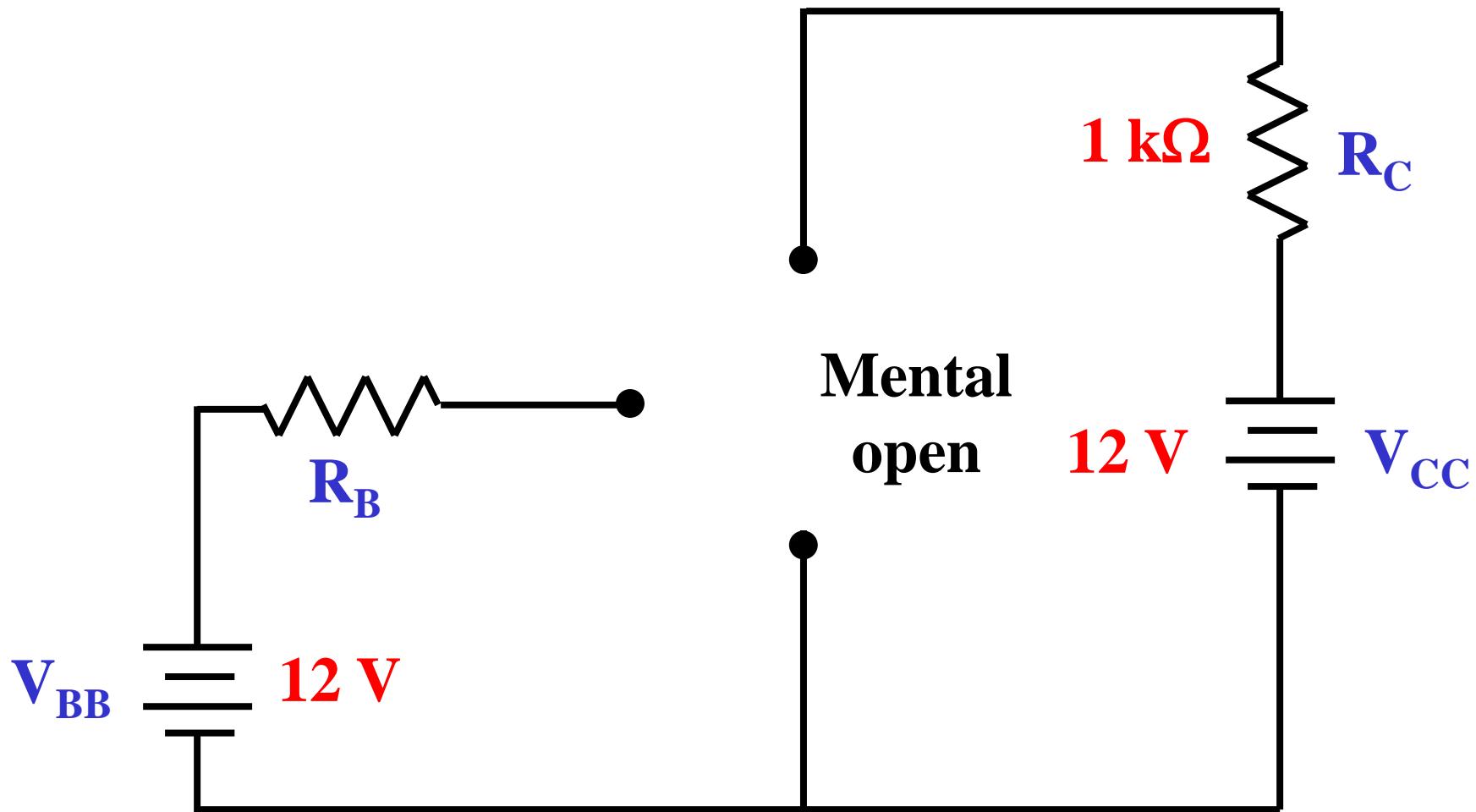


$$V_{CE(\text{cutoff})} = V_{CC}$$

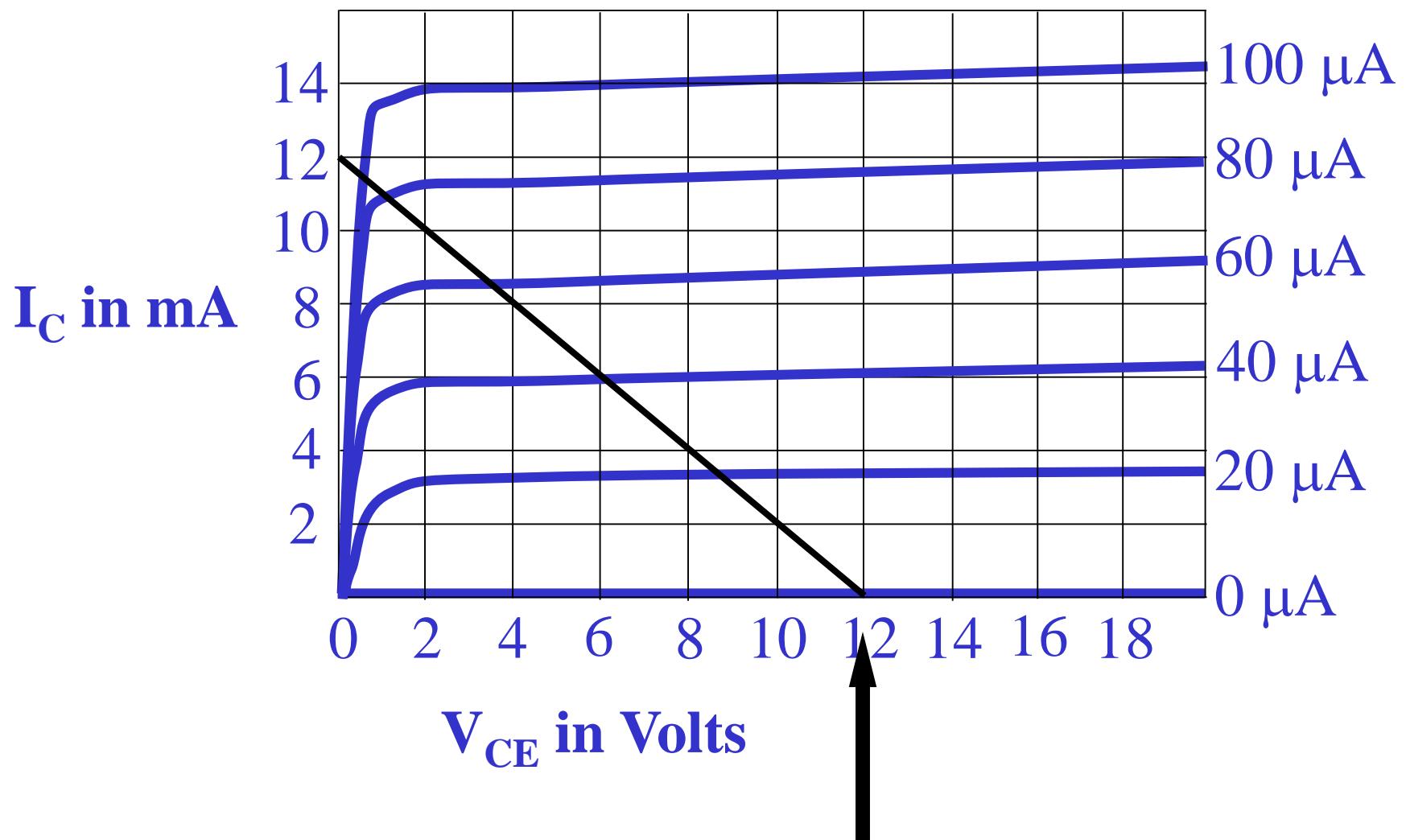

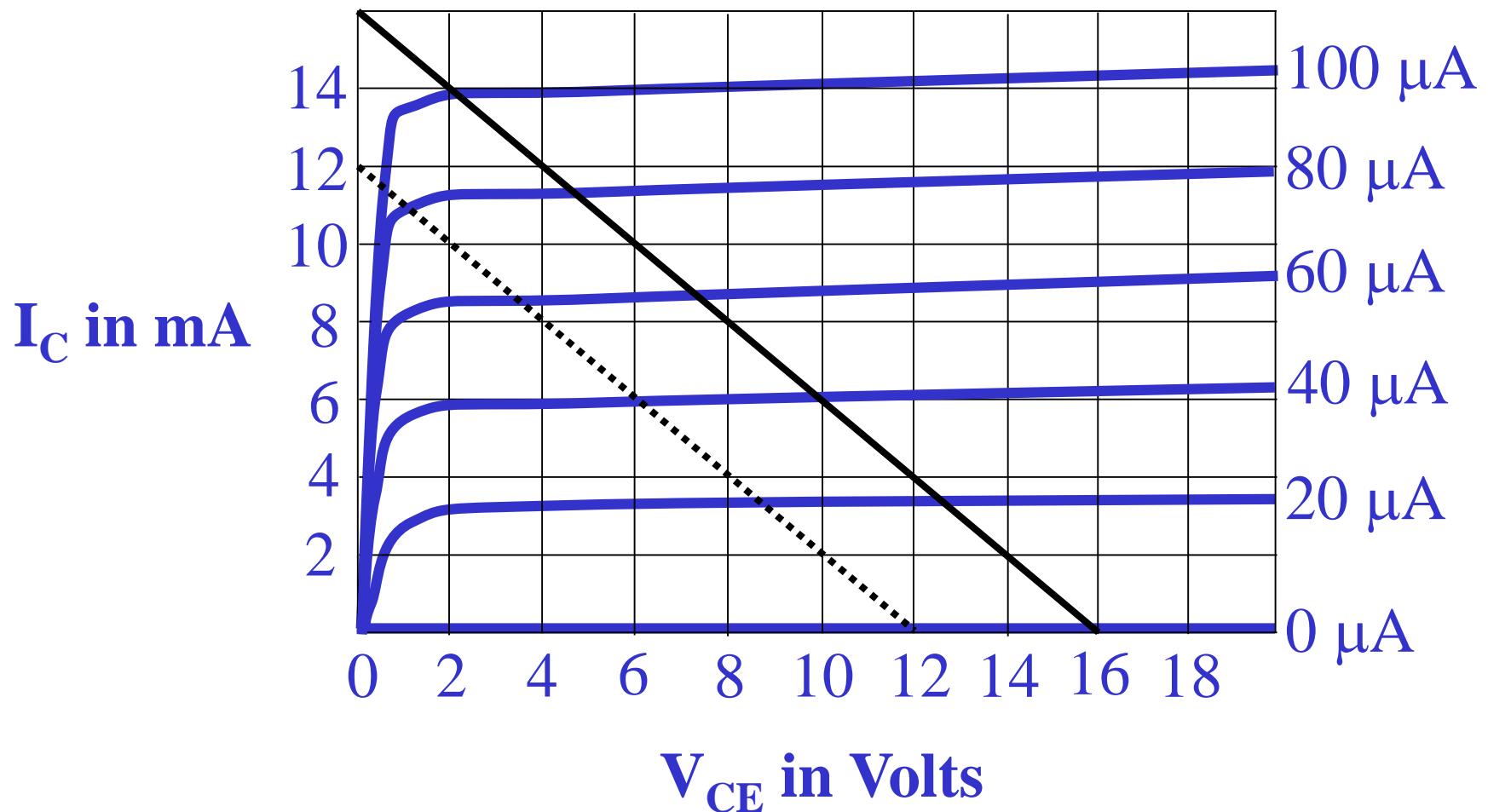
load line baru dengan kemiringan yang sama




Ubah R_C :

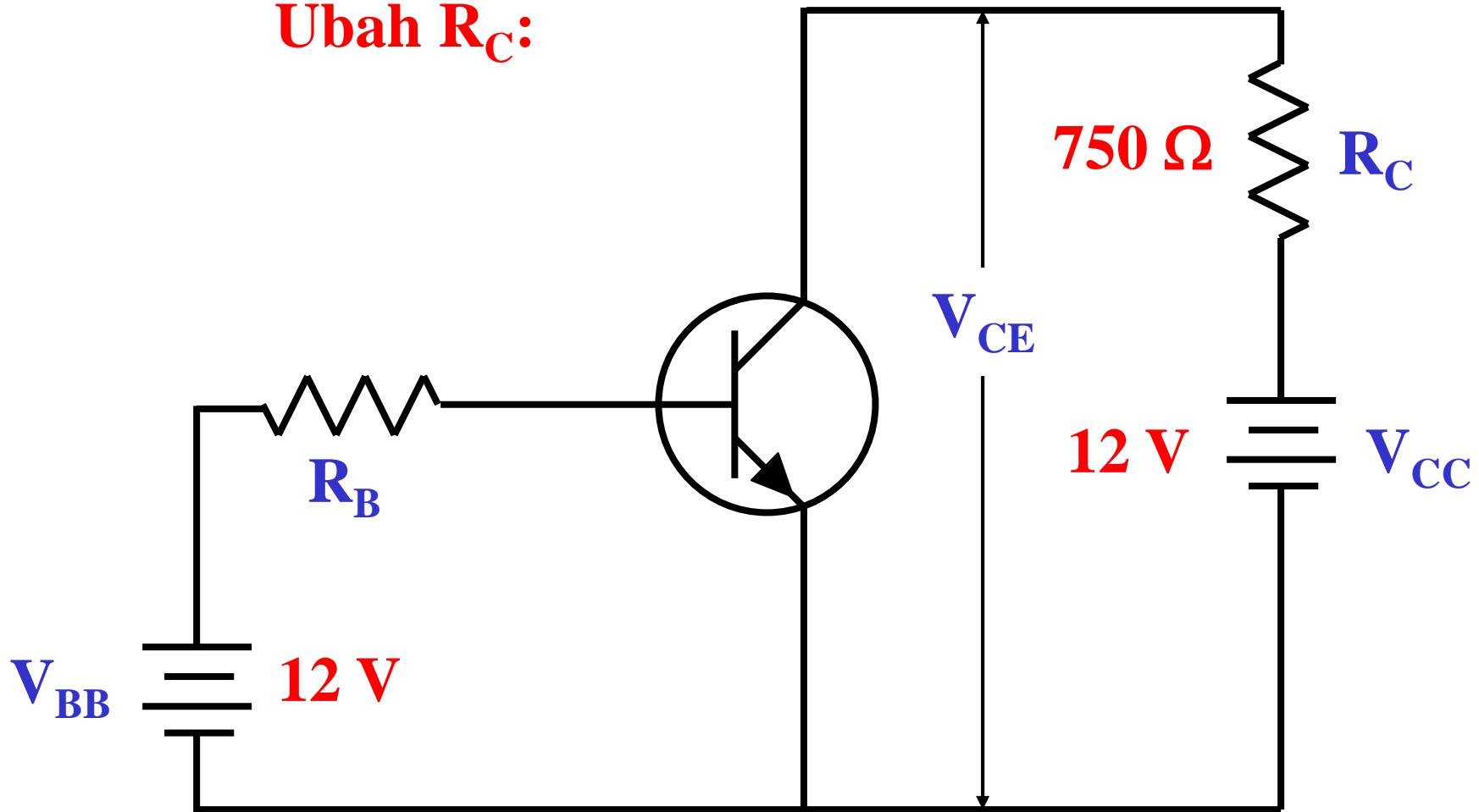

Smaller R_C menghasilkan steeper slope

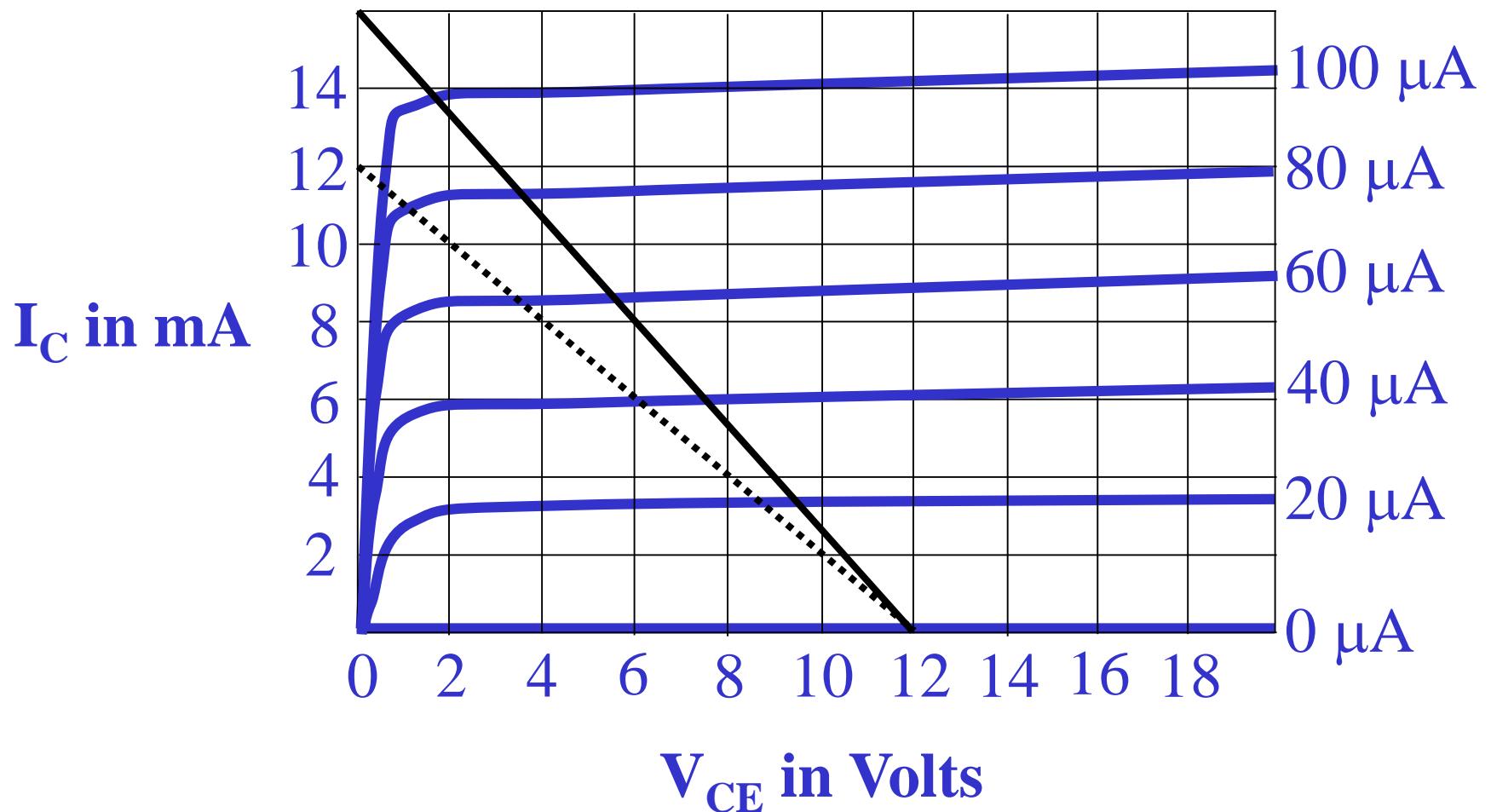

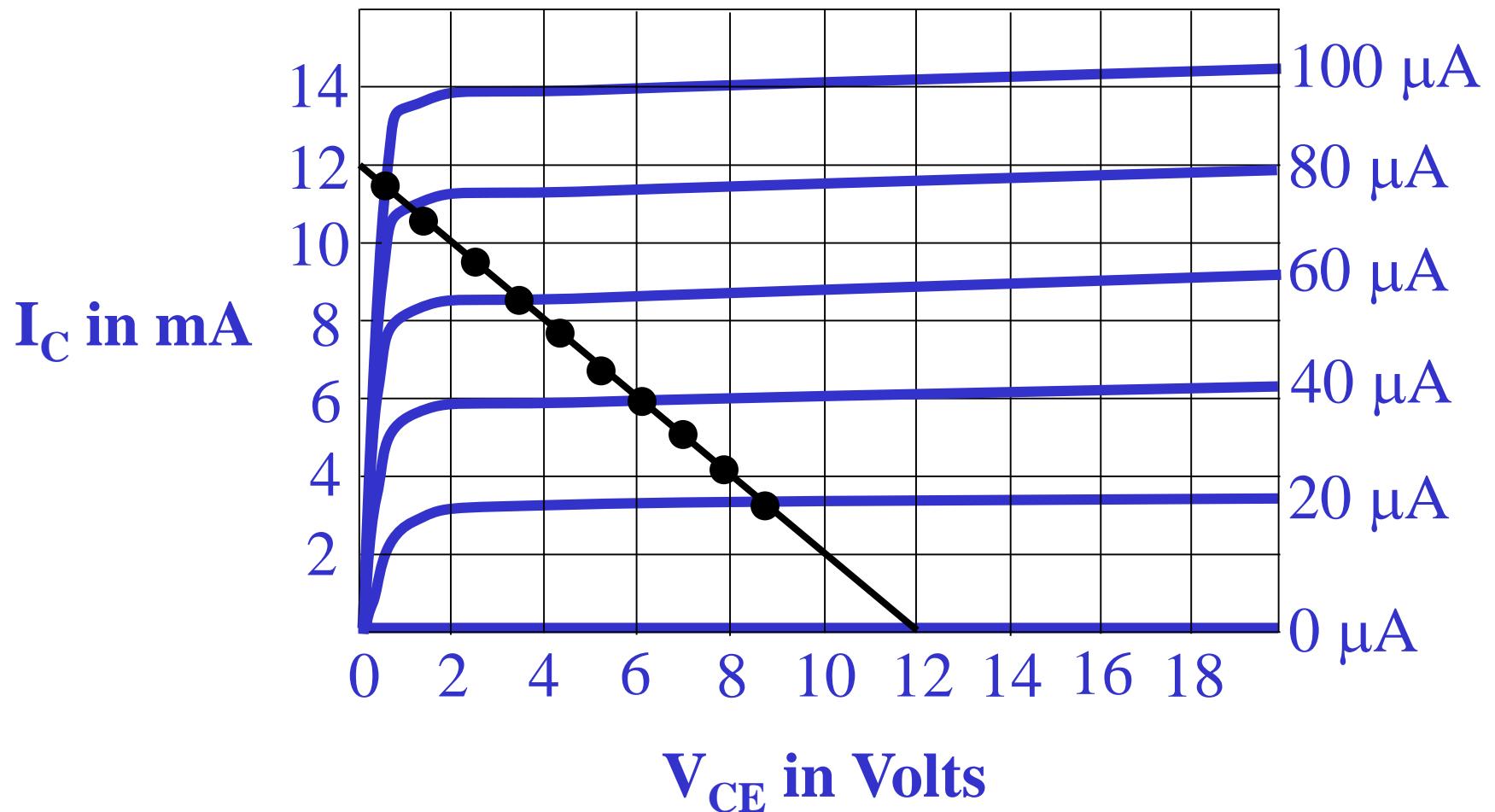
Rangkaian dapat dioperasikan pada setiap titik pada load line




The operating point is determined by the base current.

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$
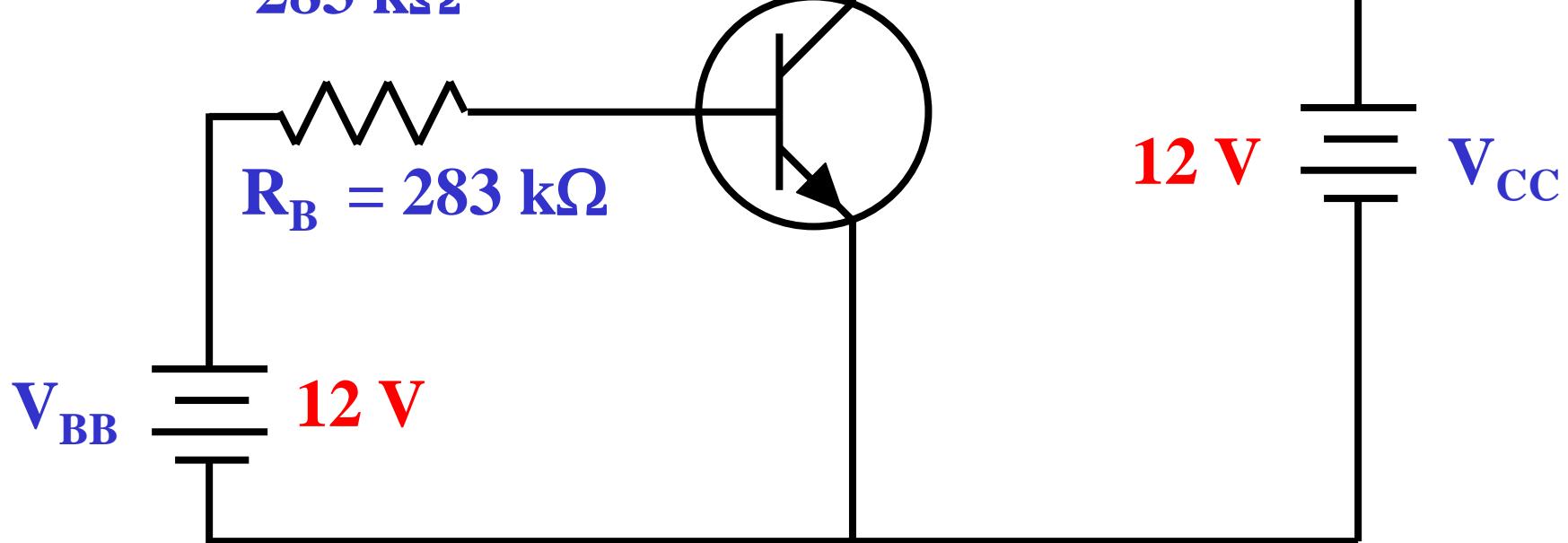
$$I_B = \frac{12 \text{ V} - 0.7 \text{ V}}{283 \text{ k}\Omega} = 40 \mu\text{A}$$




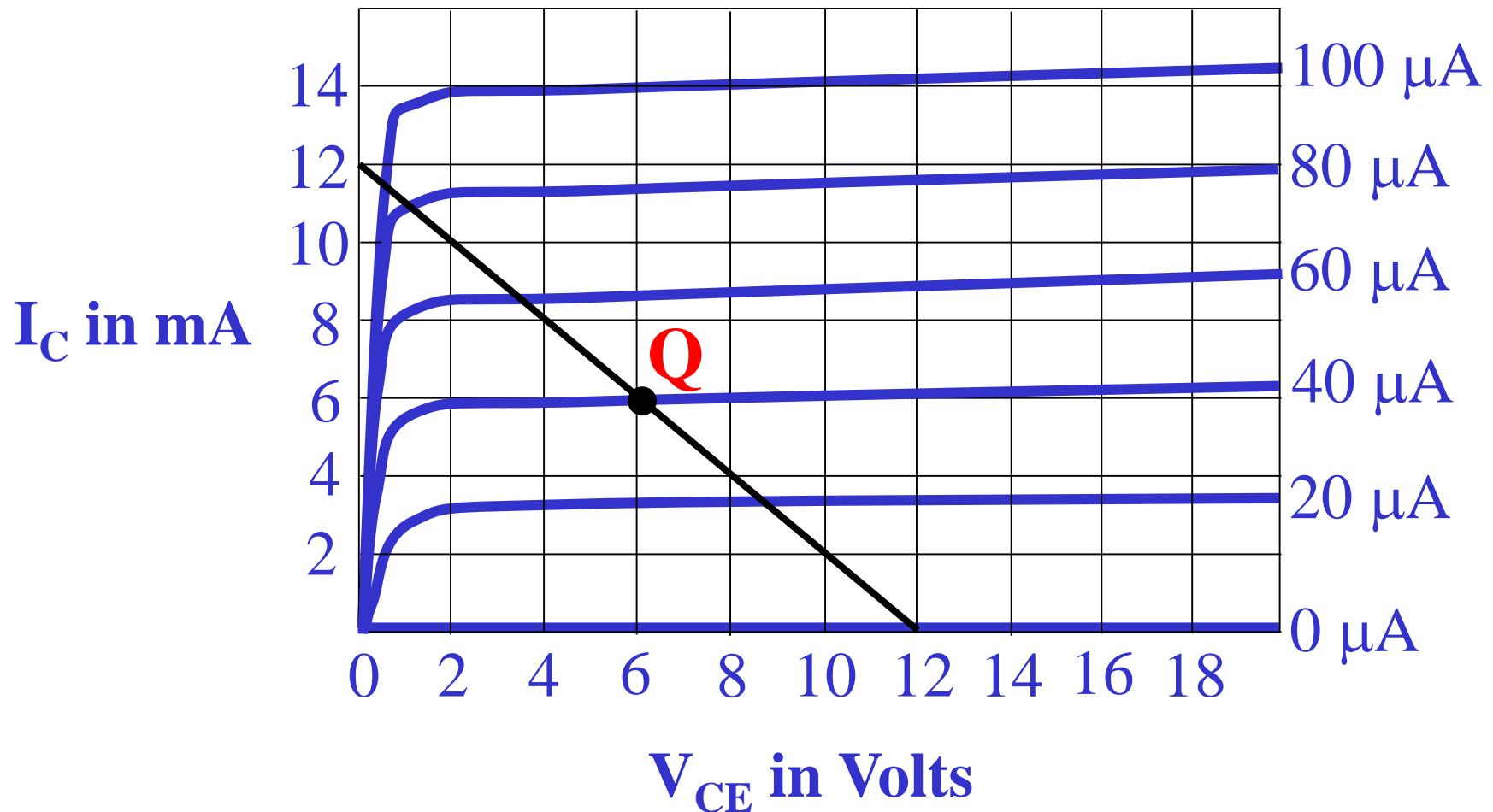The operating point is called the quiescent point.



This Q point is in the linear region.

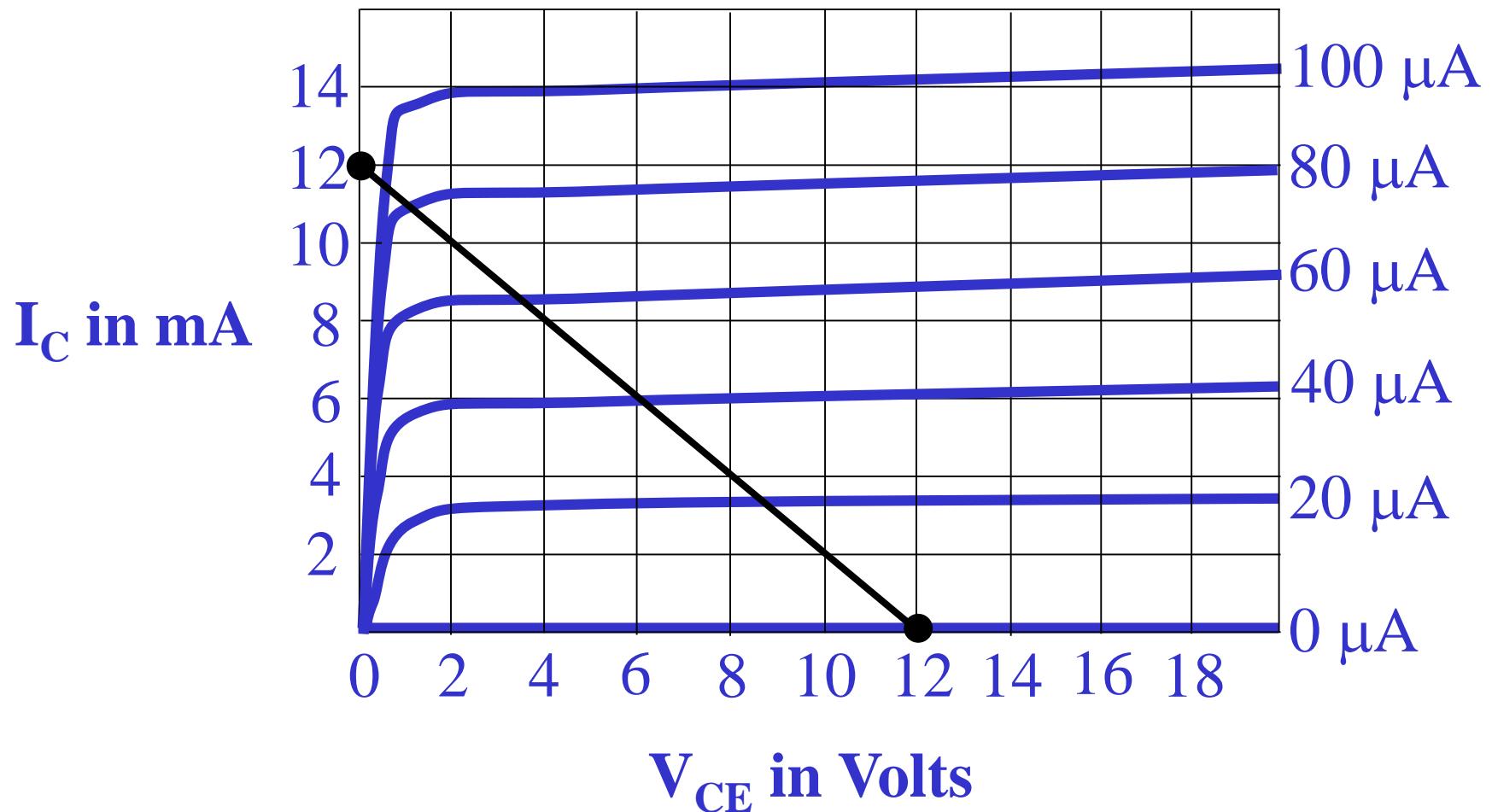Saturation and cutoff are non-linear operating points.



These Q points are used in switching applications.

Recognizing saturation


- Assume linear operation.
- Perform calculations for currents and voltages.
- An impossible result means the assumption is false.
- An impossible result indicates saturation.

Base bias

- The base current is established by V_{BB} and R_B .
- The collector current is β times larger in linear circuits.
- The transistor current gain will have a large effect on the operating point.
- Transistor current gain is unpredictable.

Emitter bias:
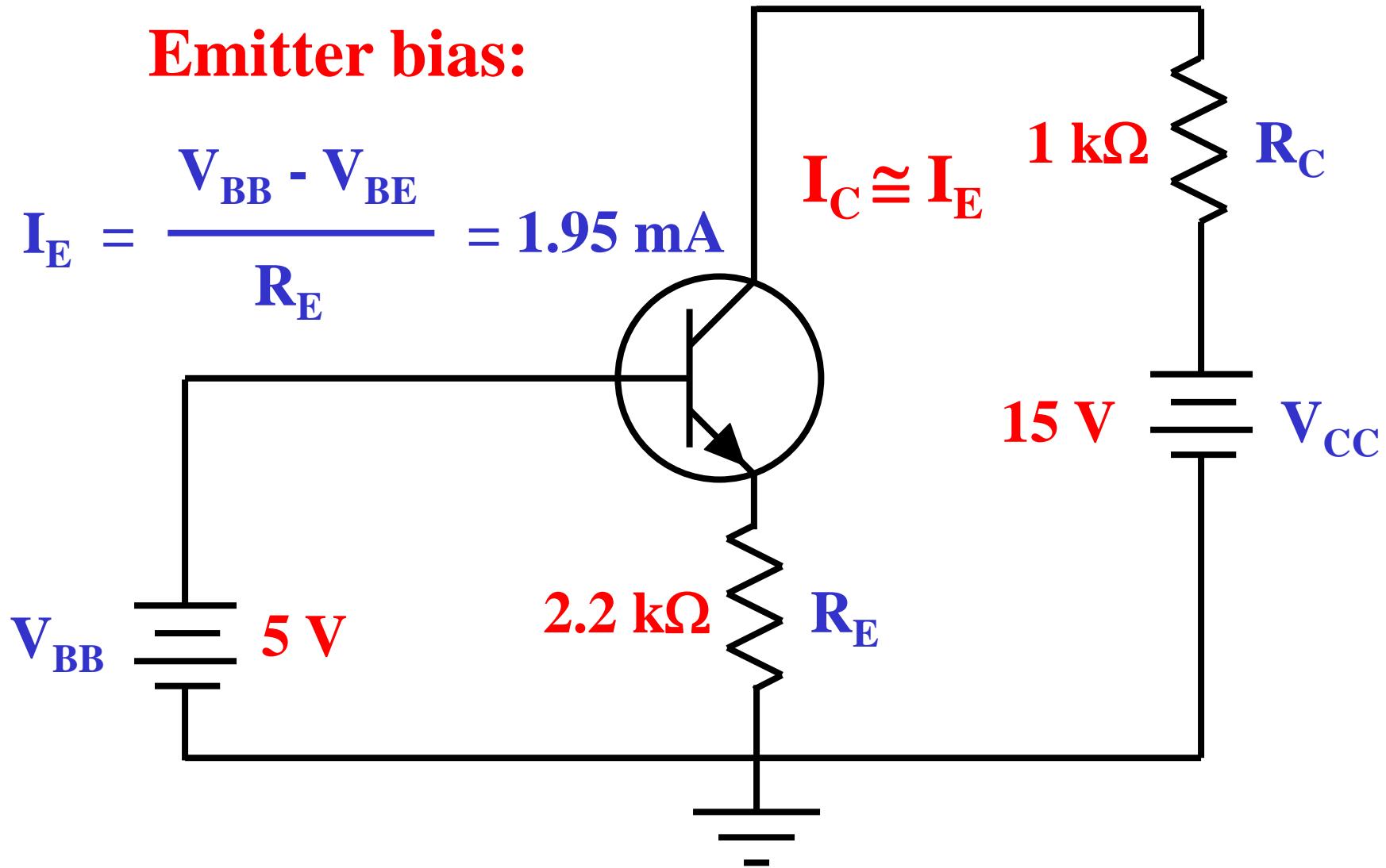
$$I_E = \frac{V_{BB} - V_{BE}}{R_E} = 1.95 \text{ mA}$$



$$V_C = 15 \text{ V} - (1.95 \text{ mA})(1 \text{ k}\Omega) = 13.1 \text{ V}$$

$$V_{CE} = 13.1 \text{ V} - 4.3 \text{ V} = 8.8 \text{ V}$$