

J-FET



(Junction Field Effect Transistor)

Elektronika

(TKE 4012)

Eka Maulana


Junction field effect transistor (JFET)

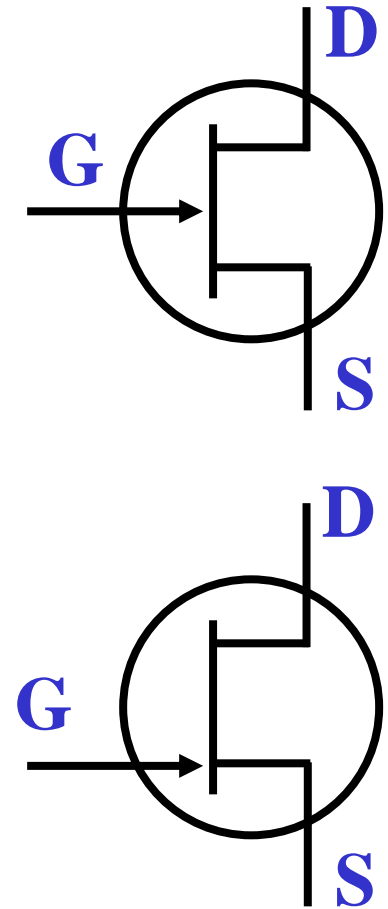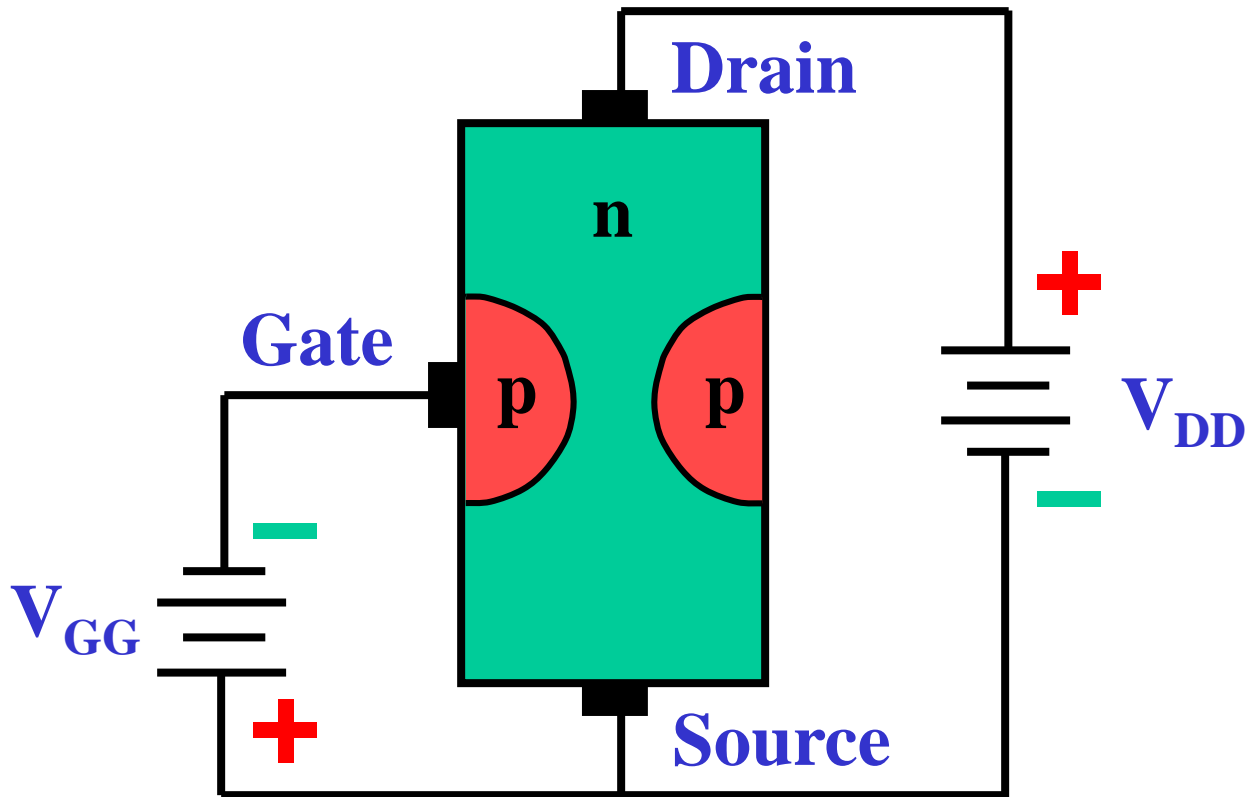

JFET


- **Unipolar device (one polarity of charge carrier)**
- **Voltage controlled (gate voltage controls drain current)**
- **High input impedance**
- **No minority carrier storage**
- **Source and drain are interchangeable in most low-frequency applications**

Drain family of curves

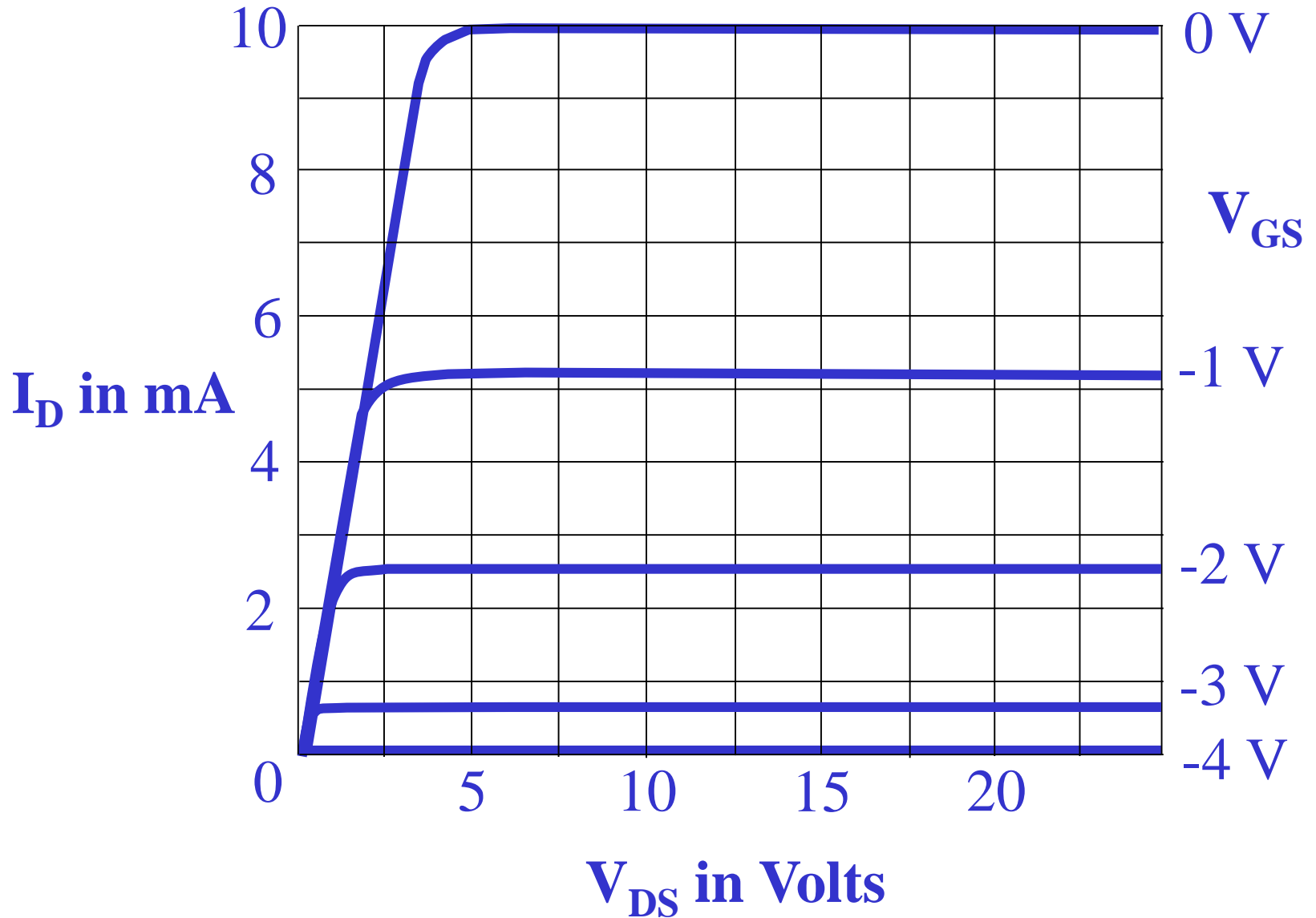


Drain curves

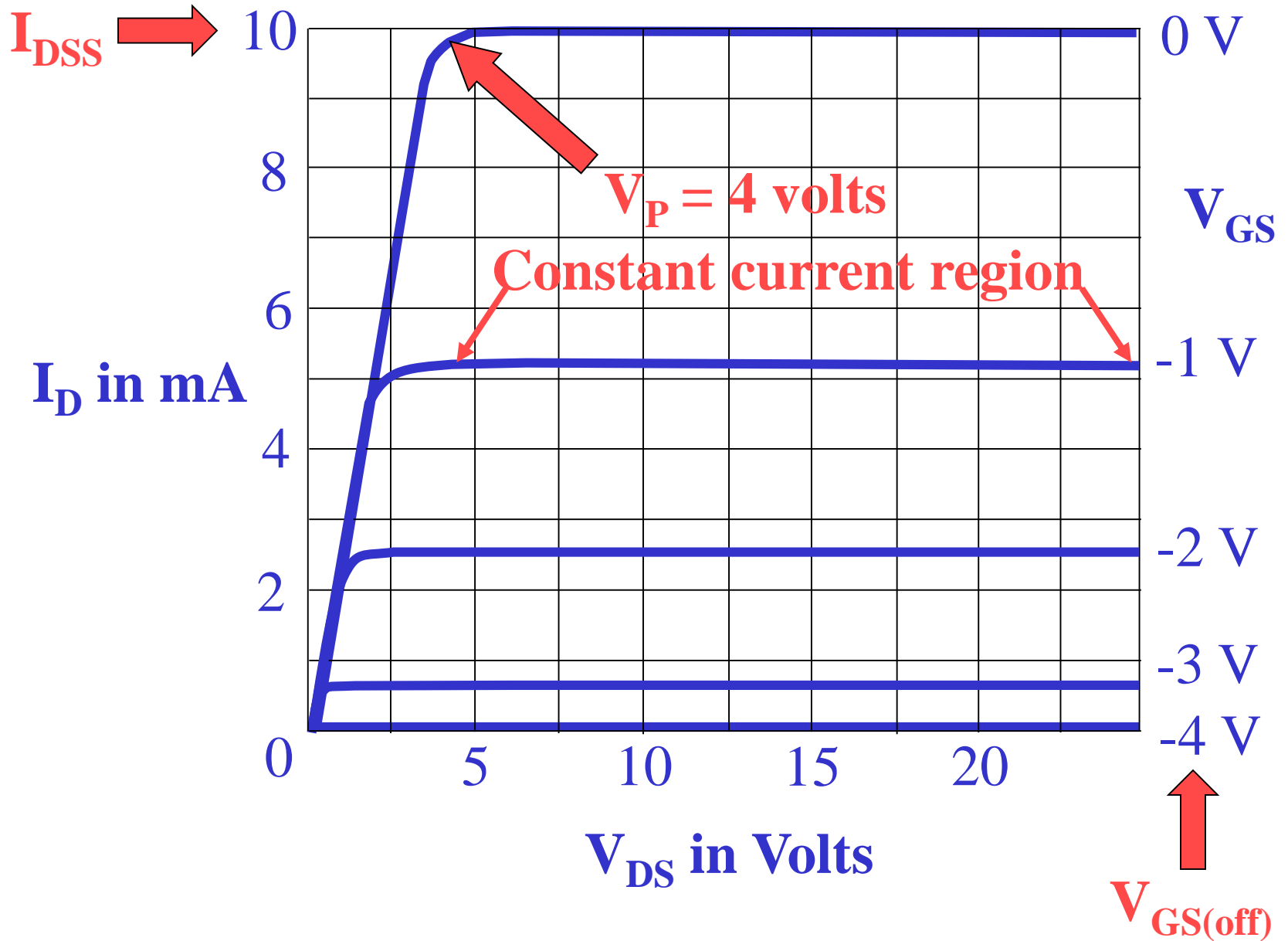- With $V_{GS} = 0$ the drain current is maximum at I_{DSS}
- V_P = the pinchoff voltage
- When $V_{DS} = V_P$ the depletion layers almost touch
- With $V_{DS} > V_P$ the JFET acts as a current source
- $V_{GS(off)} = -V_P$




Ohmic region

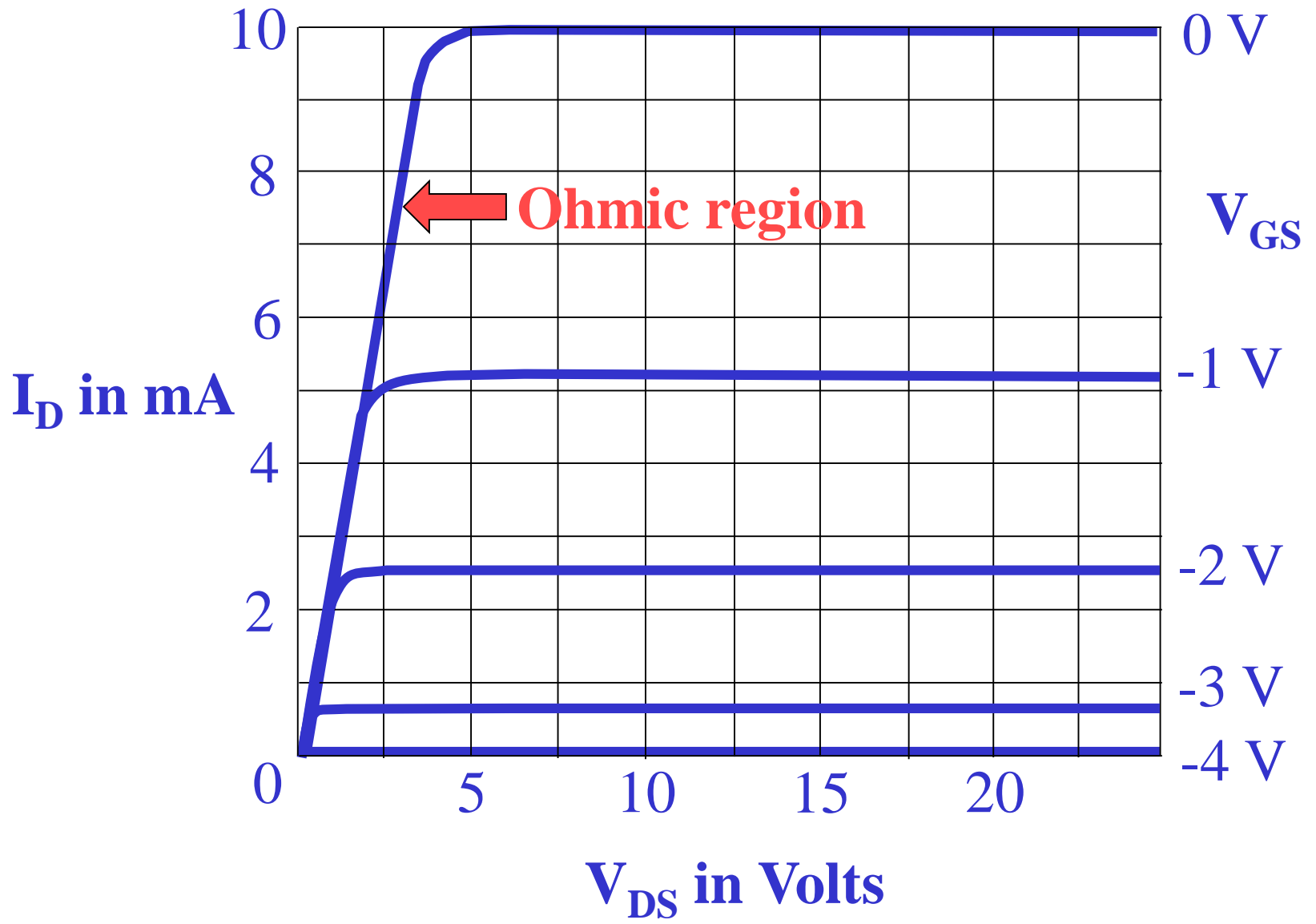
- V_P separates the active region from the ohmic region.
- The ohmic region is the almost vertical part of the drain curve.
- In this region, a JFET acts as a resistor.
- $R_{DS} = V_P / I_{DSS}$



Transconductance curve

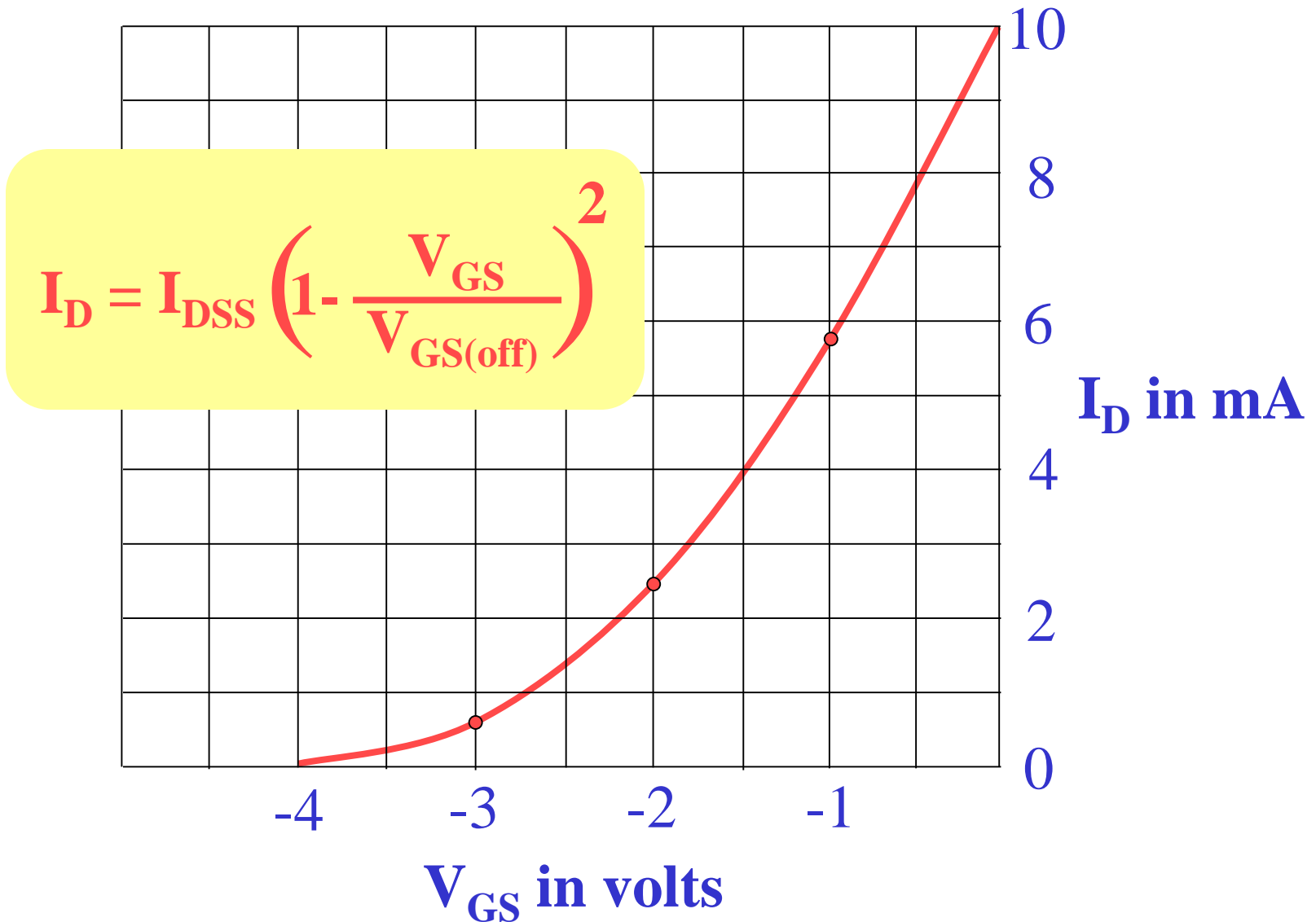


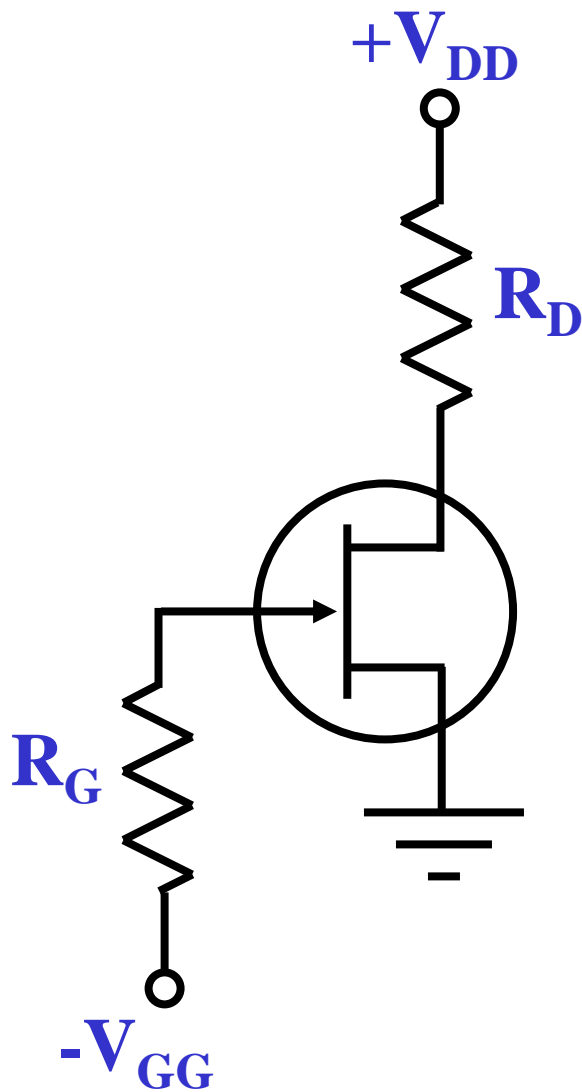Gate bias is suitable for the *ohmic region*.




$$I_{D(\text{sat})} = \frac{V_{DD}}{R_D}$$

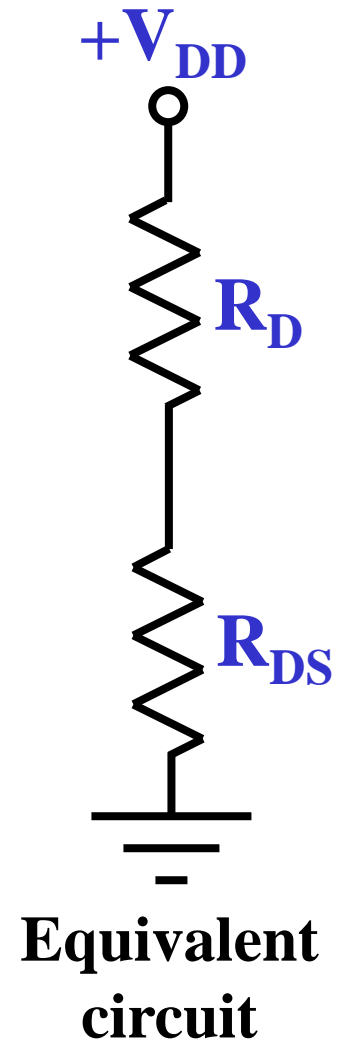
Use 0 volts for V_{GS}
and $I_{D(\text{sat})} \ll I_{DSS}$.



Q point in the ohmic region

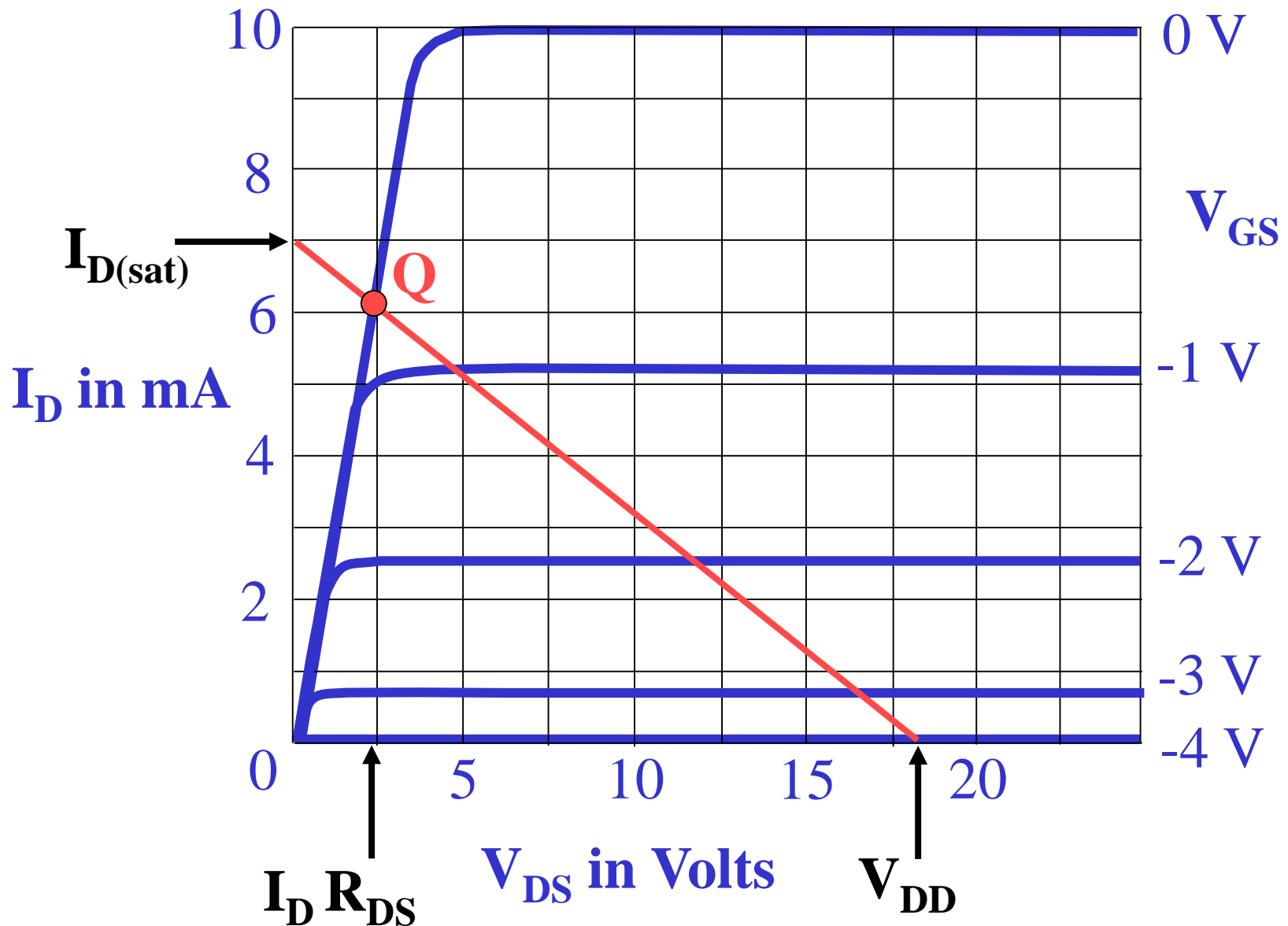

Voltage-divider bias

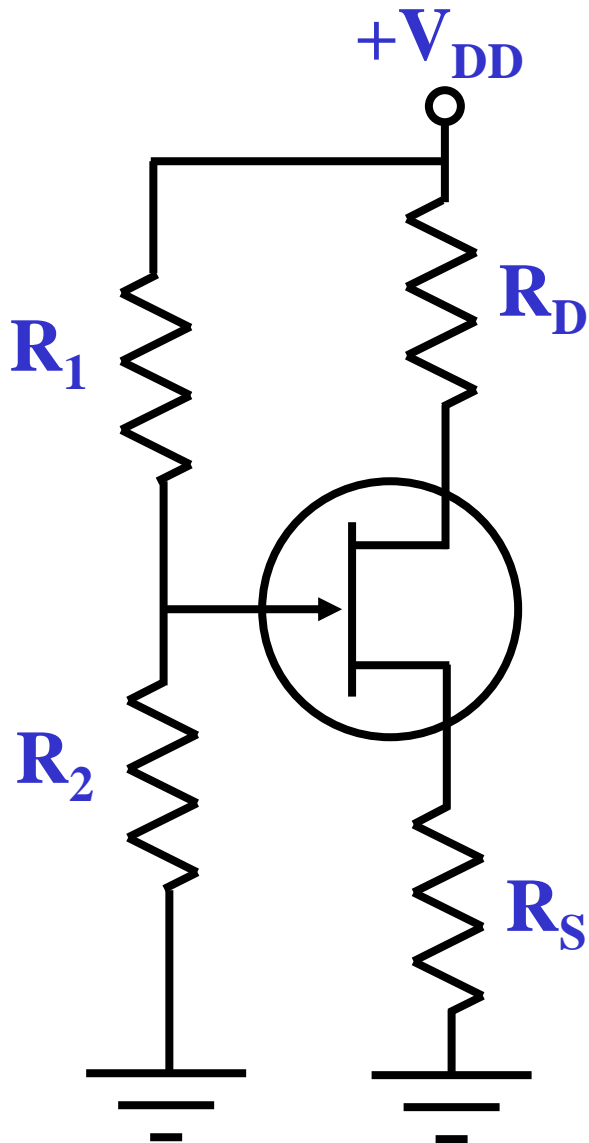


Gate bias is not suitable for the active region.

$$I_{D(\text{sat})} = \frac{V_{DD}}{R_D + R_S}$$

$$V_S = V_G - V_{GS}$$

$$I_{DQ} = \frac{V_G - V_{GS}}{R_S}$$


Q point in the active region

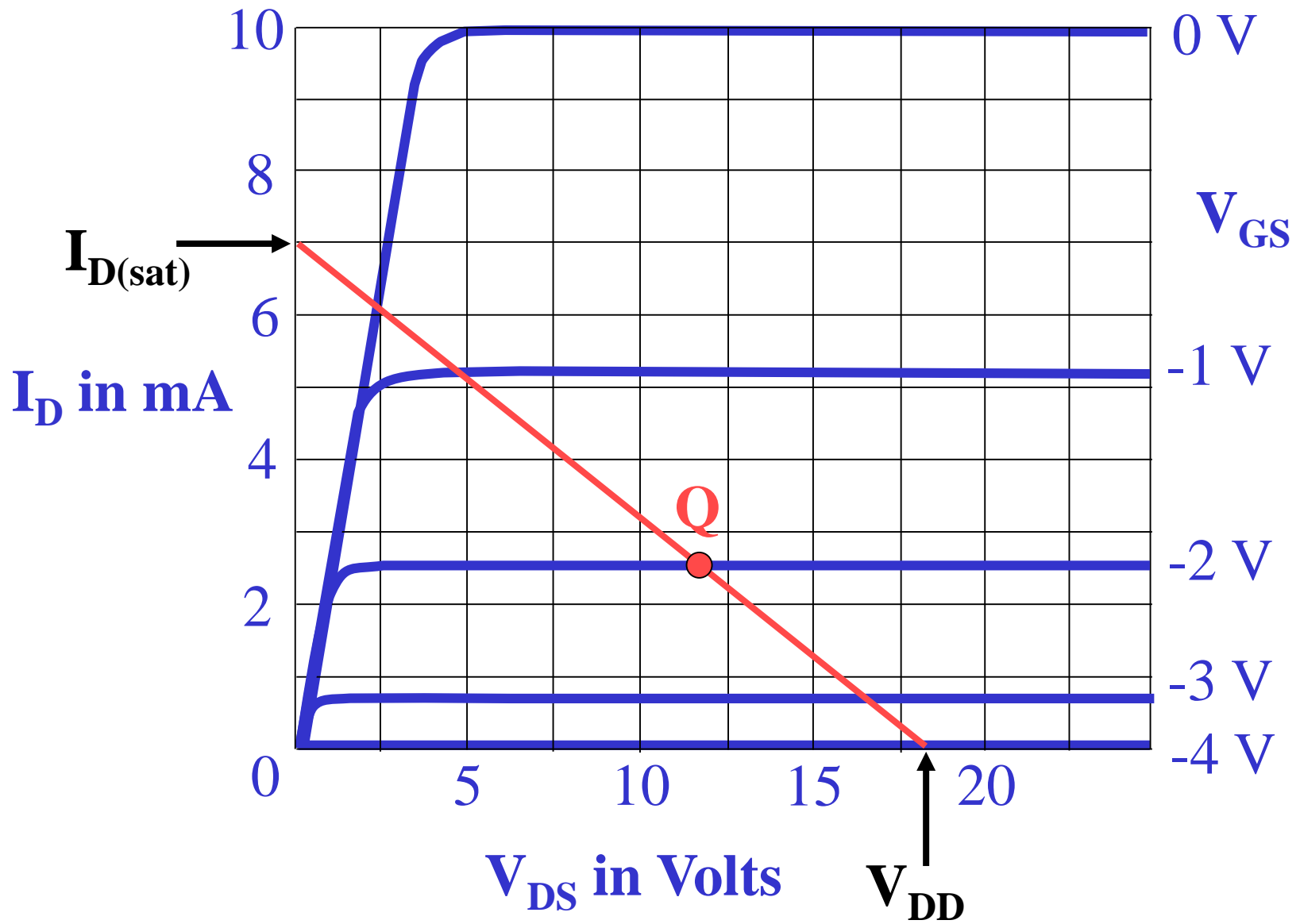


Transconductance

- Tells how effective the gate voltage is in controlling the drain current.
- $g_m = i_d / v_{gs}$
- Common units for JFETs are the micromho (μmho) or the more modern microsiemen (μS).
- g_m is the slope of the transconductance curve.
- g_{m0} is the maximum value and occurs at $V_{GS} = 0$.


Transconductance curve

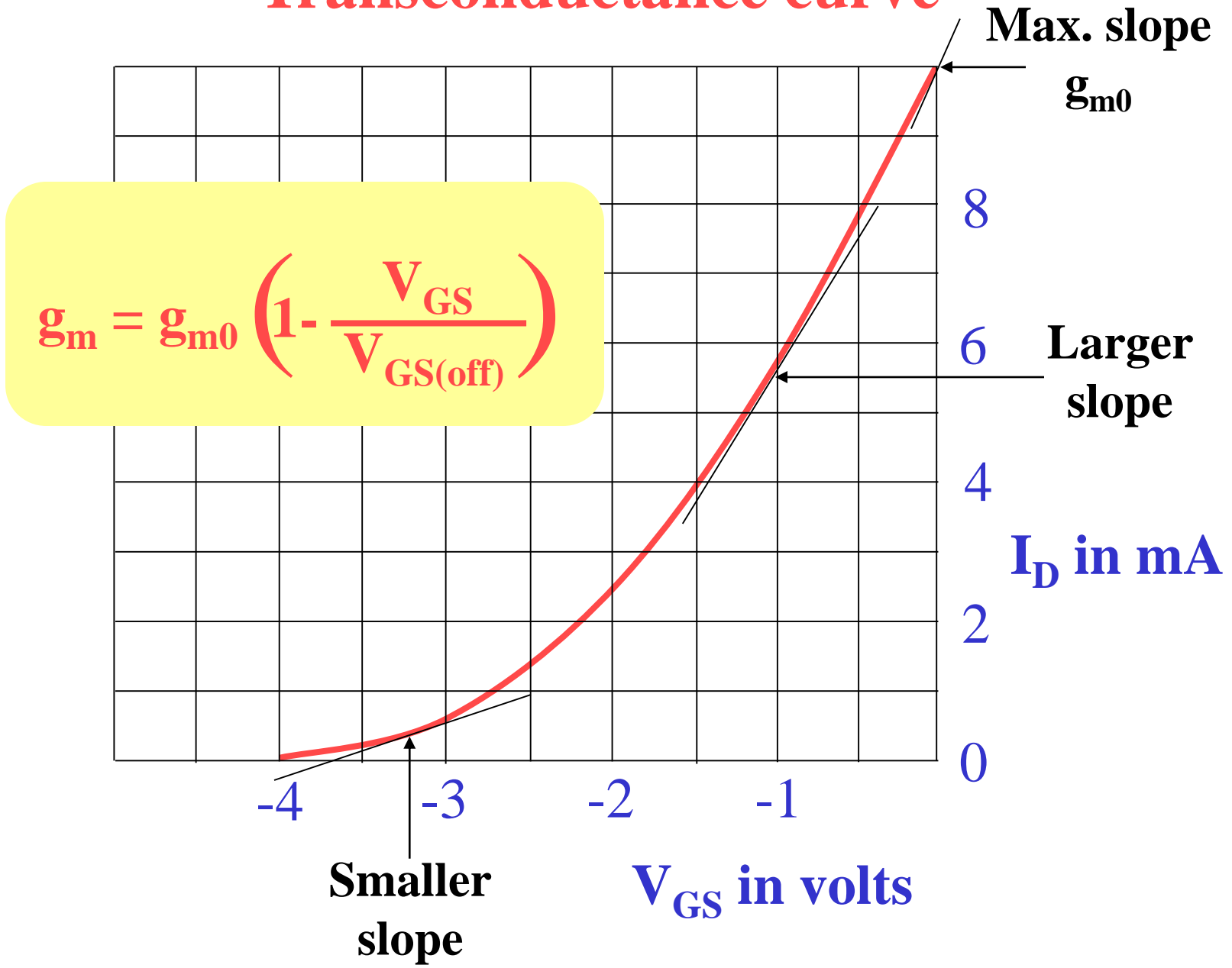


Common-source amplifier

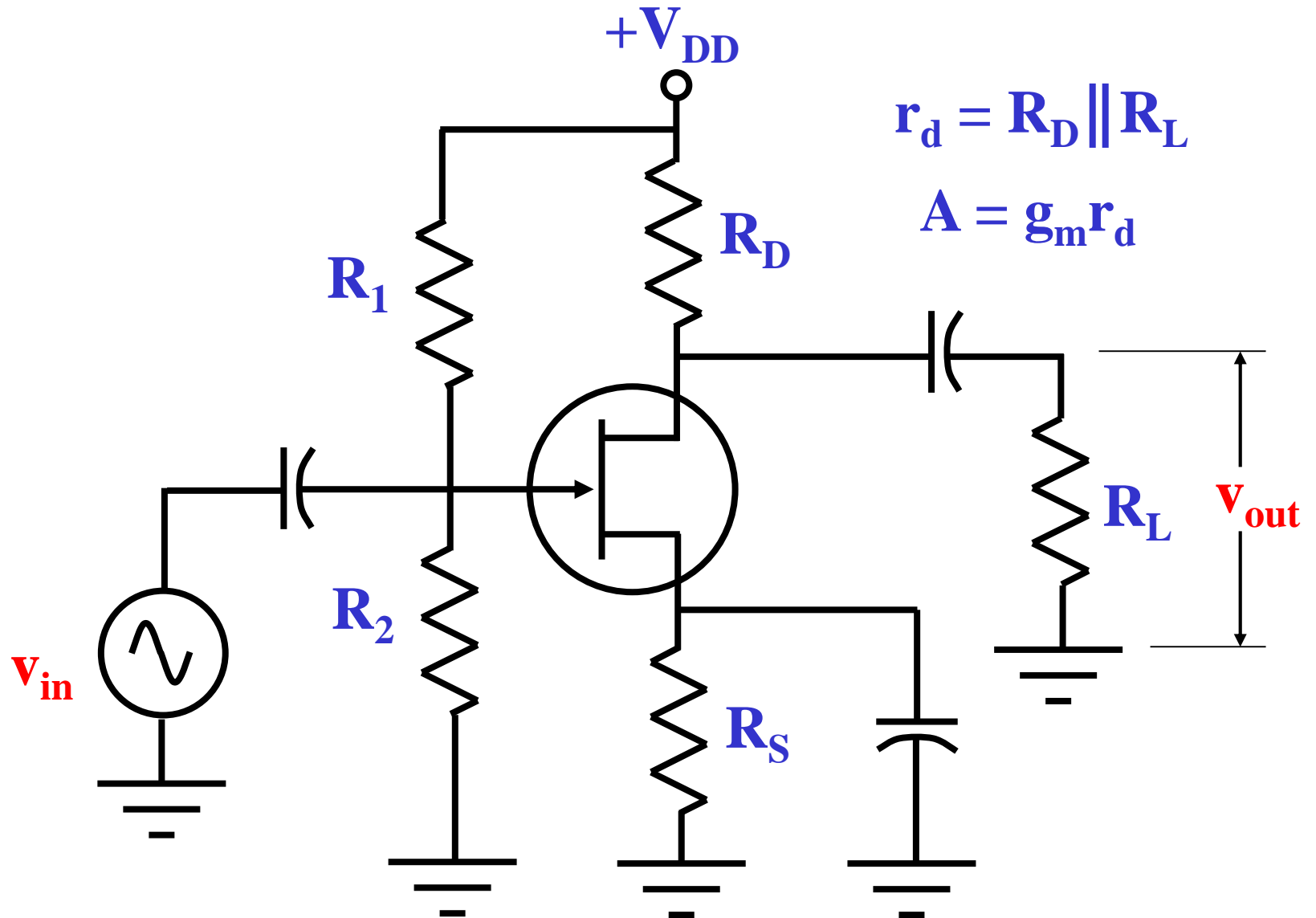

Source follower

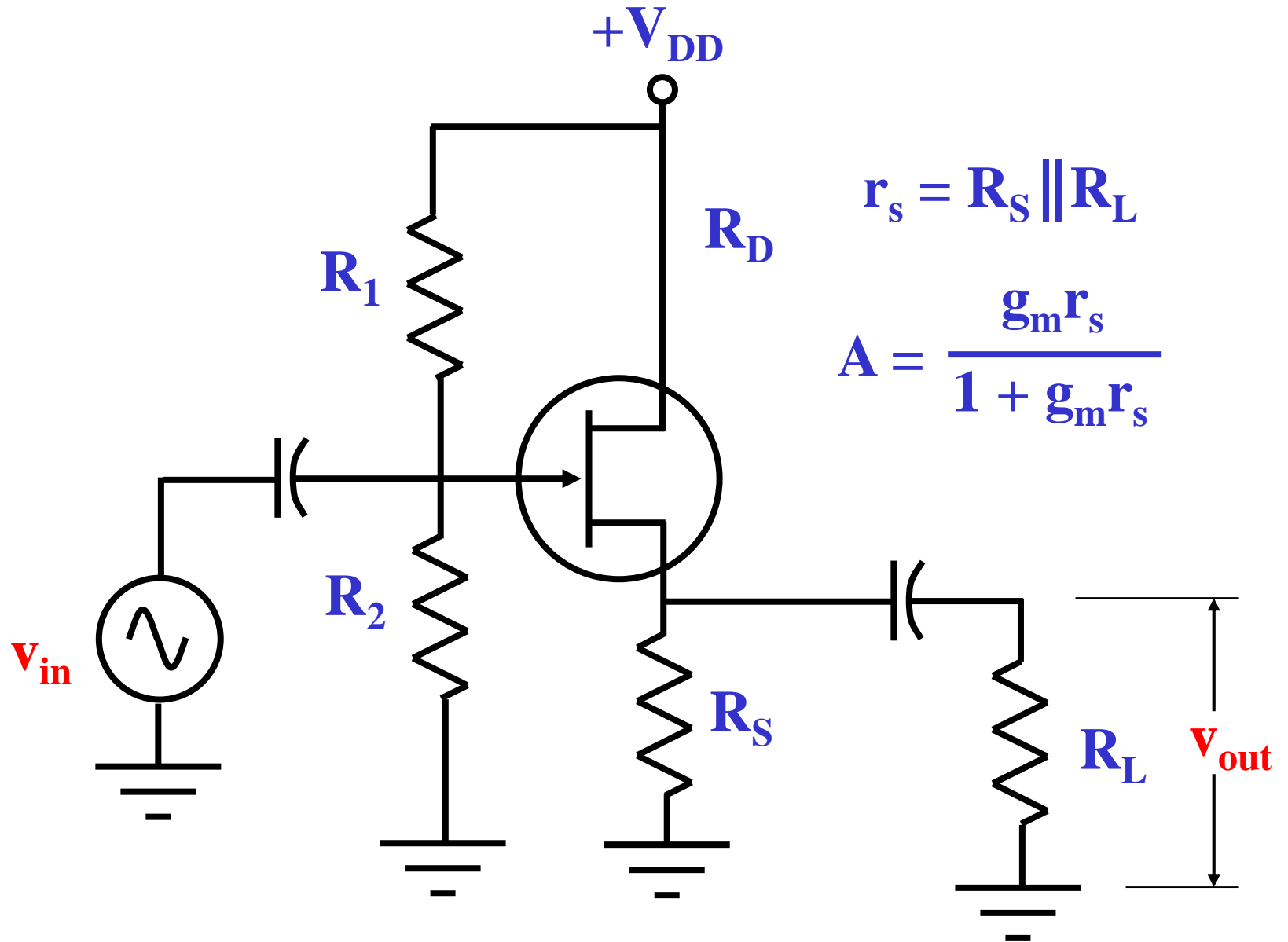


Shunt analog switch

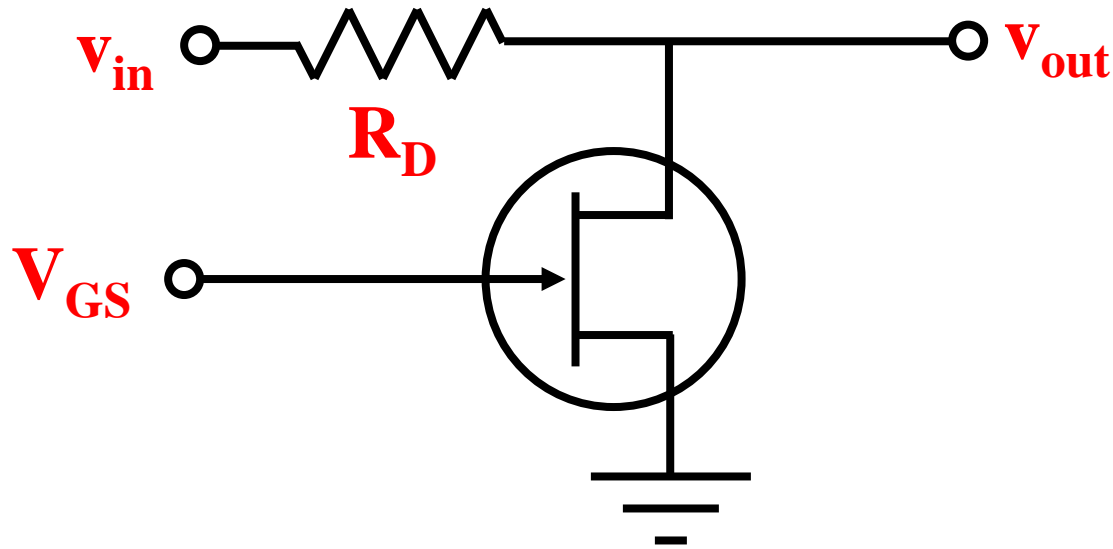

$$v_{in} < 100 \text{ mV}$$


$$R_D \gg R_{DS}$$

Series analog switch

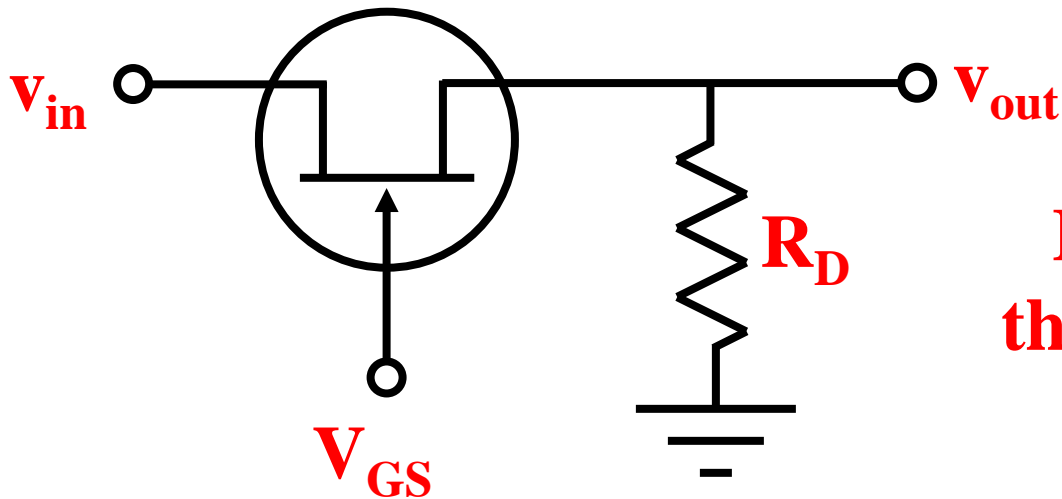

**Better on-off ratio
than the shunt switch**

Multiplexer

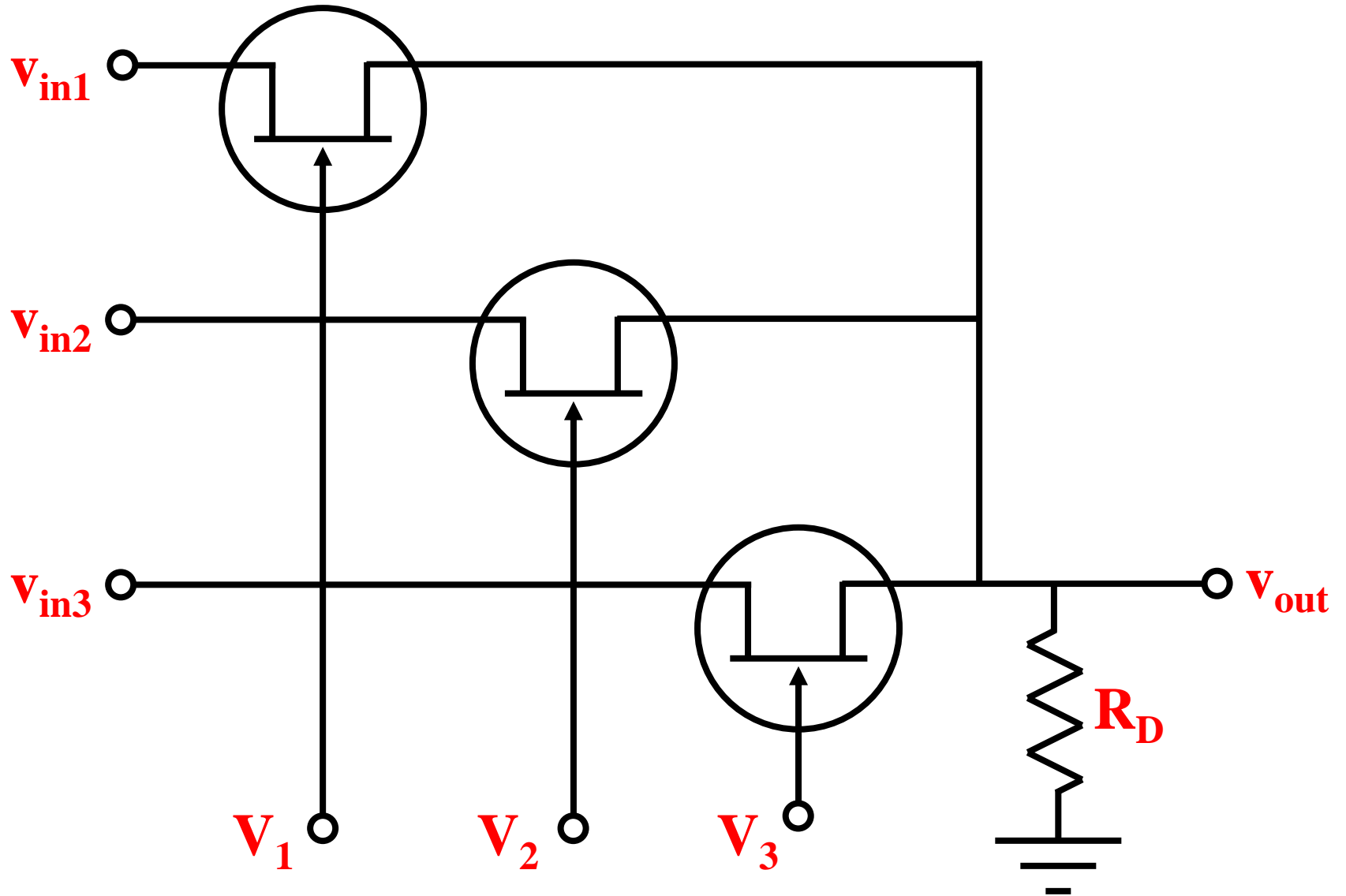

Voltage-controlled resistance

- Operates in the ohmic region with V_{GS} values between 0 and cutoff.
- Works well for ac signals of 200 mV_{PP} or less.
- Small-signal resistance: $r_{ds} = V_{DS}/I_D$
- As V_{GS} becomes more negative, r_{ds} increases.
- Both series and shunt operation can be used.