

Thyristor

Elektronika


(TKE 4012)

Eka Maulana

Thyristor

- **Thyristor**: devais semikonduktor solid state empat layer dari bahan type-n dan type-p yang berfungsi sebagai *Saklar Elektronik*
- **Jenis**: SCR, DIAC, TRIAC
photothyristor

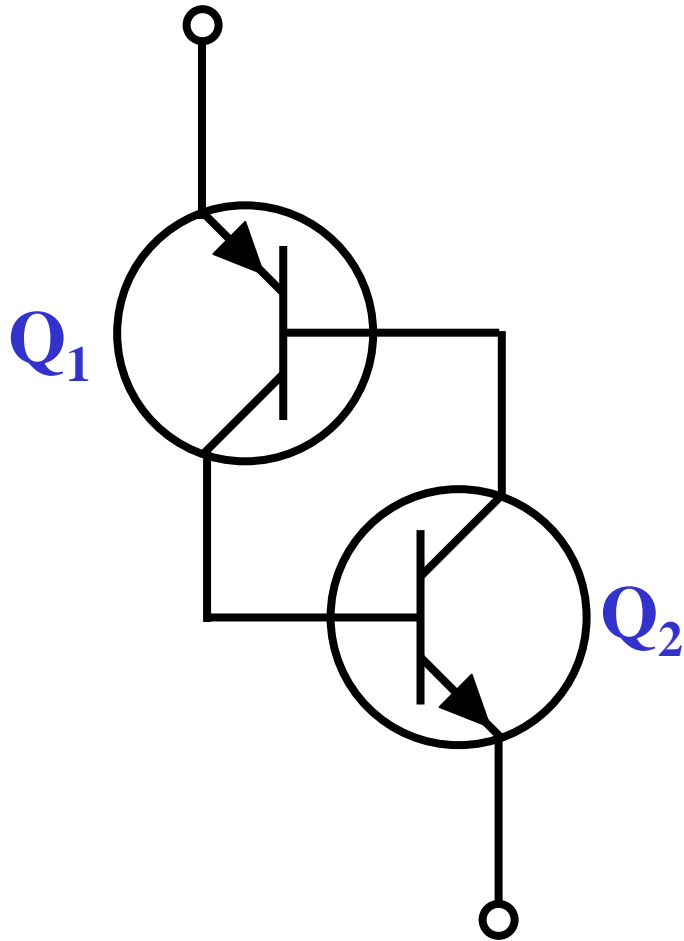This latch is stable in either of two states.



Latch




On state




Off state




The four-layer diode

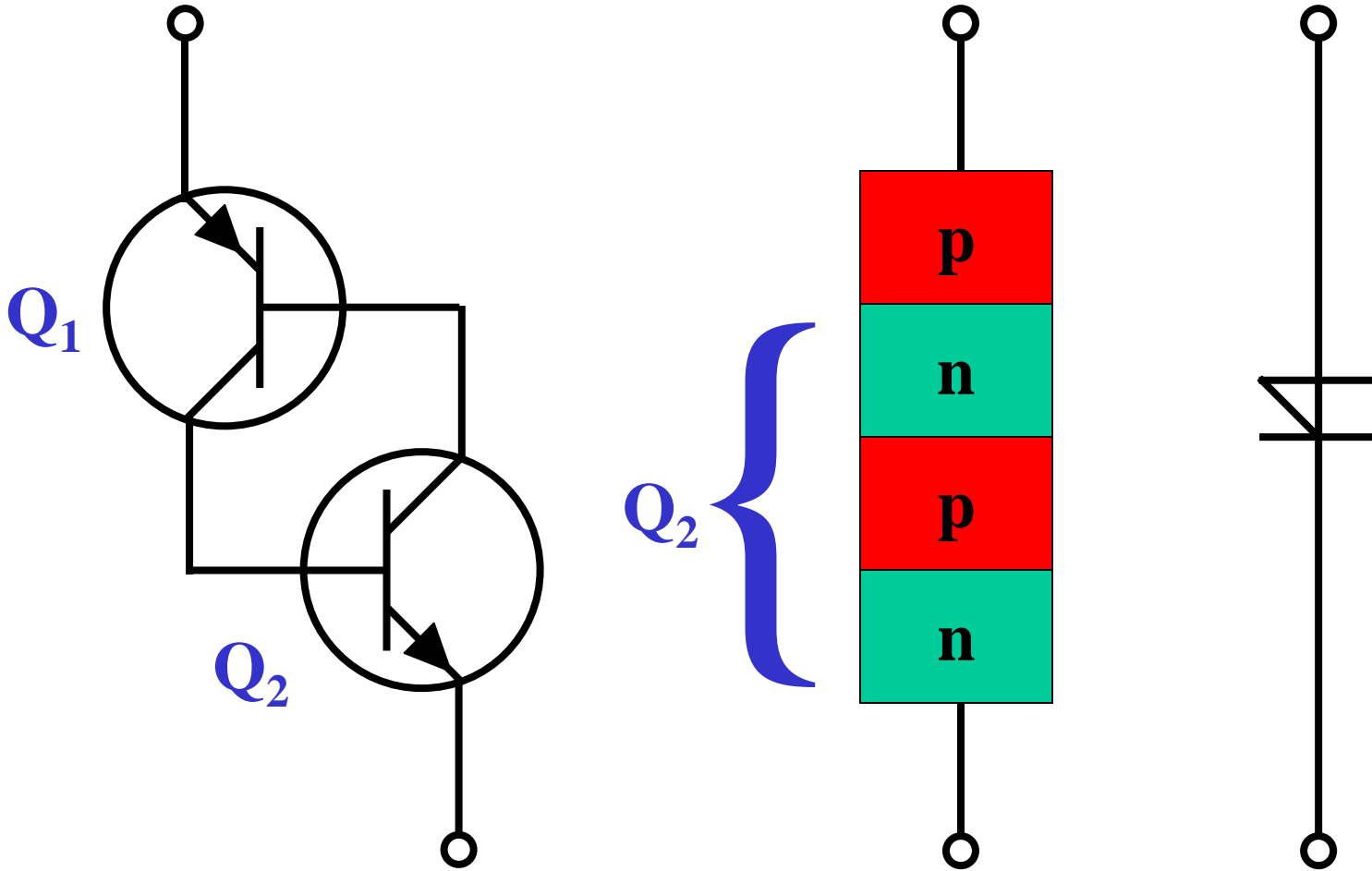

Four-layer diode breakover

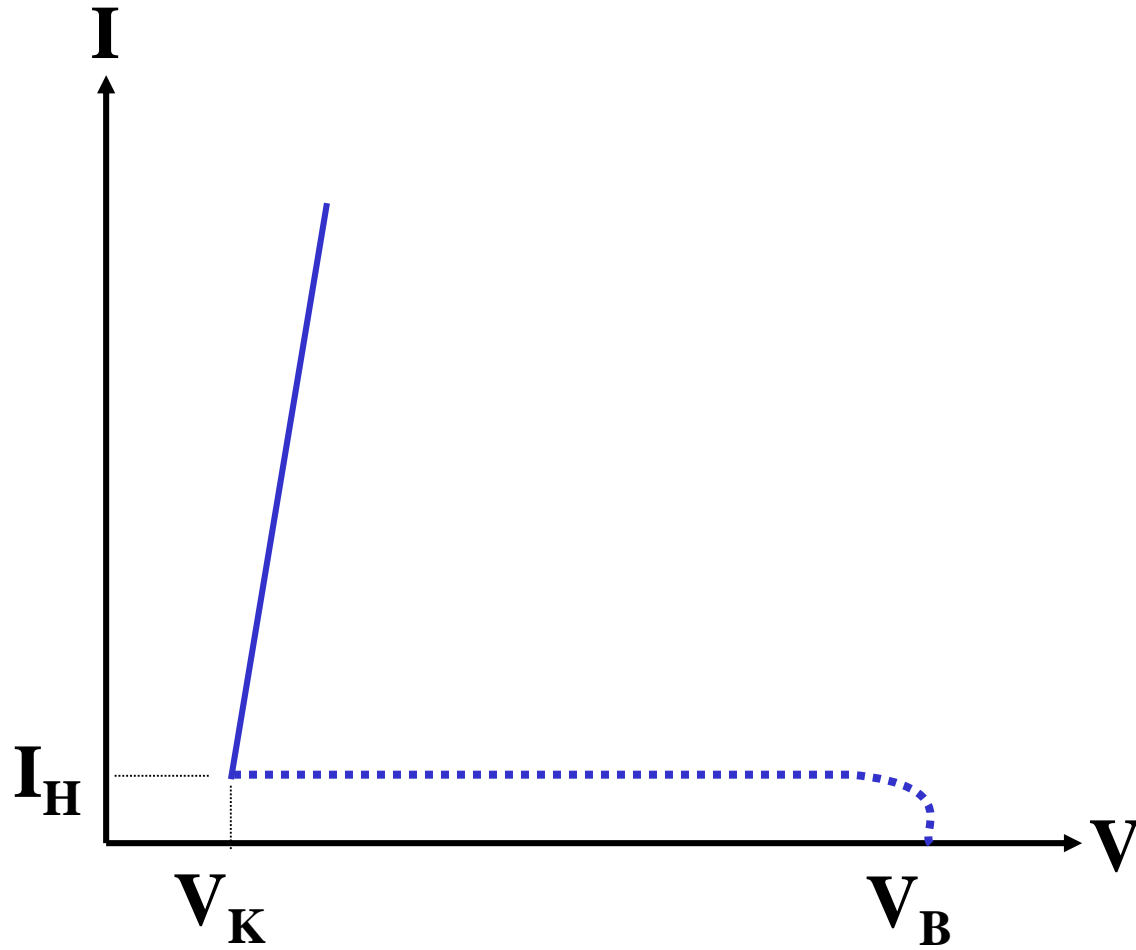


The silicon controlled rectifier (SCR)

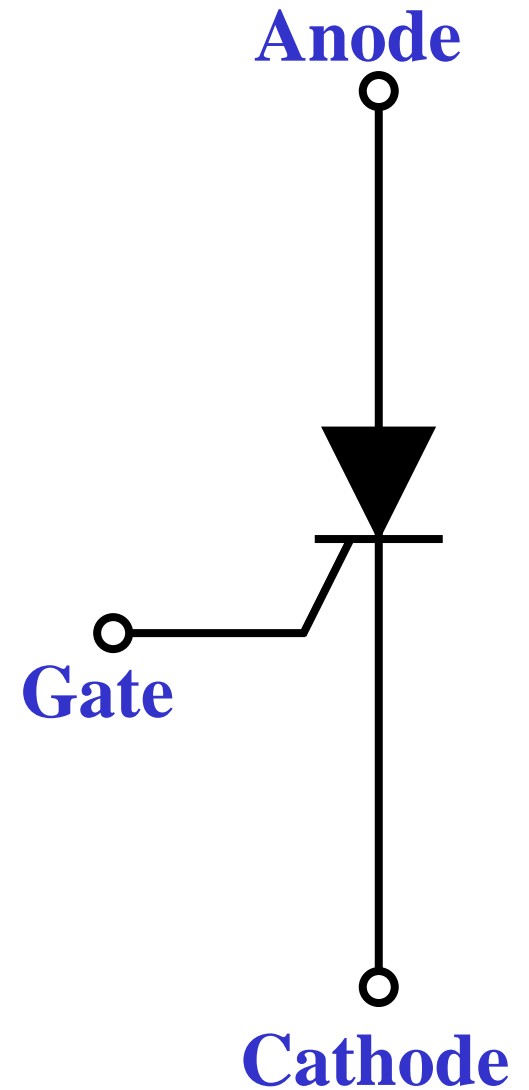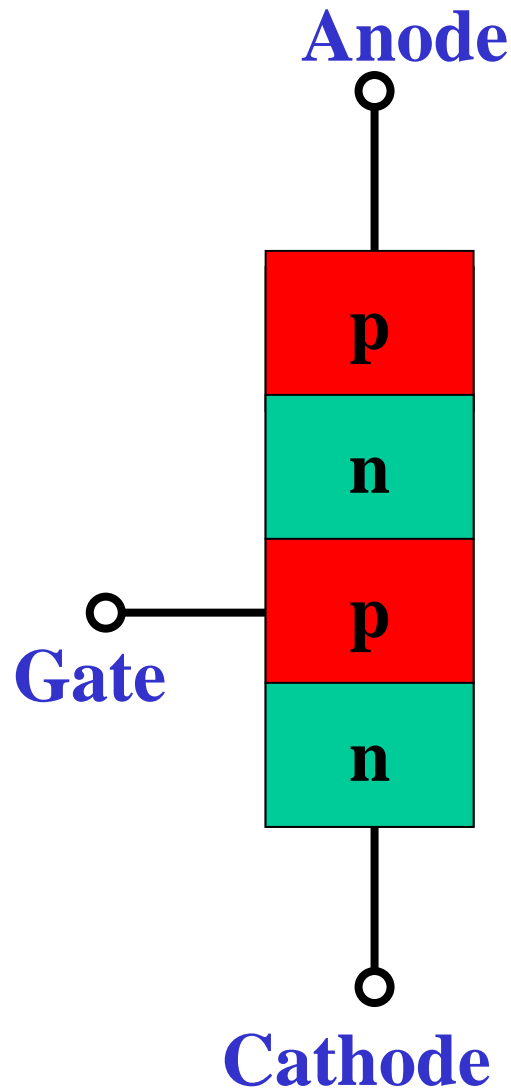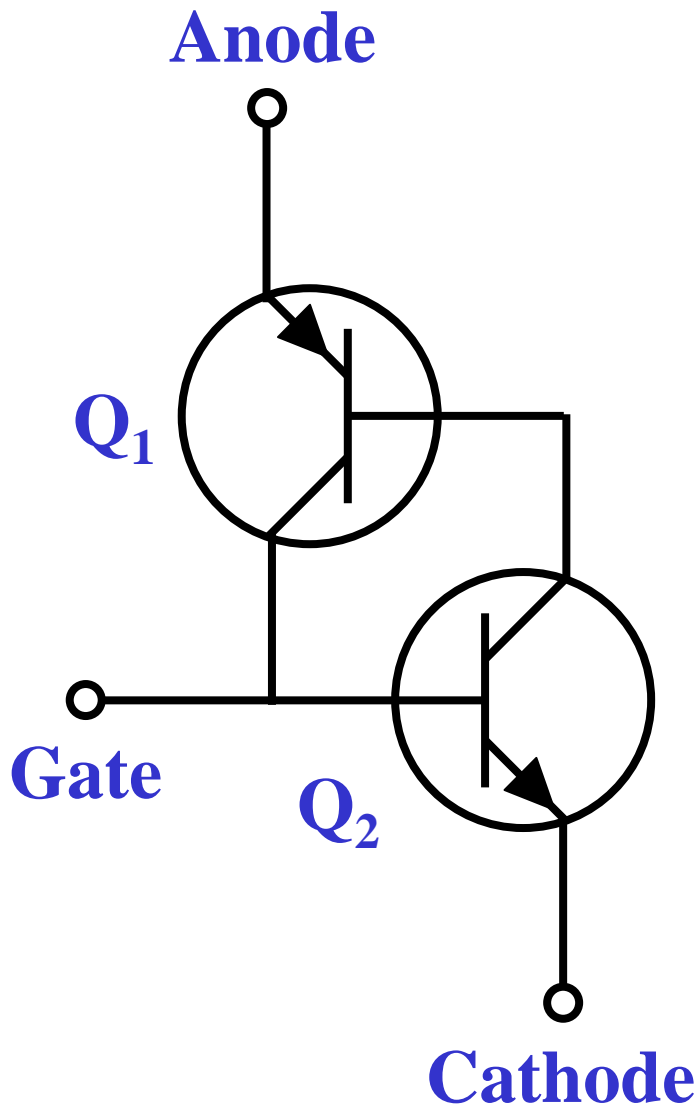


SCRs

- **The most widely used thyristors**
- **Use gate triggering for turn-on instead of breakover triggering**
- **Data sheets list the gate trigger voltage (V_{GT}) and the gate trigger current (I_{GT})**
- **Turn-off requires reducing the current to less than the holding current (I_H)**

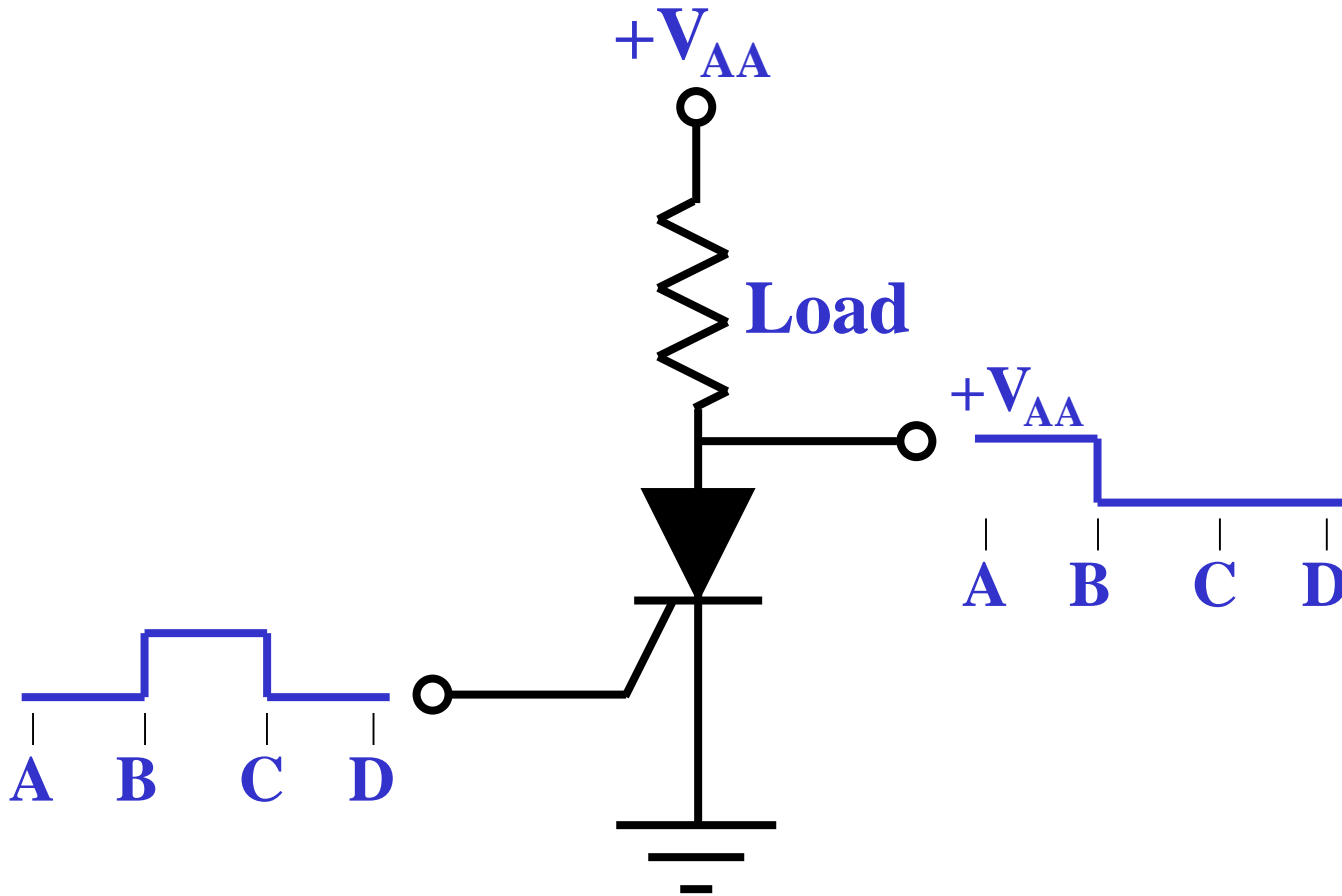An SCR does not turn off at the end of the trigger pulse.




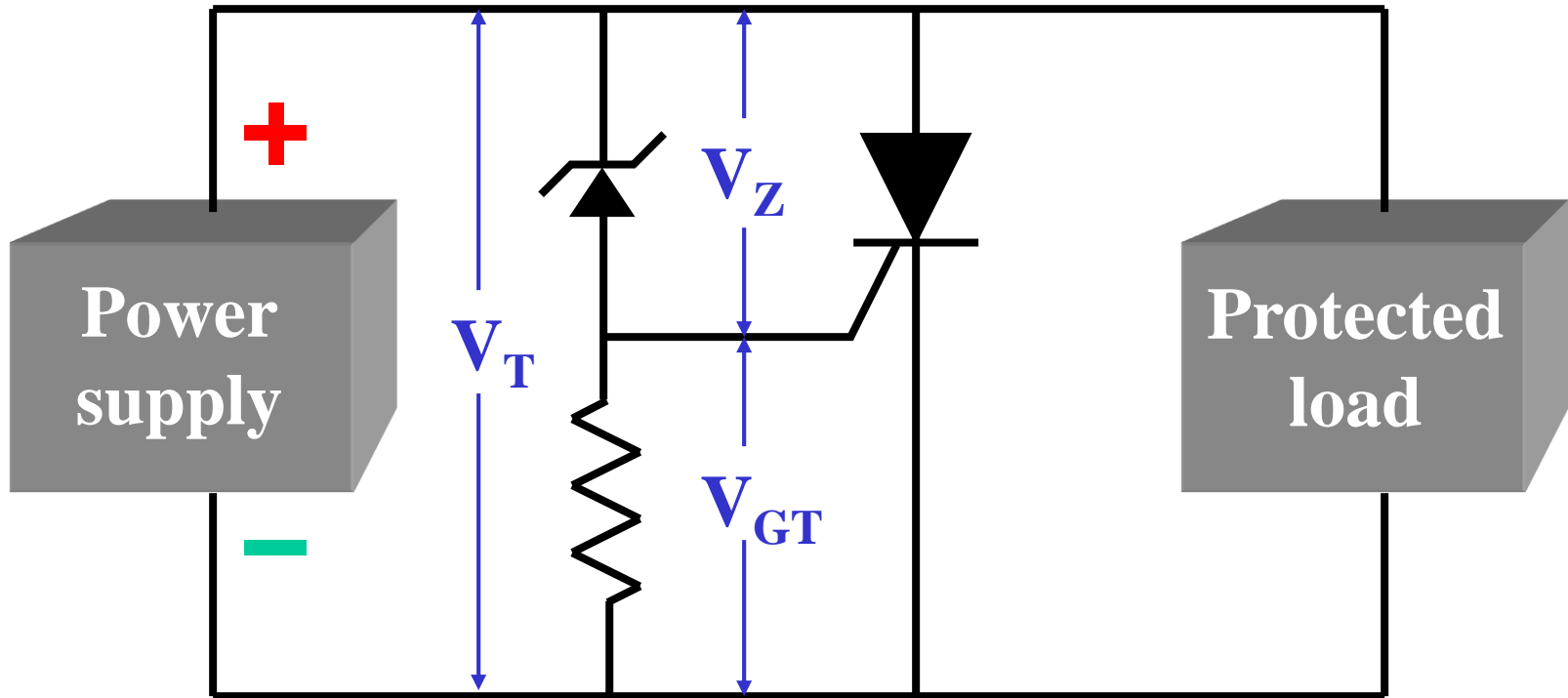SCR crowbar to protect a load from overvoltage




The overvoltage that triggers the crowbar: $V_T = V_Z + V_{GT}$

Adding gain to a crowbar circuit

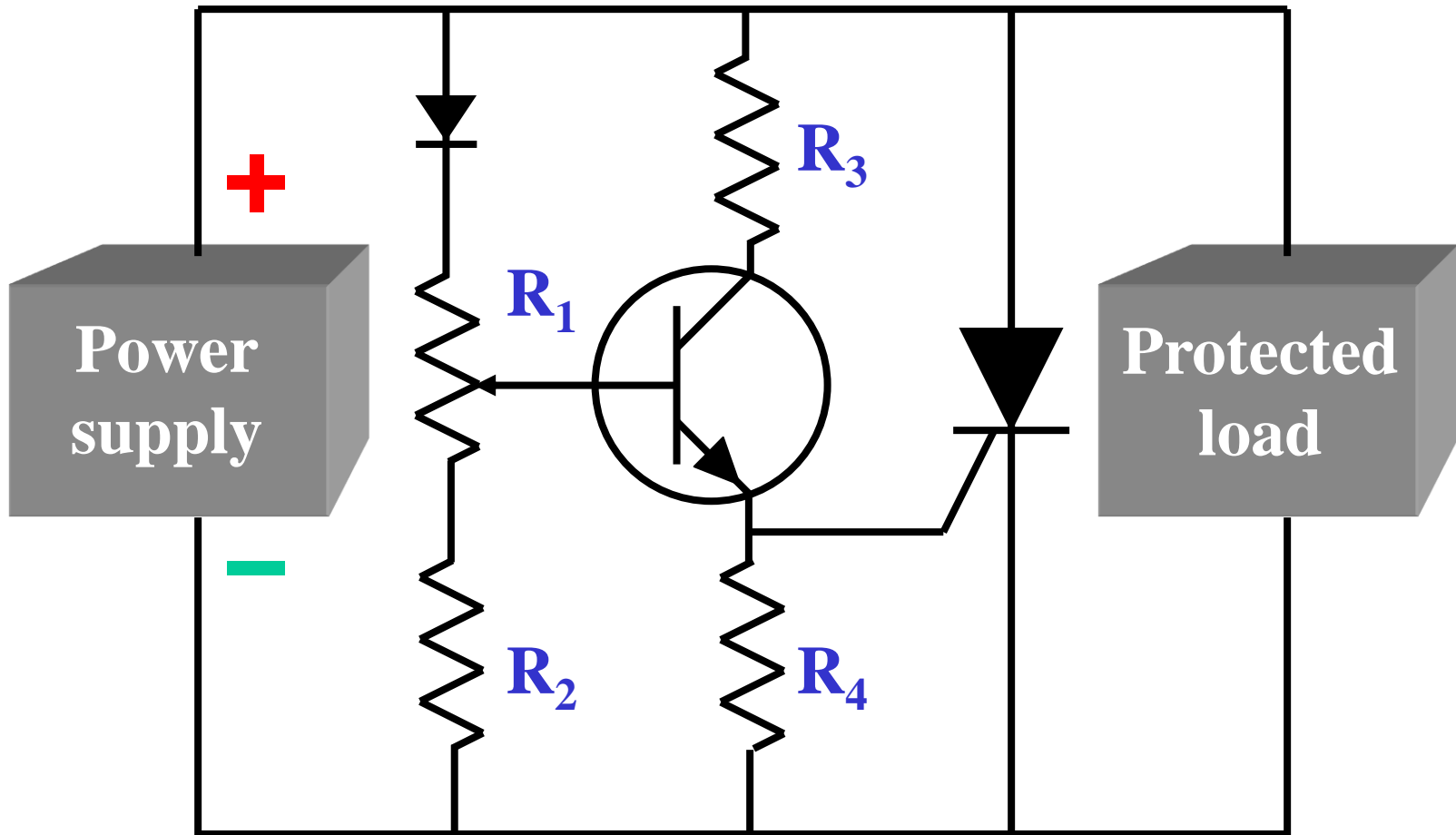



R_1 is the trigger adjust

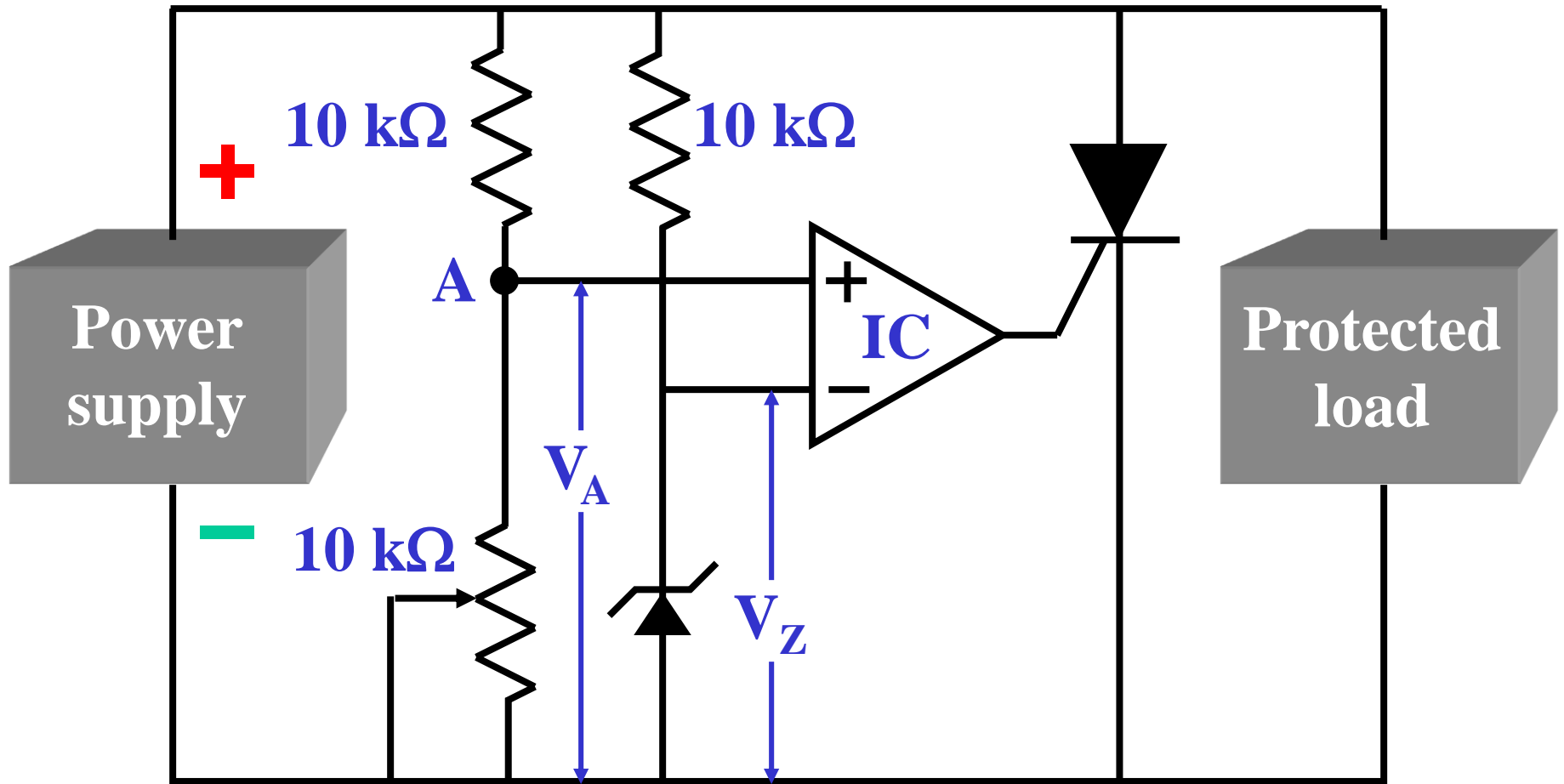Adding an IC amplifier to a crowbar circuit




The circuit triggers when V_A exceeds V_Z .


SCR phase control

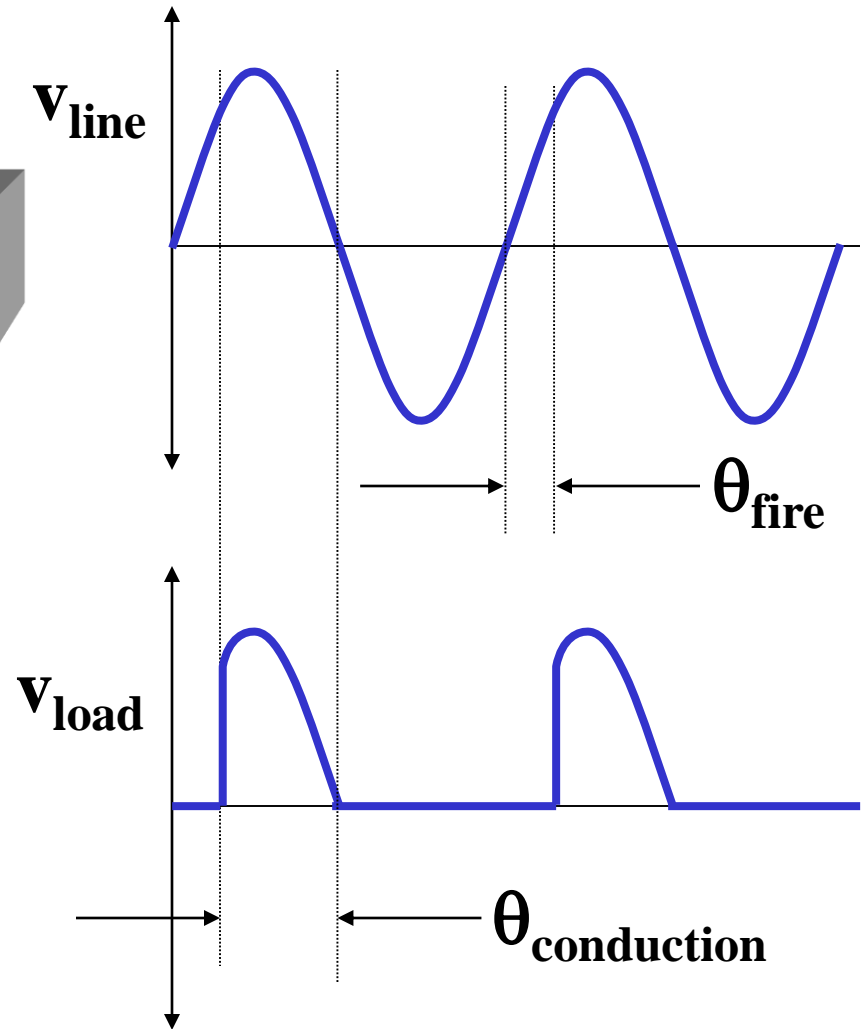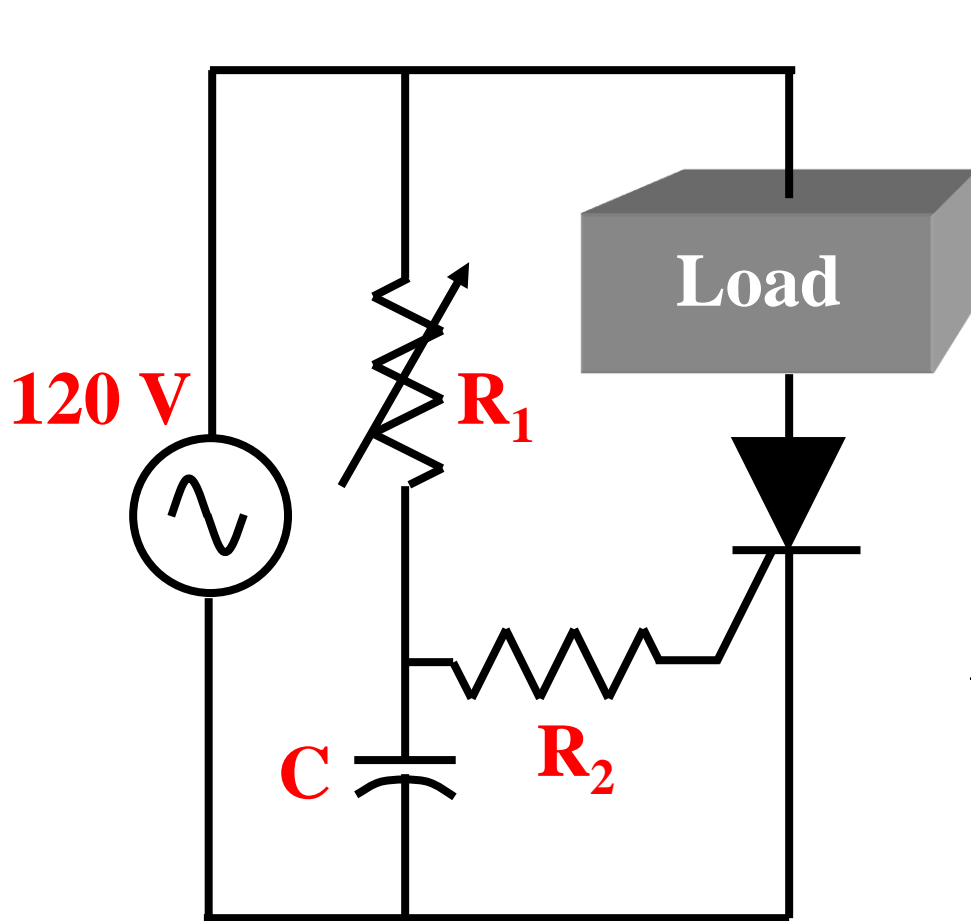

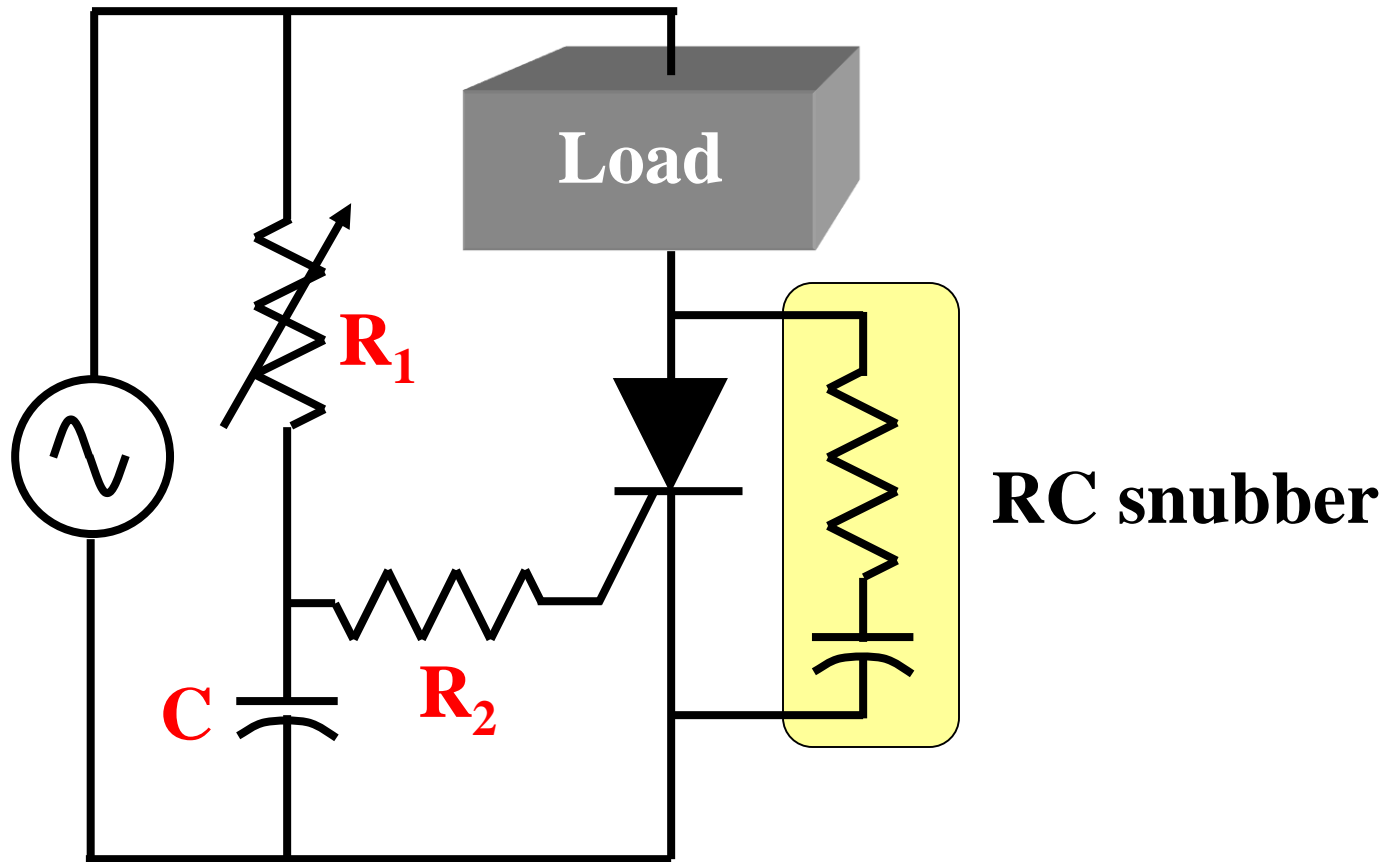
A snubber network can be used to limit the rate of voltage rise across the SCR.



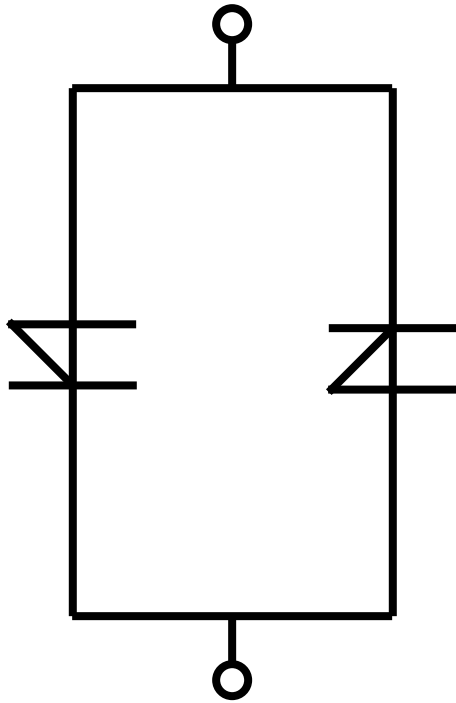Bidirectional thyristors can conduct in either direction.




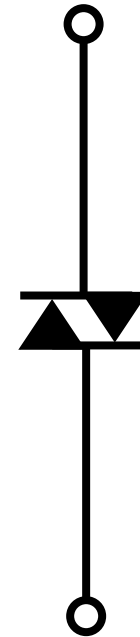**Four-layer diodes
in reverse parallel**




Diac

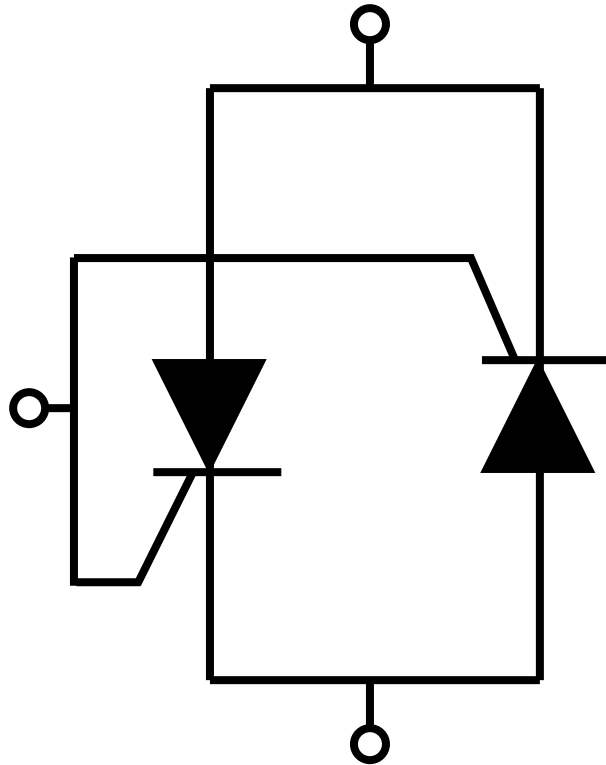The triac is a popular bidirectional thyristor.





**SCRs in
reverse parallel**

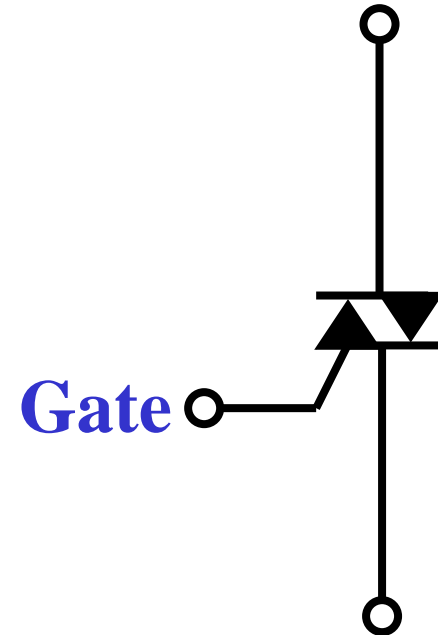


Triac

Triac phase control

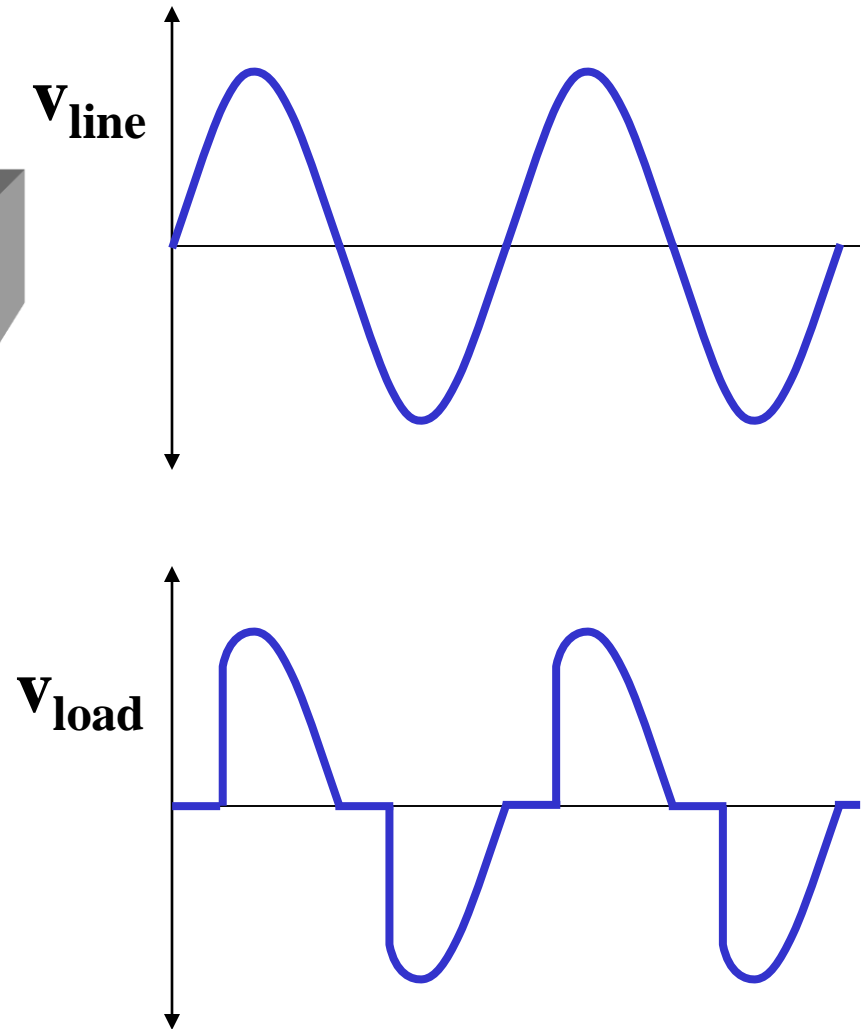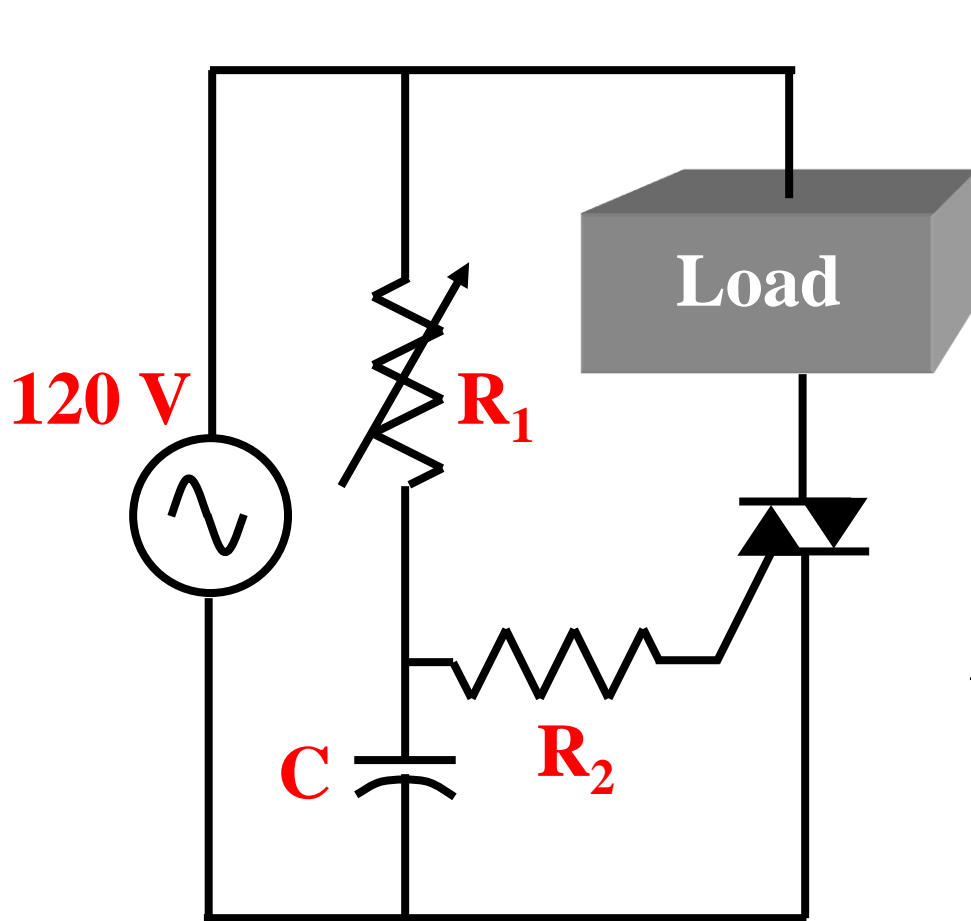


Triac crowbar

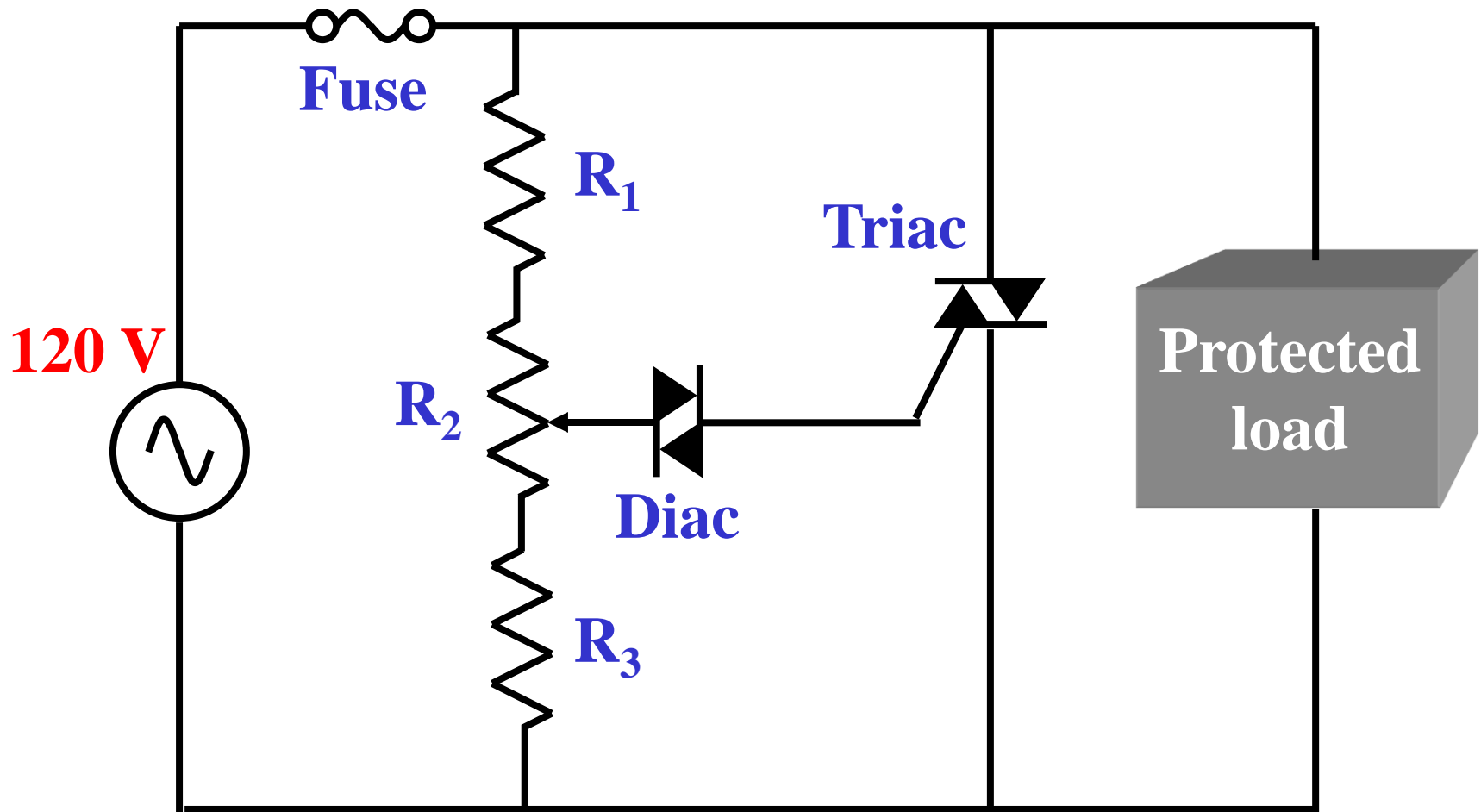


R_2 is the trigger adjust

The photo-SCR is triggered by light.

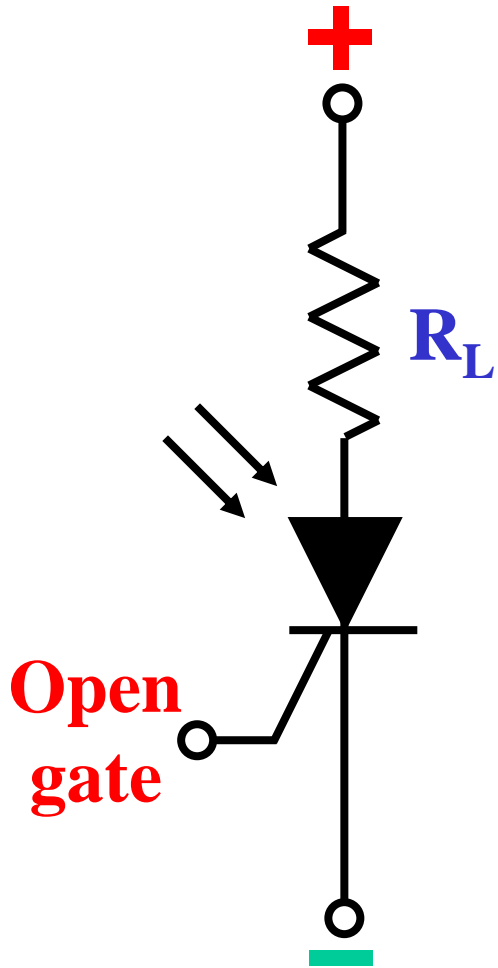


Maximum sensitivity


Sensitivity adjust

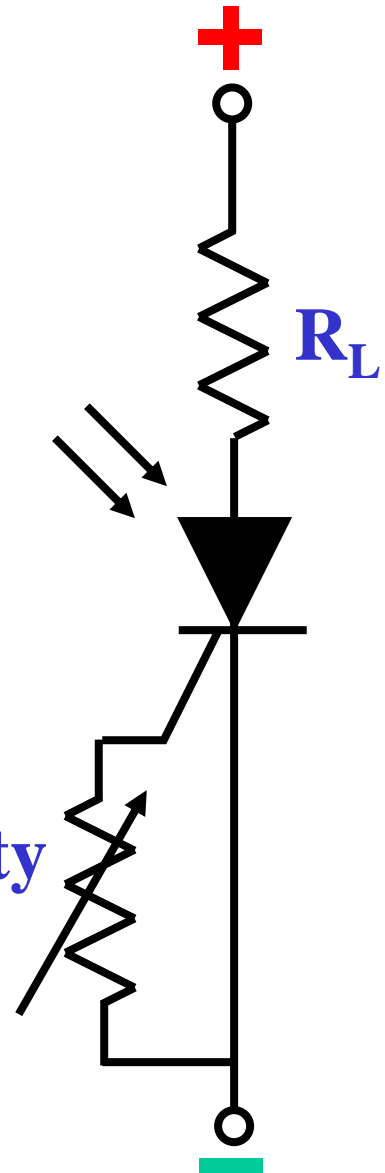

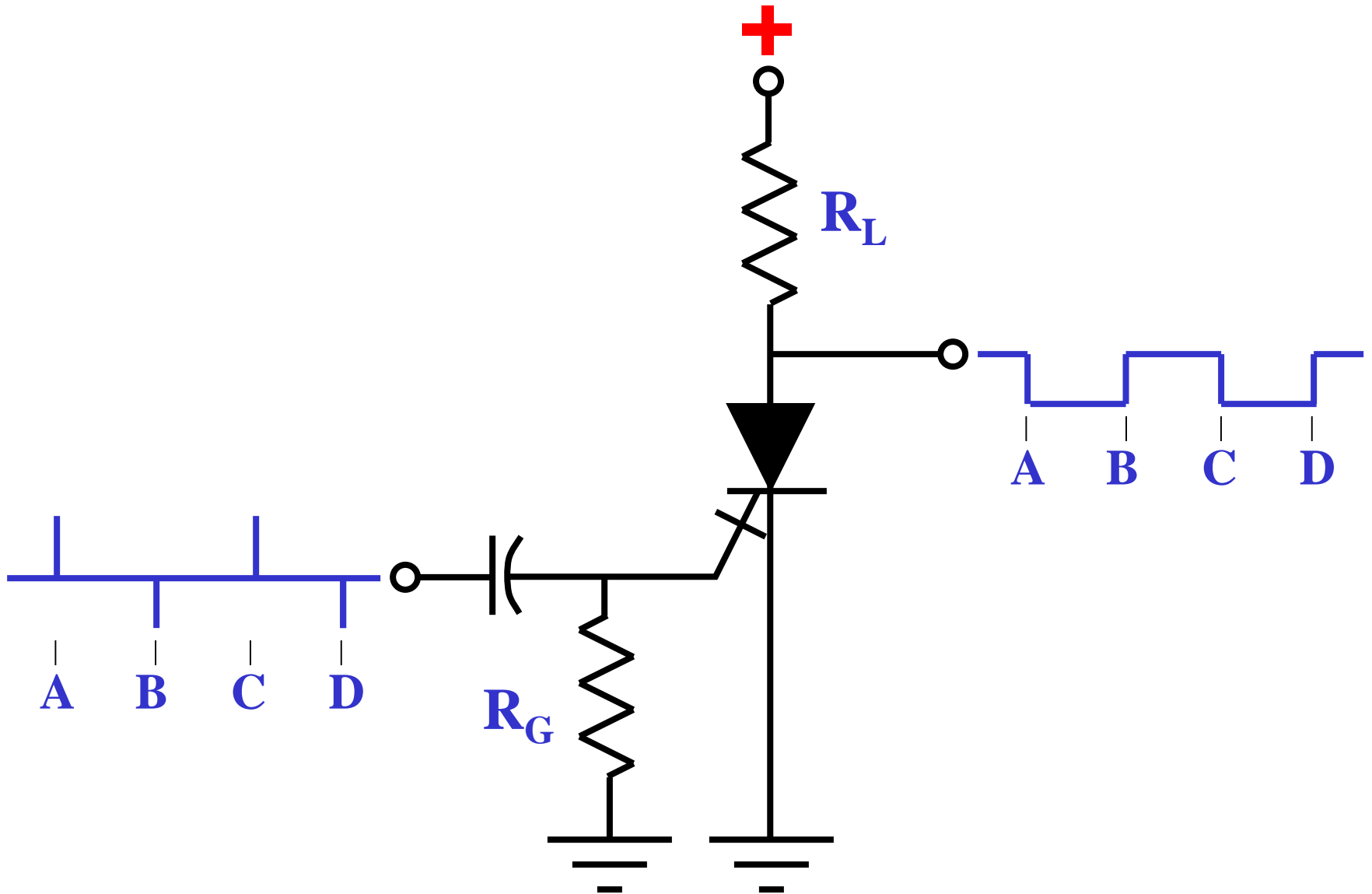The gate-controlled switch is turned off with a reverse-biased trigger.




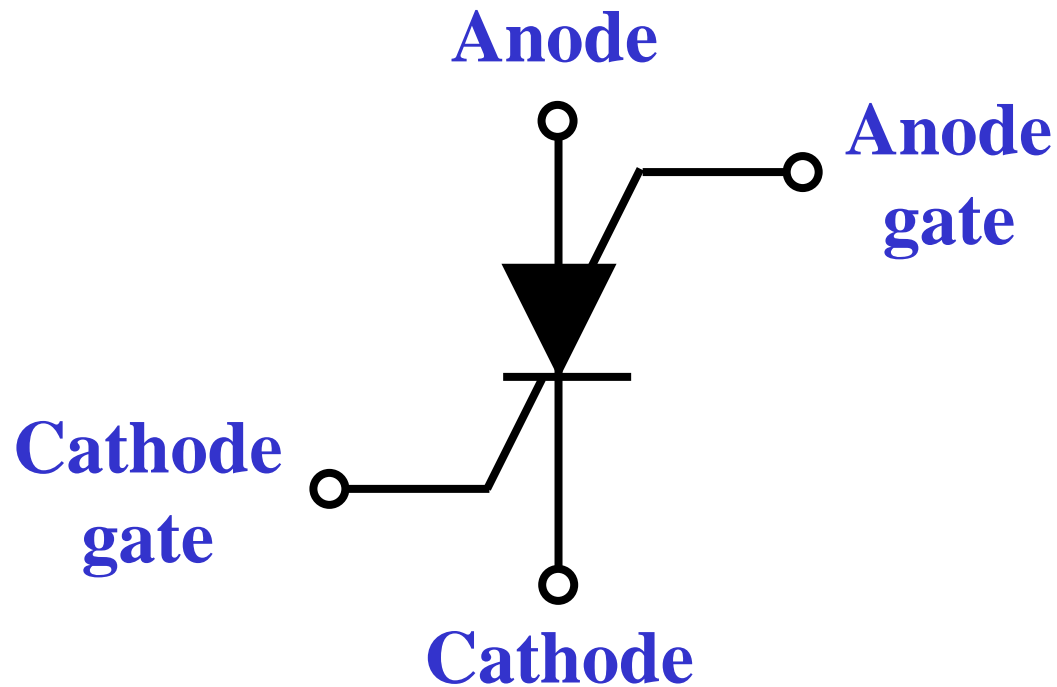**The silicon-controlled switch is
a low-current device.**



Either gate can be used to trigger or open this device.

Unijunction transistor (UJT)

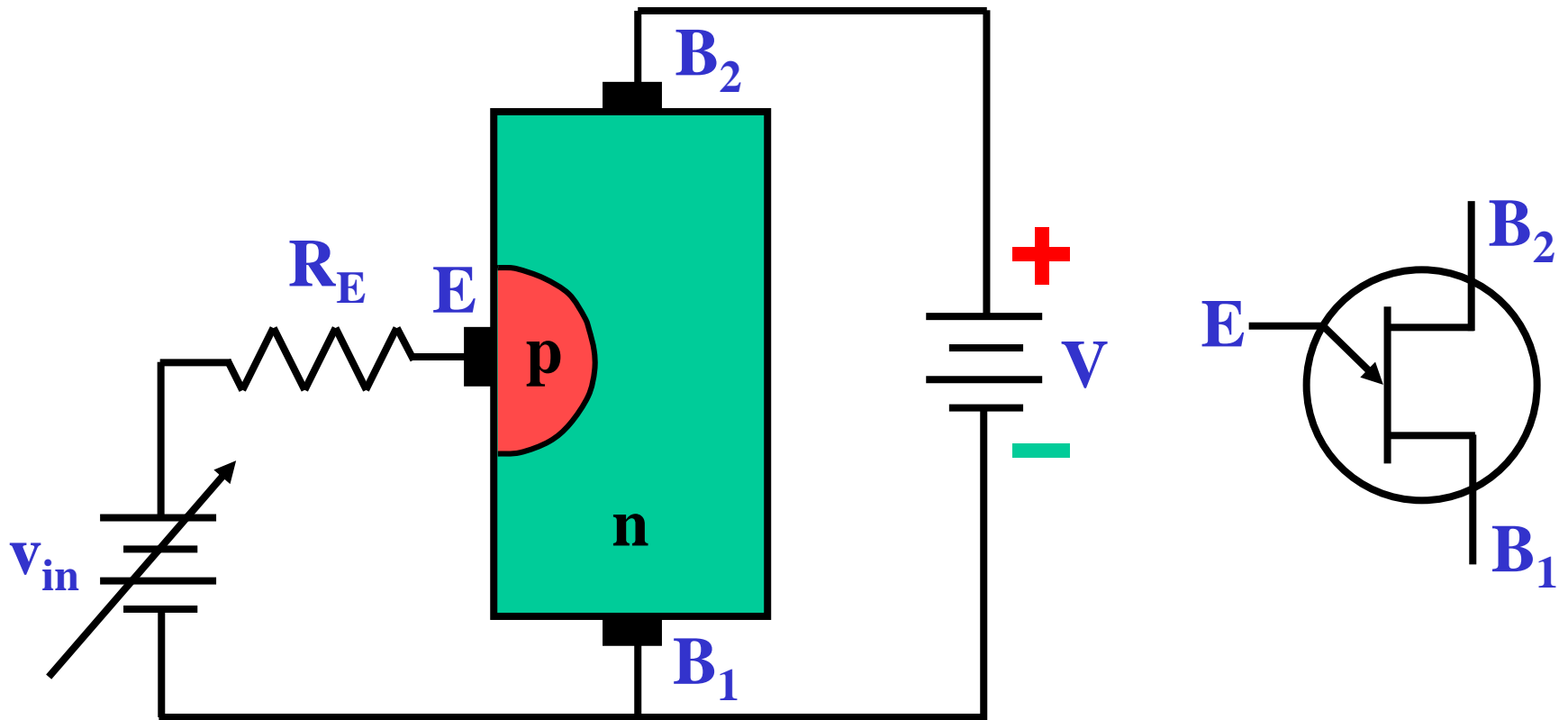

When v_{in} reaches the standoff voltage, the resistance between the emitter and B_1 drops dramatically.