


Penguat Diferensial

# Elektronika

(TKE 4012)


Eka Maulana

# A differential amplifier

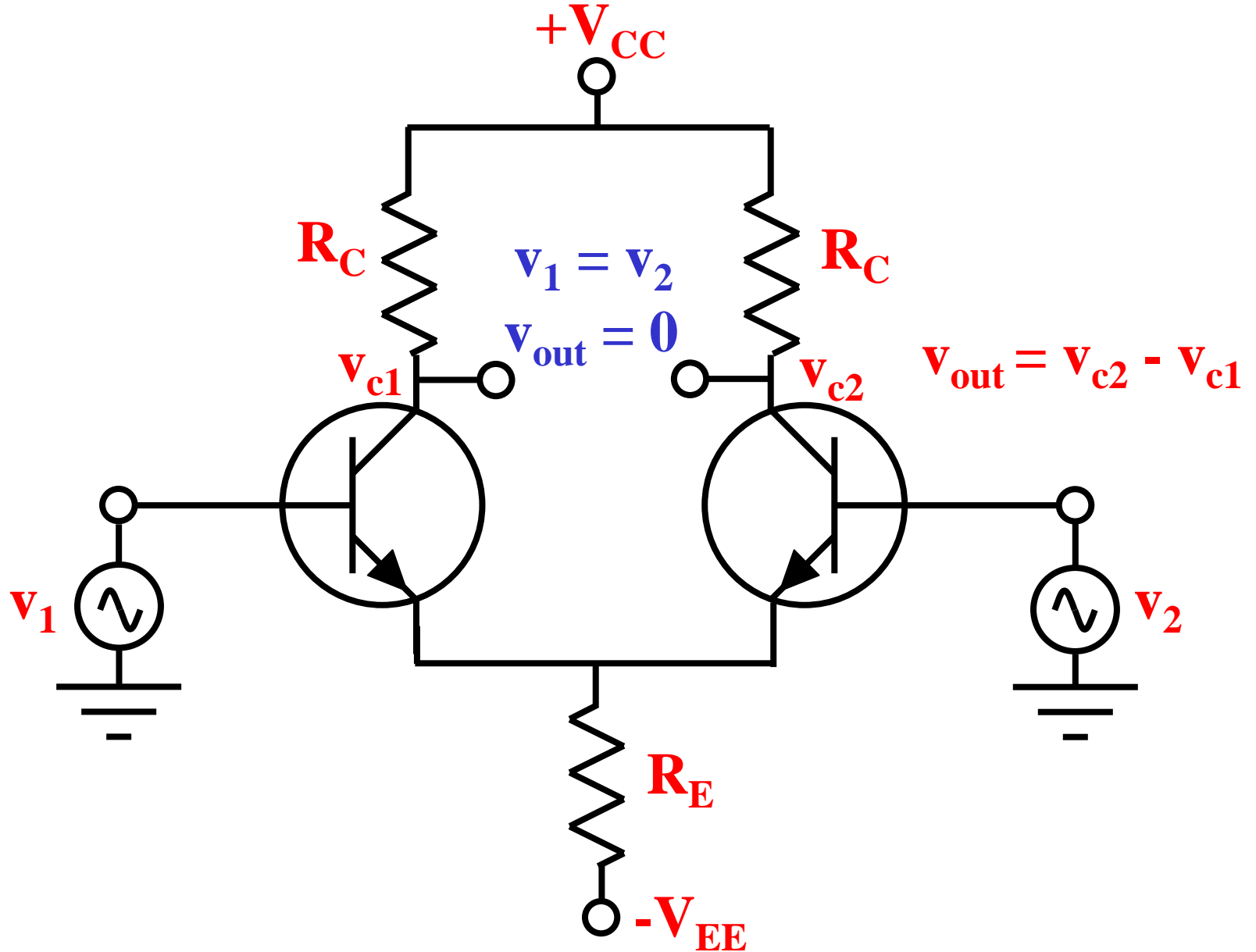


# A differential amplifier with single-ended output

## Block symbol

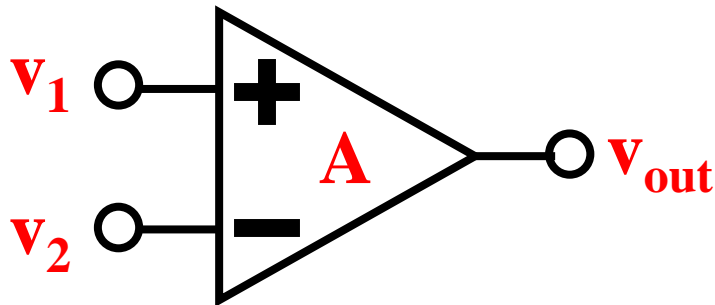


$$v_{out} = A(v_1 - v_2)$$

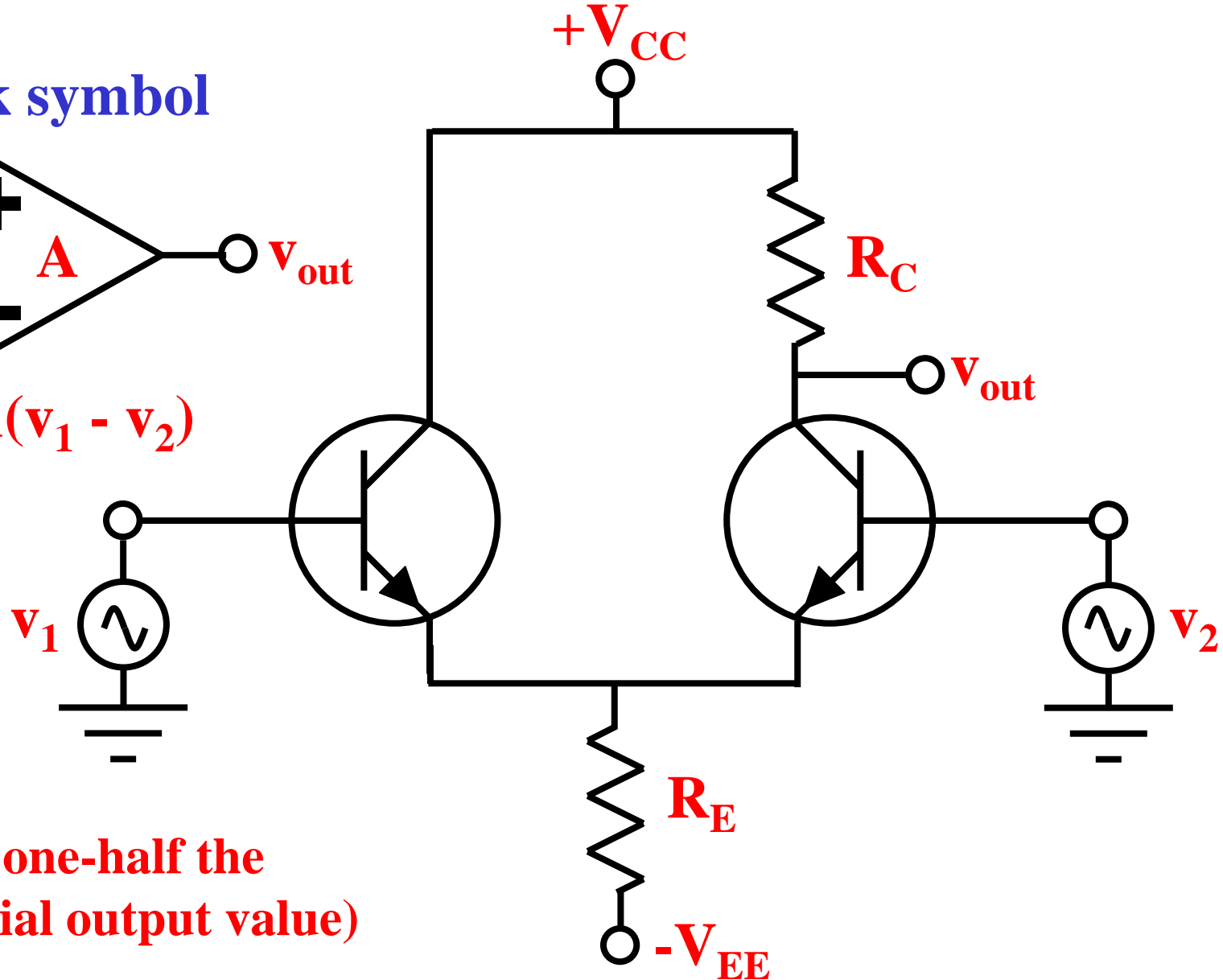
(A is one-half the differential output value)


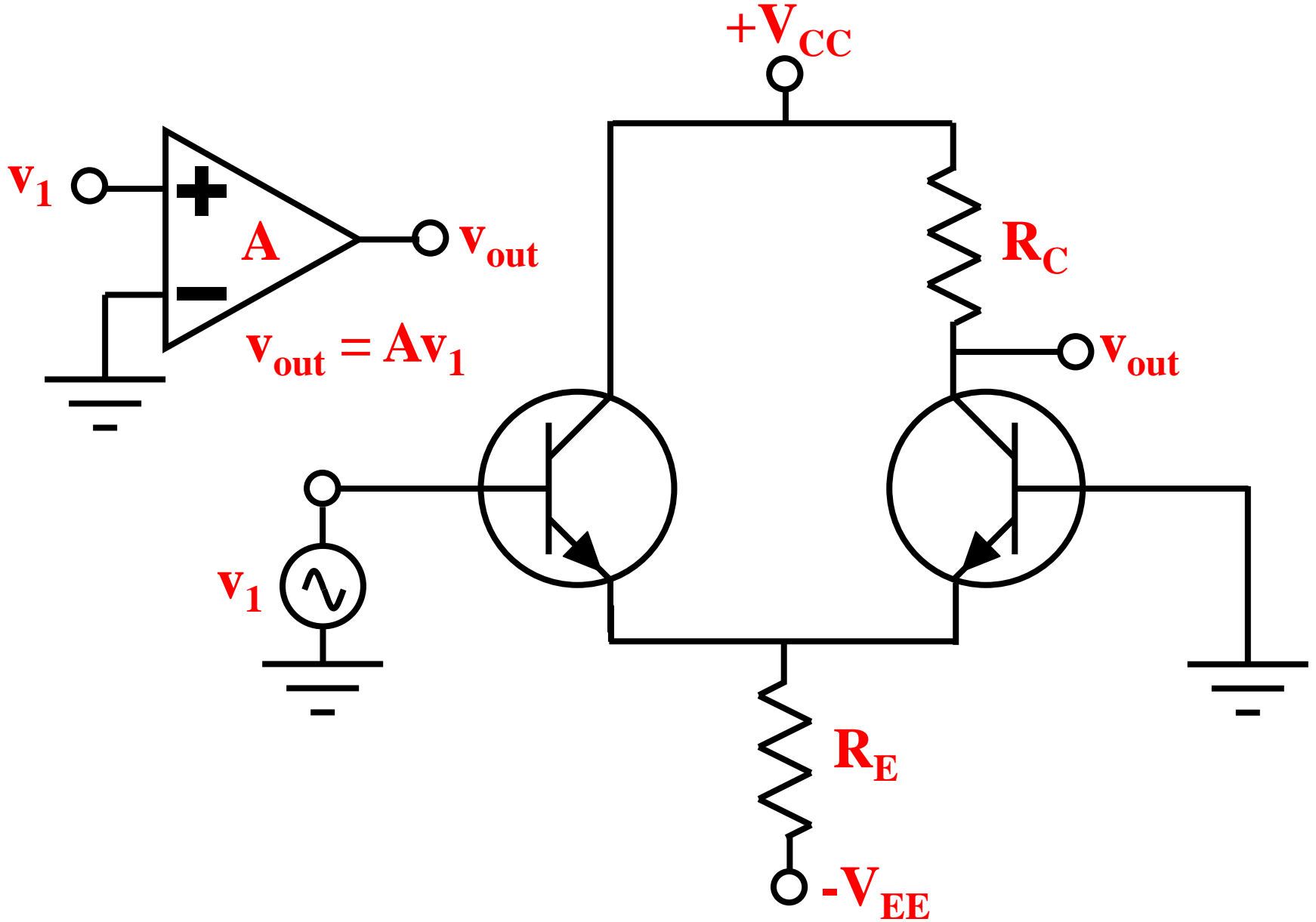
# Single-ended output and single-ended input.



# Inverting configuration

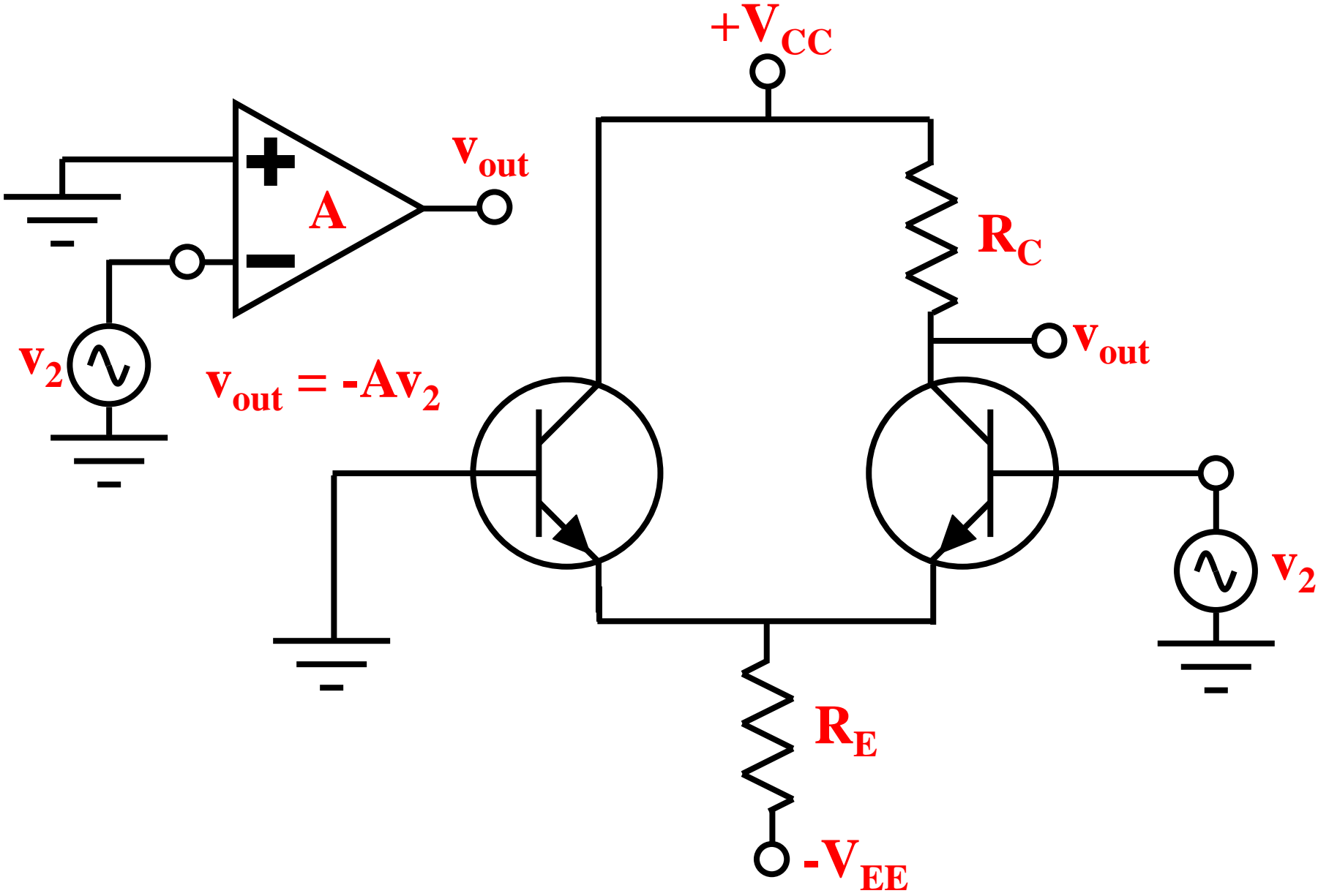


## dc analysis

$I_T$ , the *tail current*,  
flows in  $R_E$

$$I_T = \frac{V_{EE} - V_{BE}}{R_E}$$

$$I_E = \frac{I_T}{2}$$

$$V_C = V_{CC} - I_E R_C$$

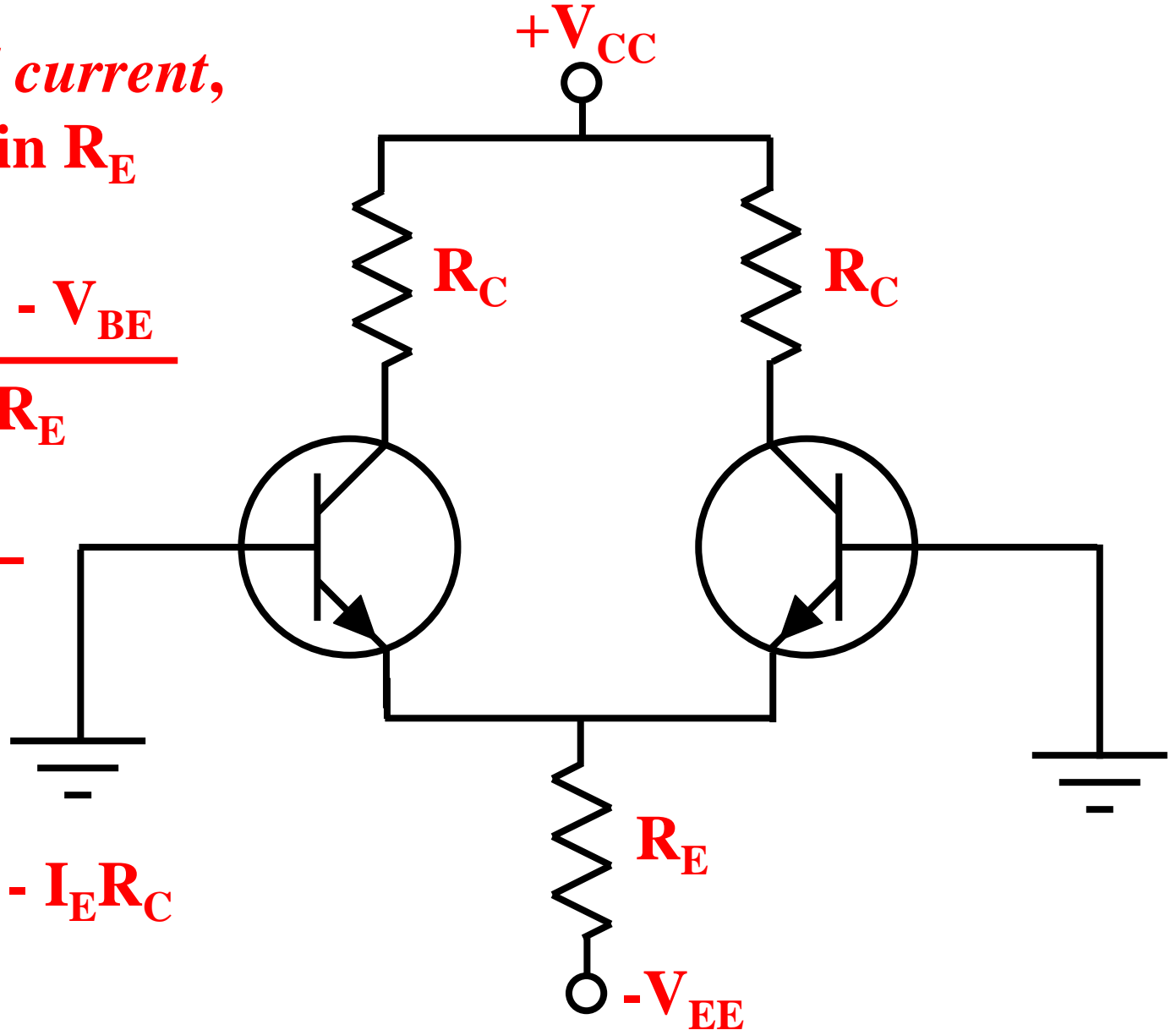


## ac analysis

$$A = \frac{R_C}{2r_e'}$$

Differential output case:  $A = \frac{R_C}{r_e'}$

$$z_{in} = 2\beta r_e'$$

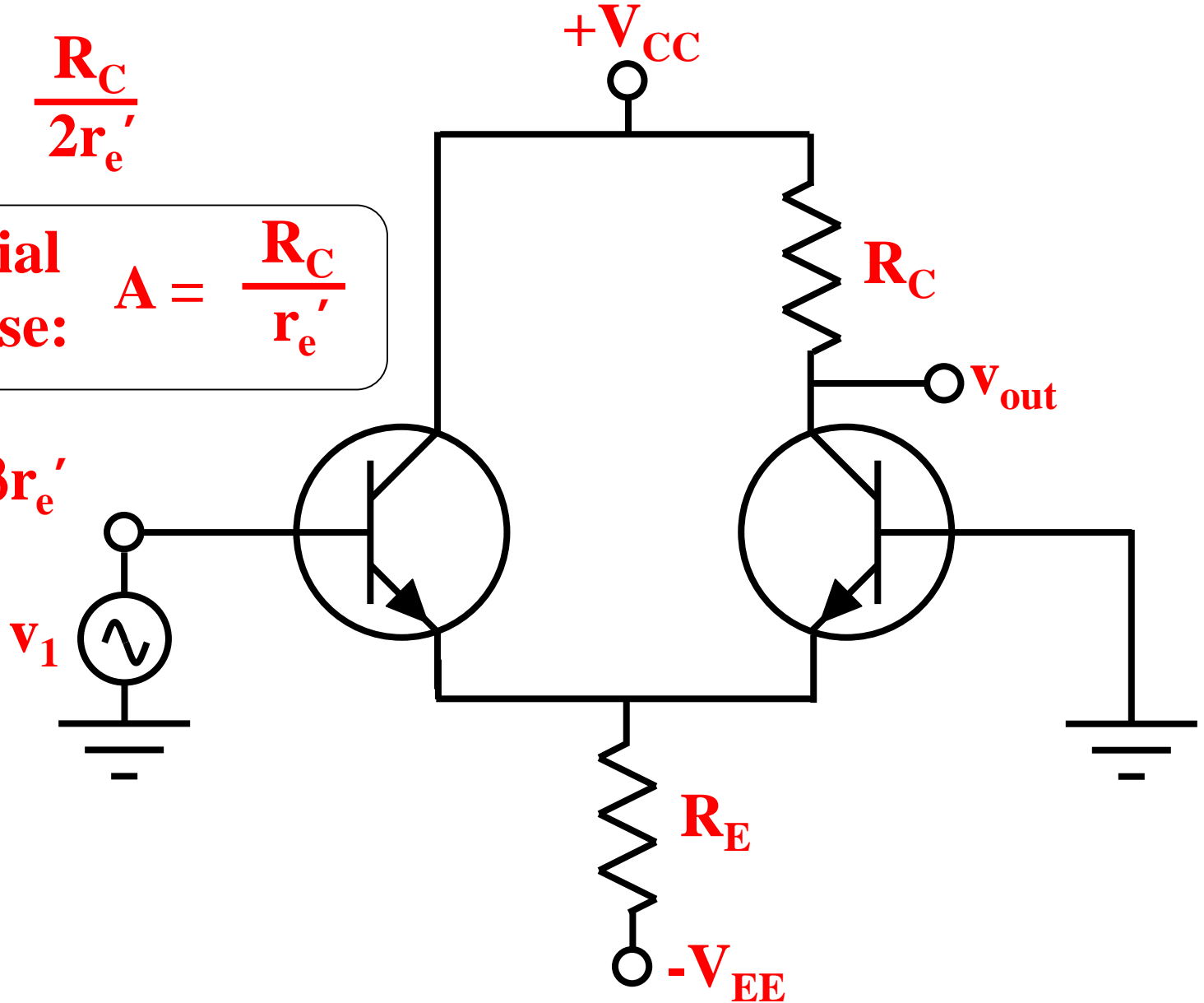


**The input transistors are not exactly the same.**

$$I_{B1} \neq I_{B2}$$

$$I_{\text{in(bias)}} = \frac{I_{B1} + I_{B2}}{2}$$

$$I_{\text{in(off)}} = I_{B1} - I_{B2}$$

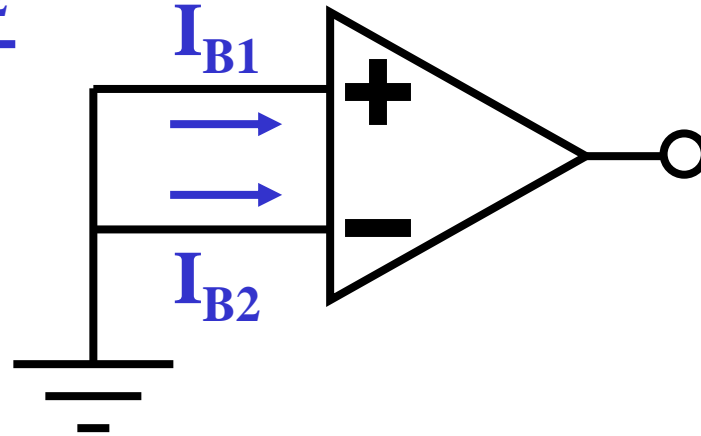


$$I_{B1} = I_{\text{in(bias)}} + \frac{I_{\text{in(off)}}}{2}$$

$$I_{B2} = I_{\text{in(bias)}} - \frac{I_{\text{in(off)}}}{2}$$




Base current can produce a false signal.

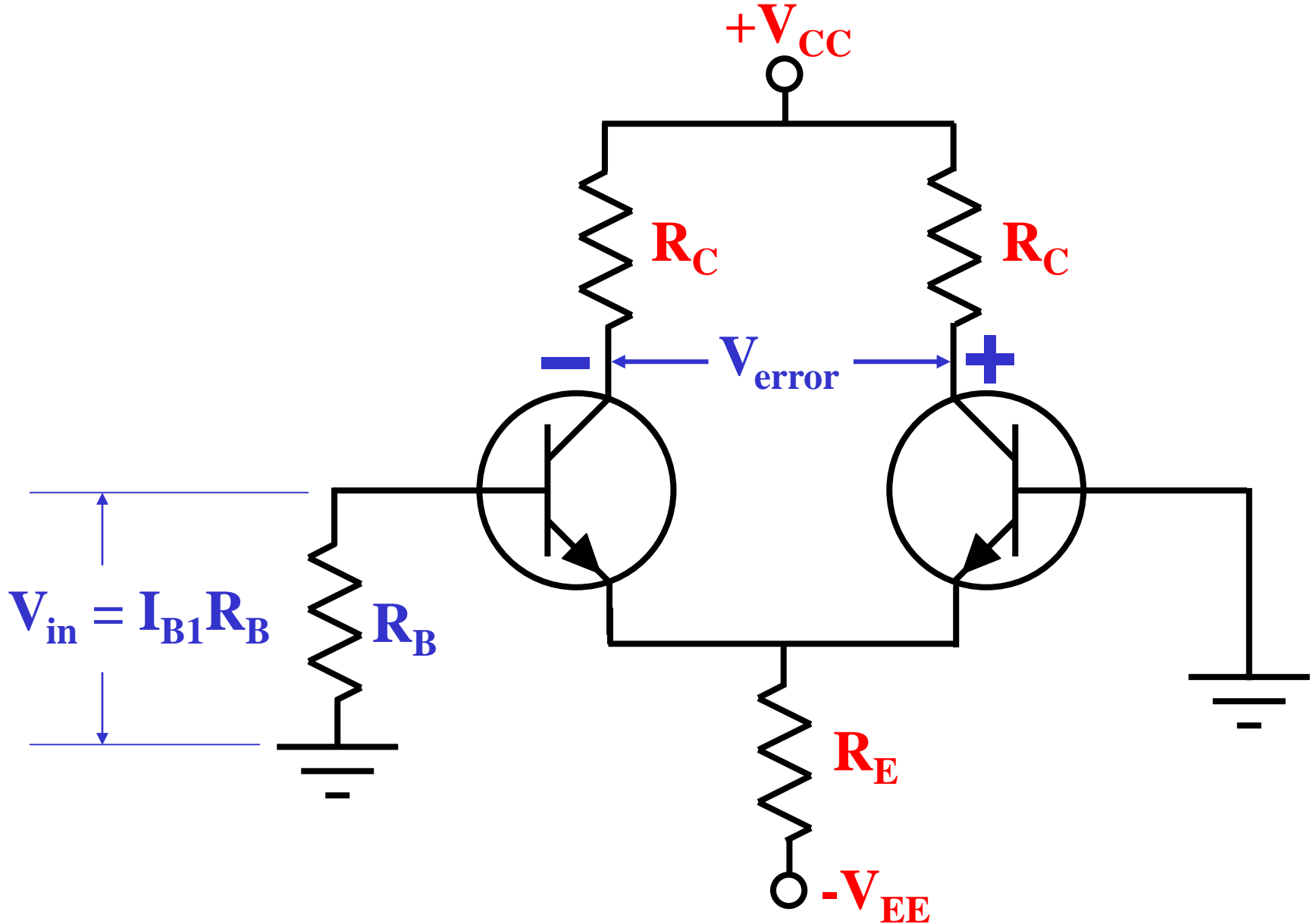

$V_{in}$  and  $V_{error}$  are minimized with equal base resistors.

$$I_{in(off)} < I_{in(bias)}$$

$$V_{in} = I_{in(off)} R_B$$

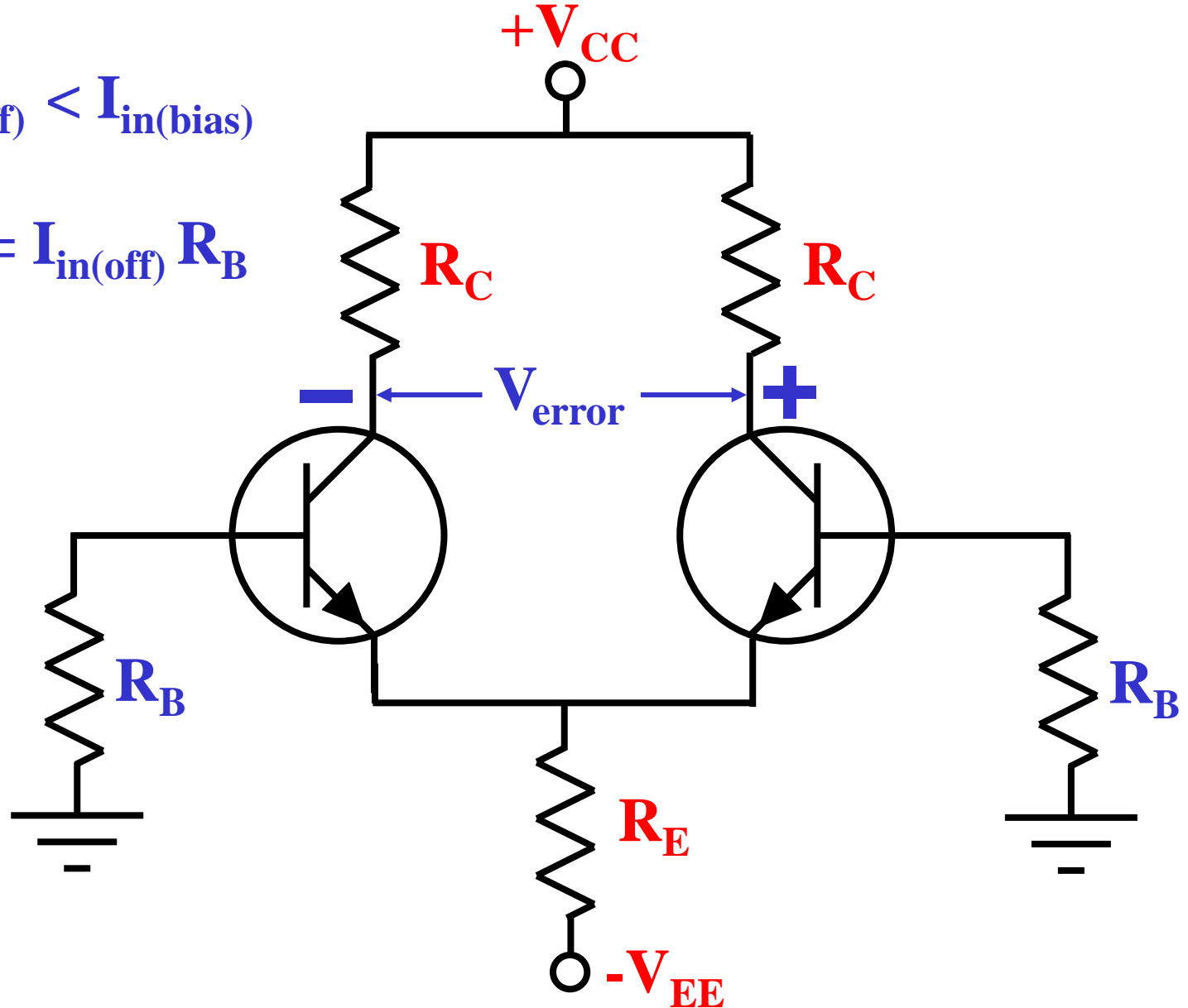

# Input offset voltage


- The  $R_C$  values may be different.
- $V_{BE}$  for each transistor may be different.
- Other parameters may differ slightly on each side of the diff amp.
- The input offset voltage would produce the same error in an ideal amplifier.
- $V_{in(off)} = V_{error}/A$
- Both bases are *grounded* when  $V_{error}$  is measured.

# Combined dc error

- $V_{1\text{err}} = (R_{B1} - R_{B2})I_{\text{in(bias)}}$
- $V_{2\text{err}} = (R_{B1} + R_{B2})I_{\text{in(off)}/2}$
- $V_{3\text{err}} = V_{\text{in(off)}}$
- $V_{\text{error}} = A(V_{1\text{err}} + V_{2\text{err}} + V_{3\text{err}})$
- $V_{1\text{err}}$  eliminated with equal base resistors
- $V_{2\text{err}}$  reduced with smaller base resistors
- $V_{3\text{err}}$  reduced with premium op amps

# Common-mode gain

$$A_{CM} = \frac{R_C}{2R_E}$$

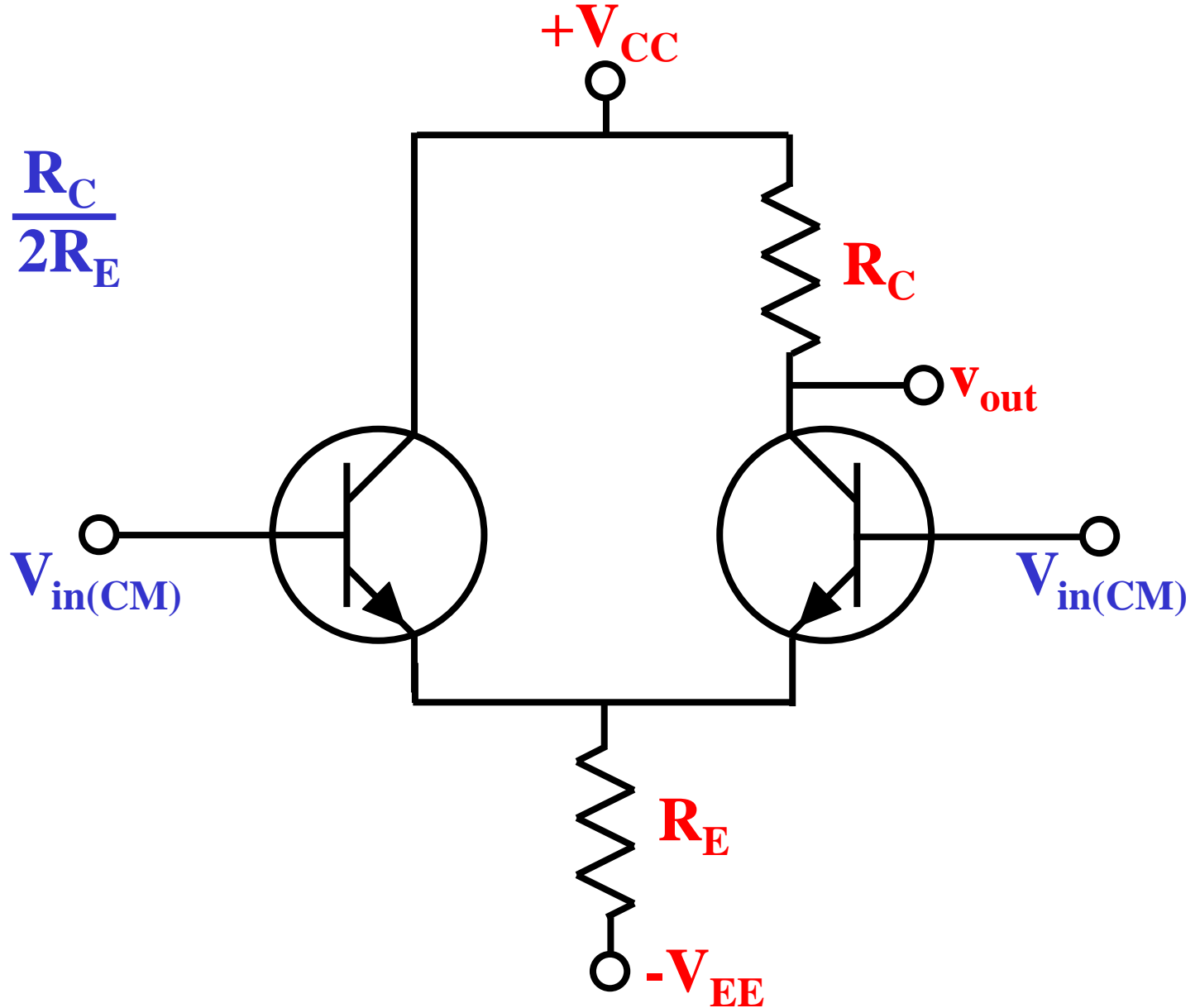

# Common-mode rejection ratio


- $\text{CMRR} = A/A_{\text{CM}}$
- $\text{CMRR}_{\text{dB}} = 20\log \text{CMRR}$
- The higher the CMRR, the better
- A typical op amp has  $\text{CMRR}_{\text{dB}} = 90 \text{ dB}$
- Much interference is common-mode and a high CMRR means an amplifier will be effective in rejecting interference

# The current mirror


$$I_R = \frac{V_{CC} - V_{BE}}{R}$$

$$I_C = I_R$$

**Compensating diode**

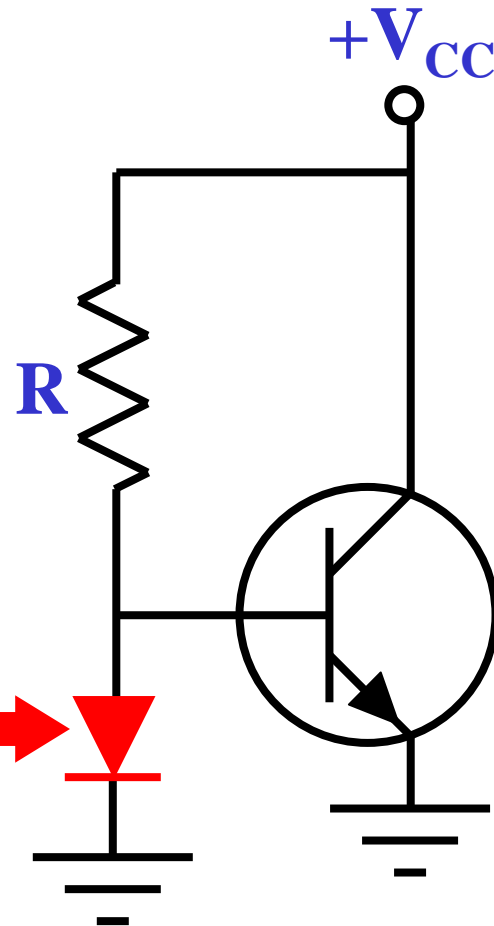

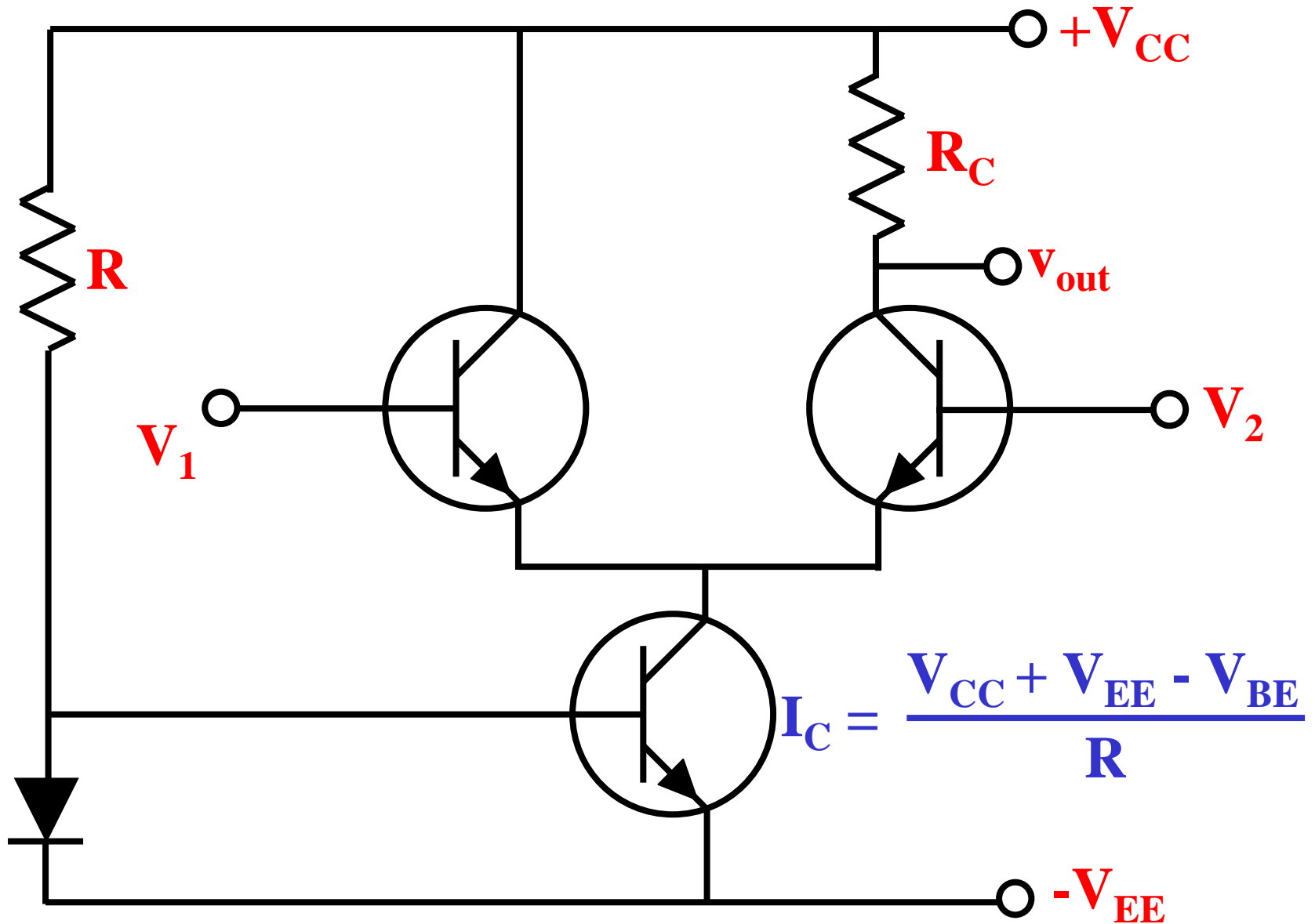
# In ICs, a current mirror sources the tail current






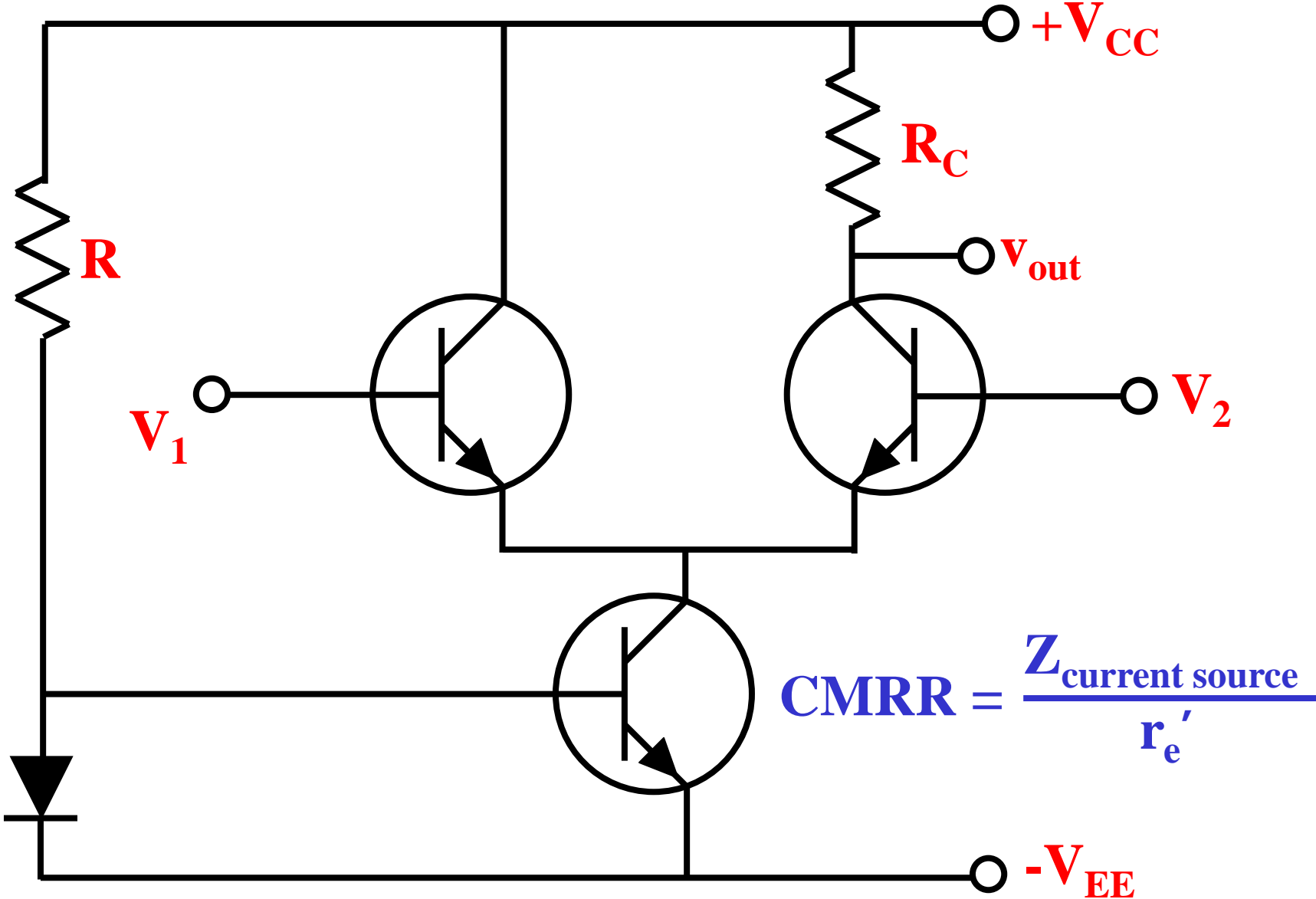
The impedance of a current source is very high.



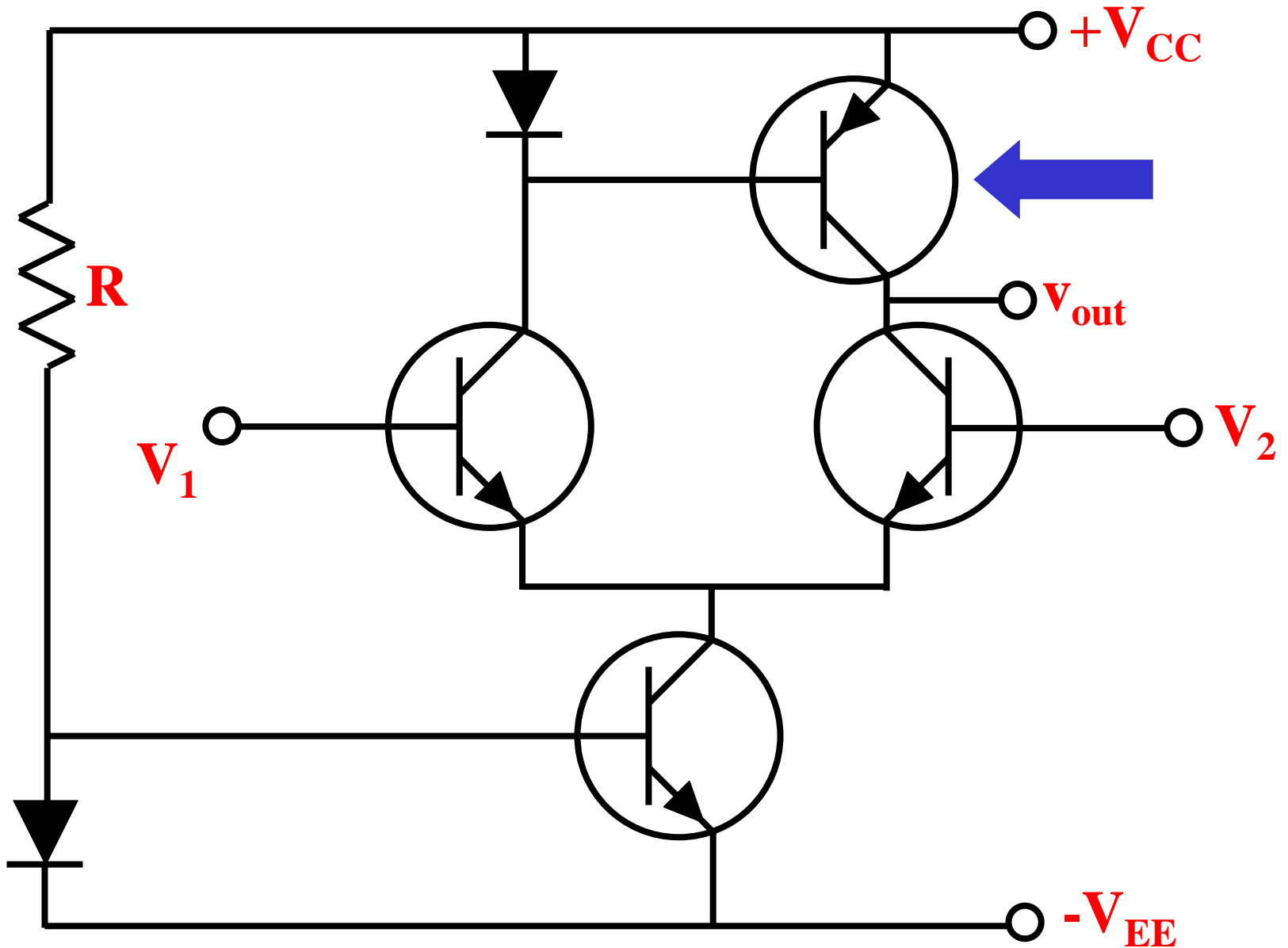
*Active loading* produces a very high voltage gain.



# Loaded diff amps

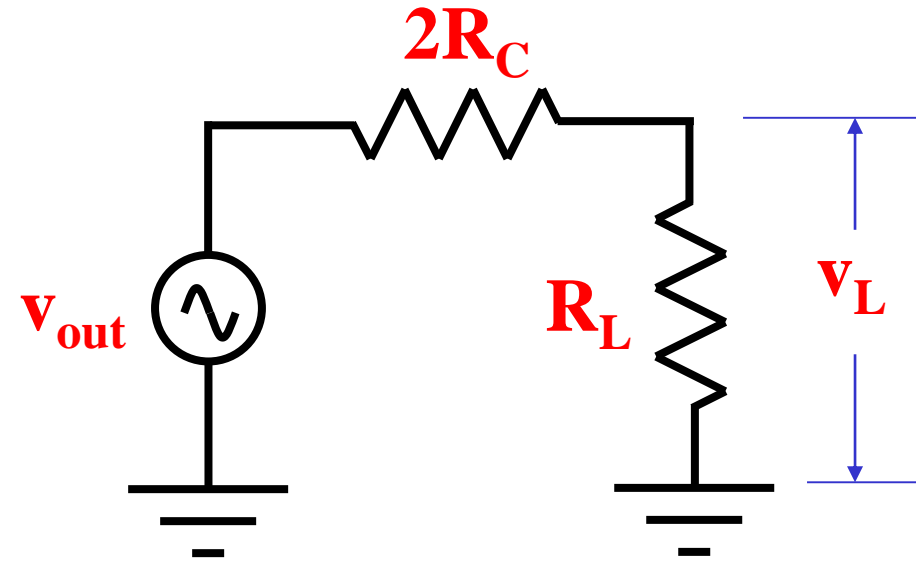

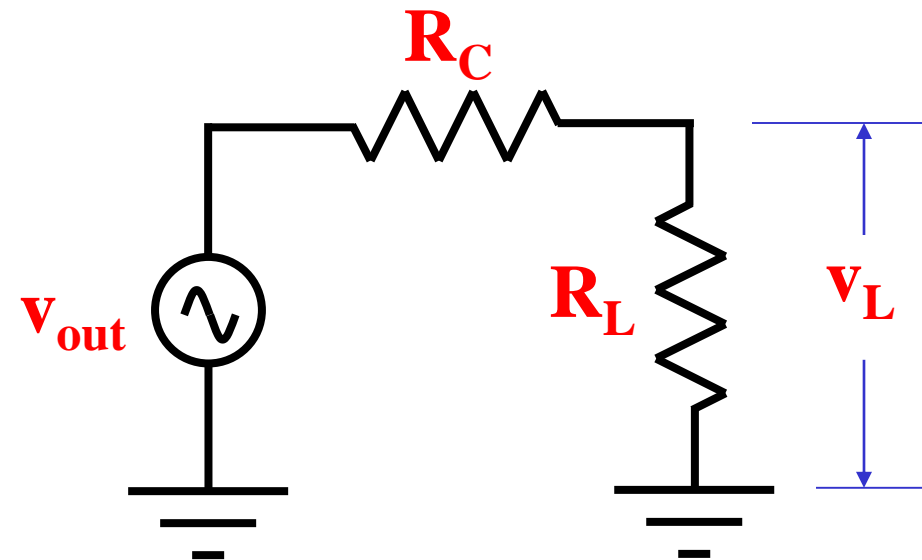Thevenin equivalent circuit  
for differential output



Thevenin equivalent circuit  
for single-ended output