


Respons Frekuensi

Elektronika

(TKE 4012)

Eka Maulana

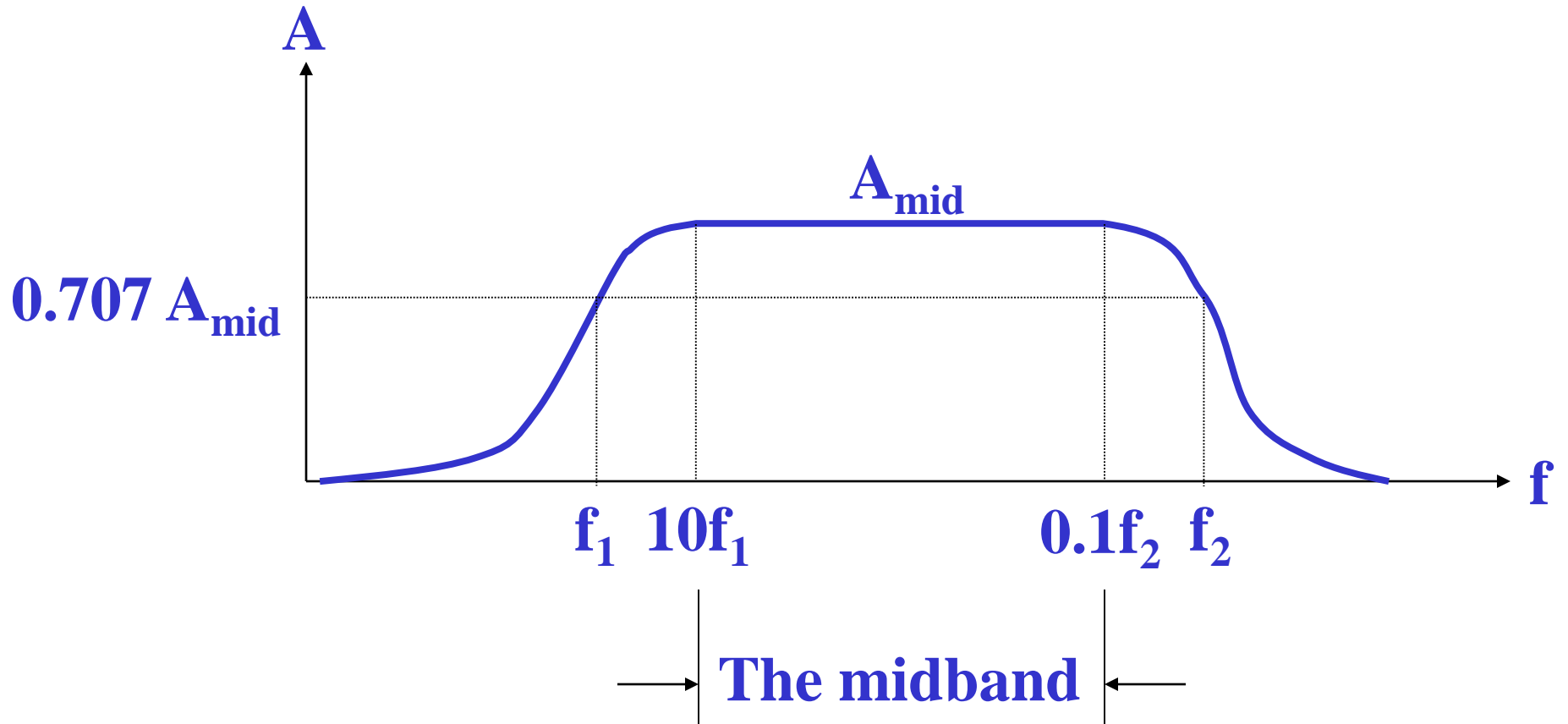The frequency response curve of an ac amplifier



The gain is maximum in the midband.

Review of logarithms

- A logarithm is an exponent
- If $x = 10^y$, then $y = \log_{10}x$
- $y = \log 10 = 1$
- $y = \log 100 = 2$
- $y = \log 1000 = 3$
- $y = \log 0.1 = -1$
- $y = \log 0.01 = -2$
- $y = \log 0.001 = -3$

Definition of G_{dB}


- $G = p_{\text{out}}/p_{\text{in}}$
- $G_{\text{dB}} = 10 \log G$
- **Memorize:**
 - if $G = 2$, $G_{\text{dB}} = +3$
 - if $G = 0.5$, $G_{\text{dB}} = -3$
 - if $G = 10$, $G_{\text{dB}} = +10$
 - if $G = 0.1$, $G_{\text{dB}} = -10$

Definition of A_{dB}


- $A = v_{\text{out}}/v_{\text{in}}$
- $A_{\text{dB}} = 20 \log A$
- **Memorize:**
 - > if $A = 2$, $A_{\text{dB}} = +6$
 - > if $A = 0.5$, $A_{\text{dB}} = -6$
 - > if $A = 10$, $A_{\text{dB}} = +20$
 - > if $A = 0.1$, $A_{\text{dB}} = -20$
- **Cascade:** $A = A_1 A_2$, $A_{\text{dB}} = A_{1\text{dB}} + A_{2\text{dB}}$

More on the decibel

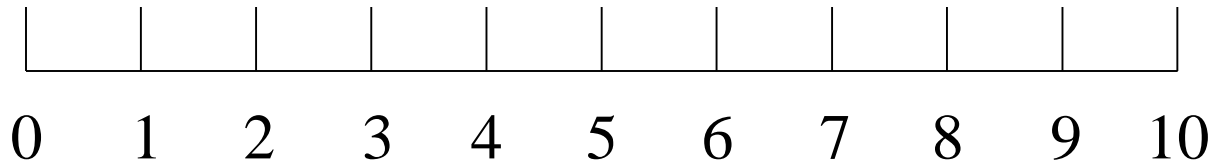- $G_{\text{dB}} = A_{\text{dB}}$ only if *impedance matched*
- $G = \text{antilog } G_{\text{dB}}/10$
- $A = \text{antilog } A_{\text{dB}}/20$
- $P_{\text{dBm}} = 10 \log P/1 \text{ mW}$
- $P = \text{antilog } P_{\text{dBm}}/10$
- $V_{\text{dBV}} = 20 \log V$
- $V = \text{antilog } V_{\text{dBV}}/20$



Linear scale

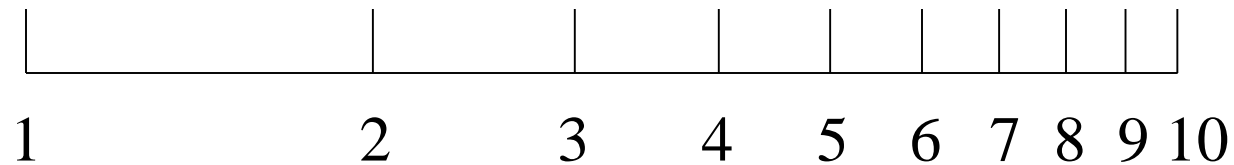


Logarithmic scale

A logarithmic scale compresses large values and allows a large range to be covered without losing resolution for the smaller values.

Bode plots

- Use semilogarithmic graph paper (the horizontal axis is logarithmic; the vertical is linear)
- Plot dB voltage gain on the vertical axis
- Plot frequency on the horizontal axis
- An octave refers to a ratio of 2
- A decade refers to a ratio of 10



Ideal Bode plot of an ac amplifier

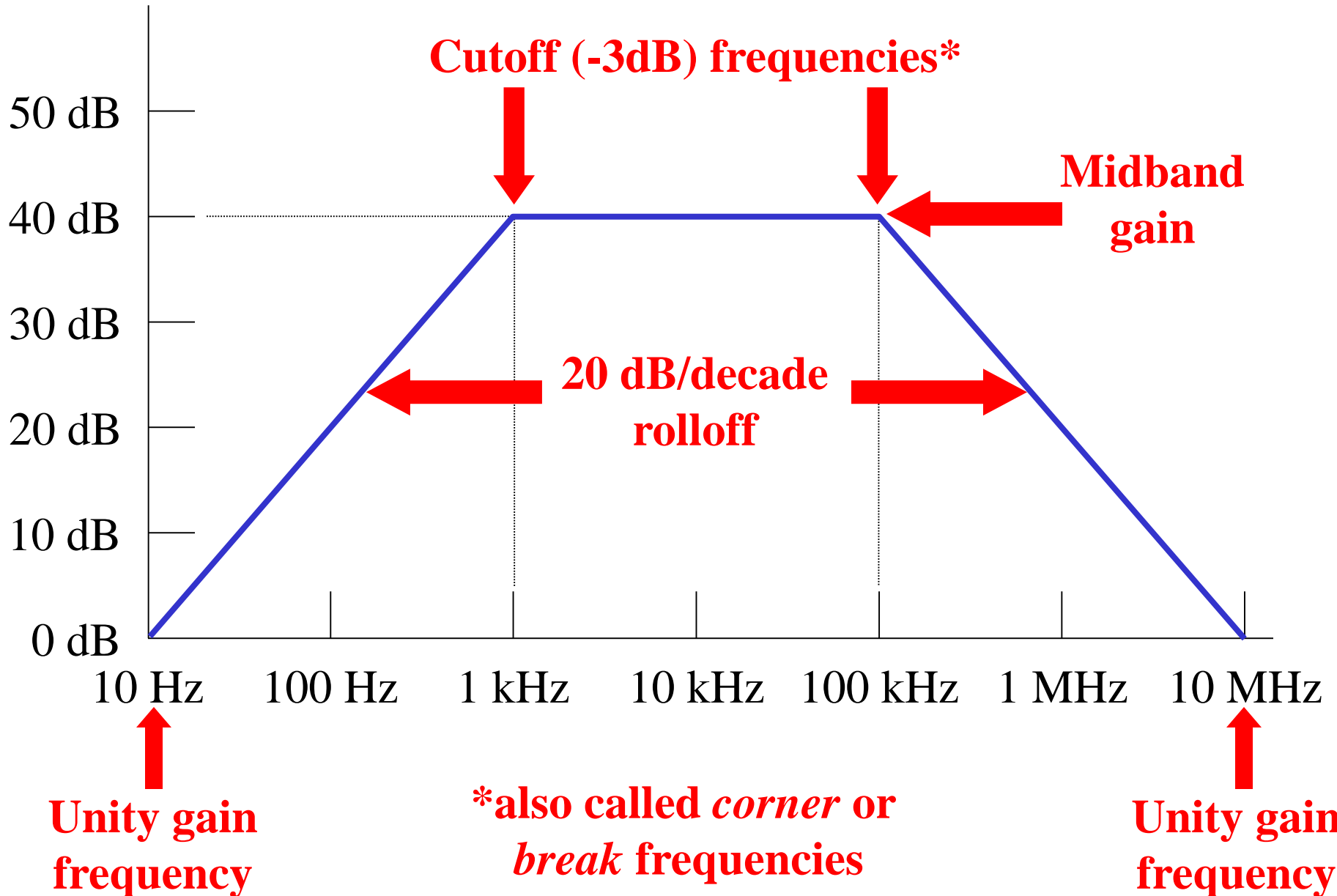

Amplitude response of RC lag circuit



$$f_2 = \frac{1}{2\pi RC}$$
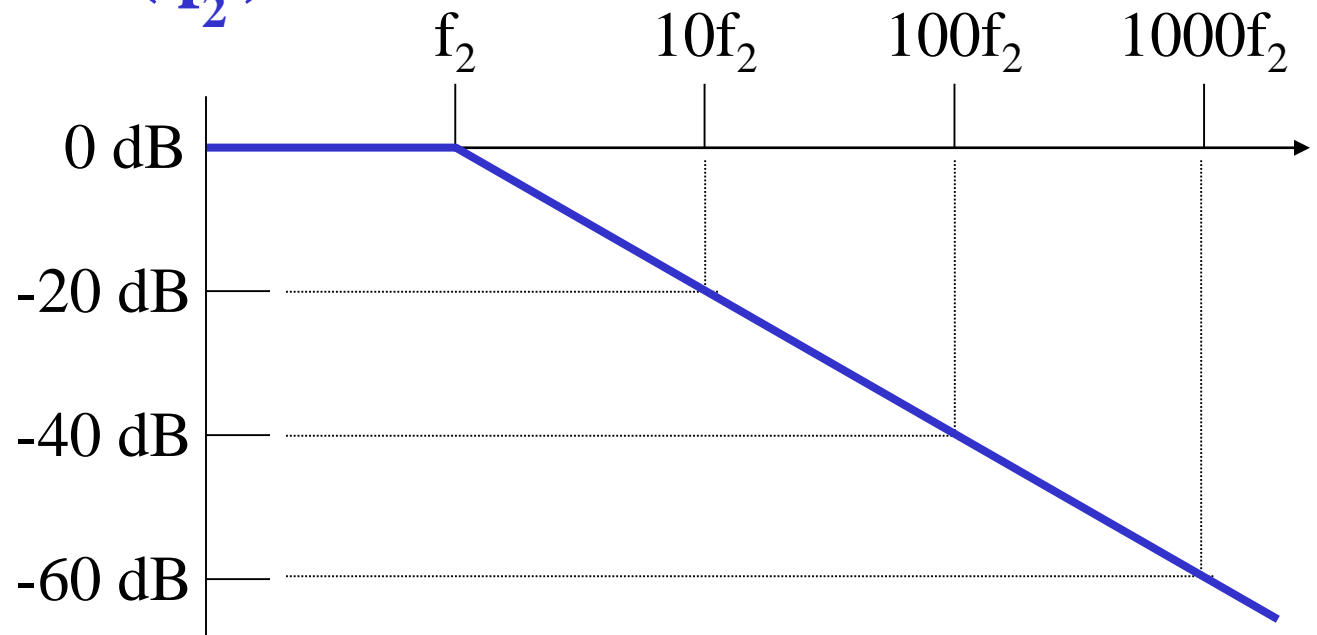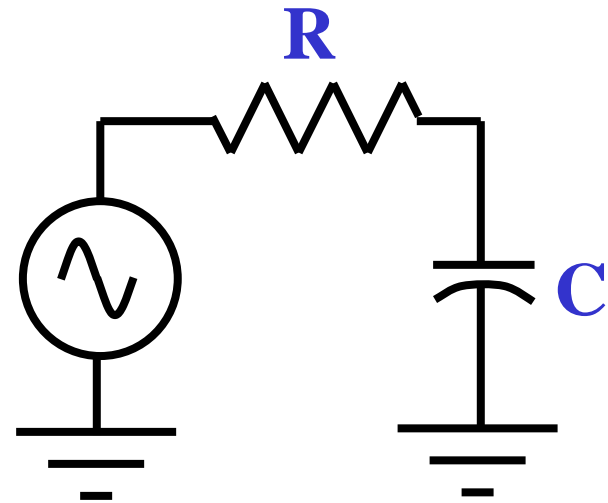
$$A = \frac{1}{\sqrt{1 + \left(\frac{f}{f_2}\right)^2}}$$





Angular response of RC lag circuit

$$\phi = -\arctan \frac{f}{f_2}$$

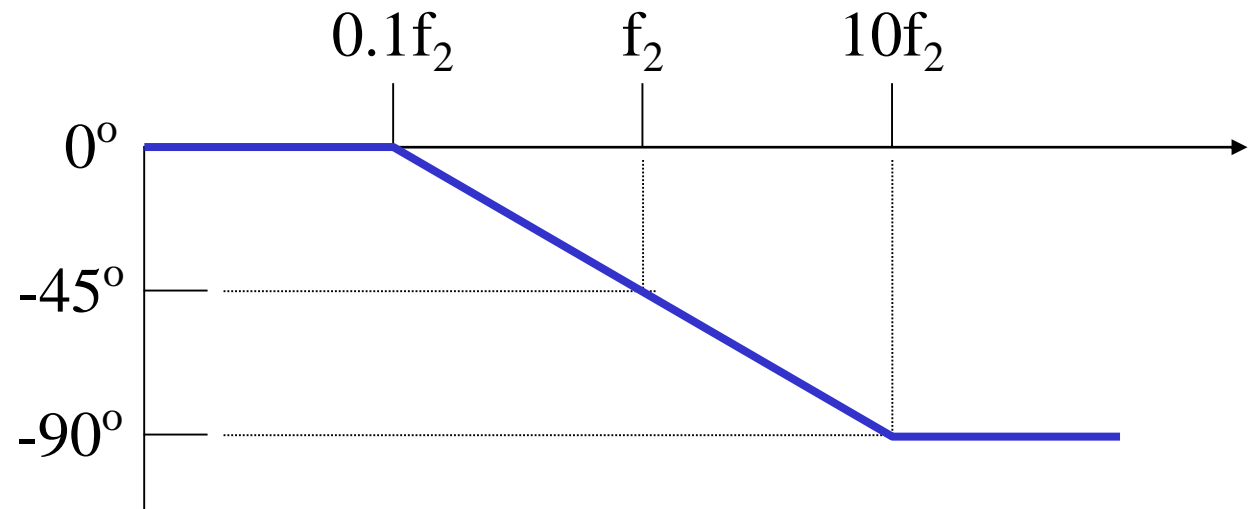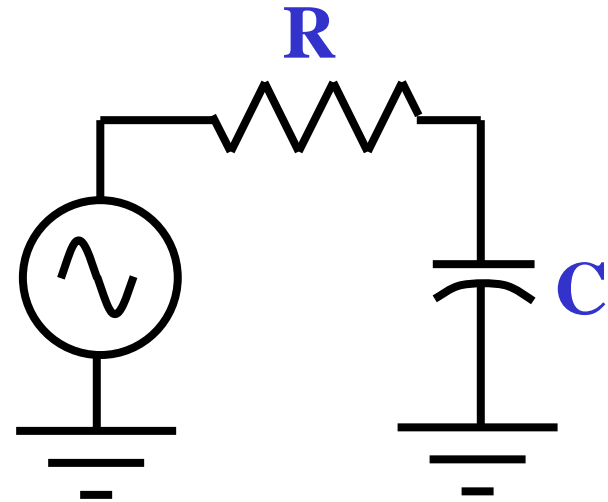

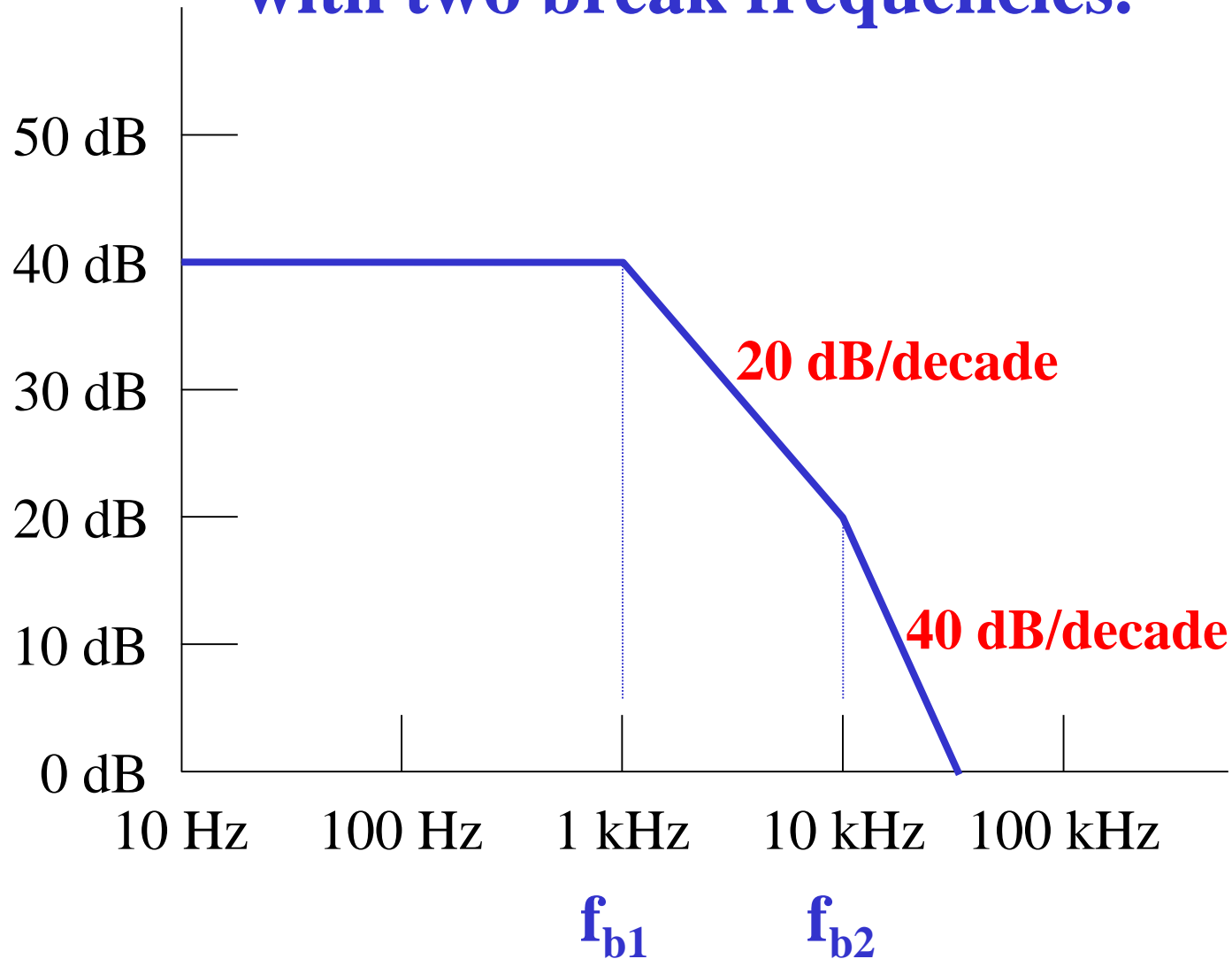Ideal Bode plot of a dc amplifier with two break frequencies.



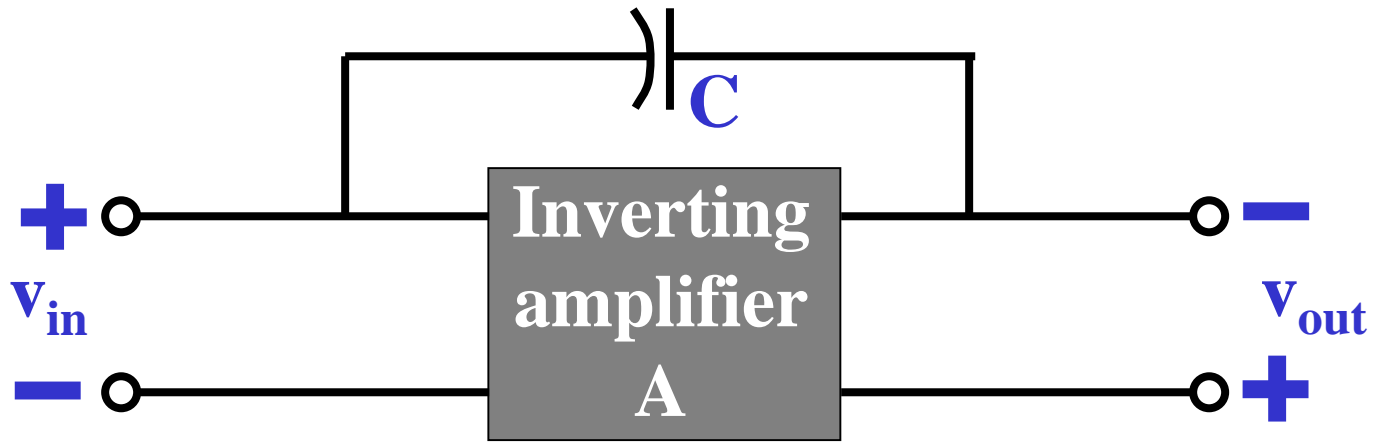

Inverting amplifier with feedback capacitor



Miller equivalent circuit


$$C_{in} = C(A+1)$$

$$C_{out} = C \frac{A+1}{A}$$

Frequency compensation


- **Most op amps are internally compensated to prevent oscillations**
- **One dominant internal compensation capacitor rolls off the gain at 20 dB/decade**
- **IC capacitors are limited to the pF range**
- **The Miller effect makes the internal compensation capacitor equivalent to a much larger capacitor**

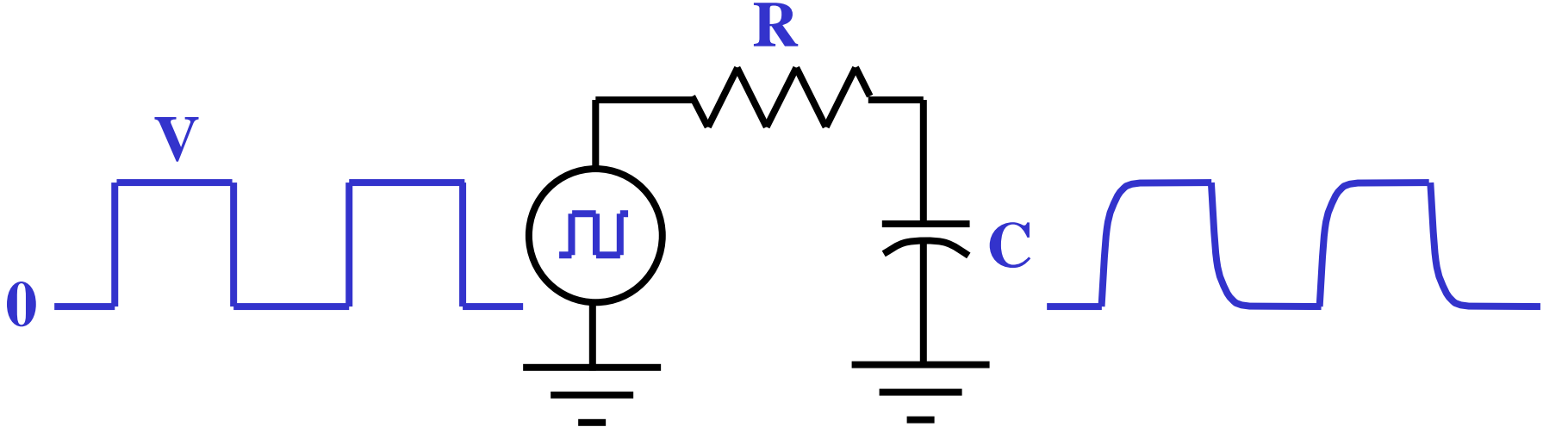Square-wave response of a circuit with limited bandwidth



$$T_R = 2.2RC$$


$$f_{\text{cutoff}} = \frac{0.35}{T_R}$$

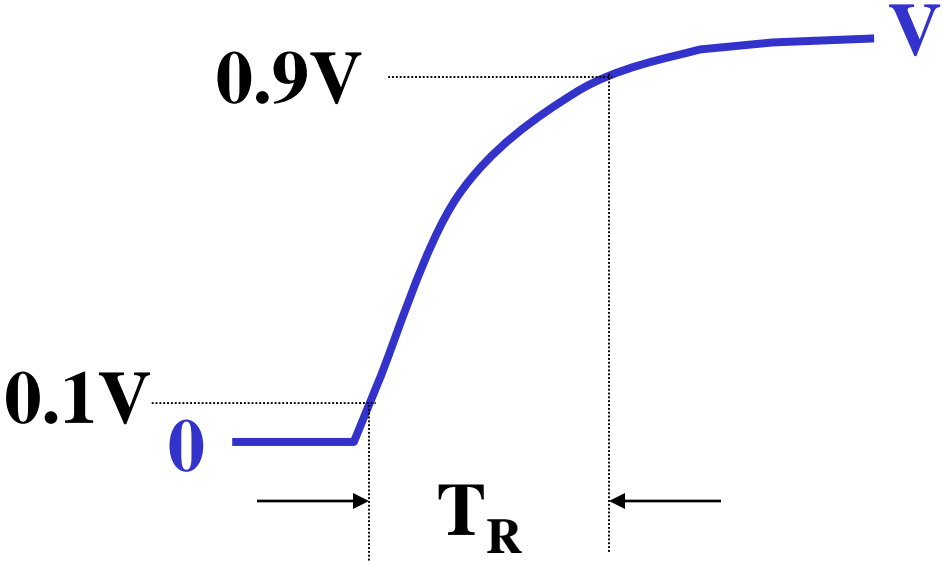

Cutoff frequency of input coupling capacitor


$$Z_{\text{in(stage)}} = R_1 \parallel R_2 \parallel \beta r_e'$$
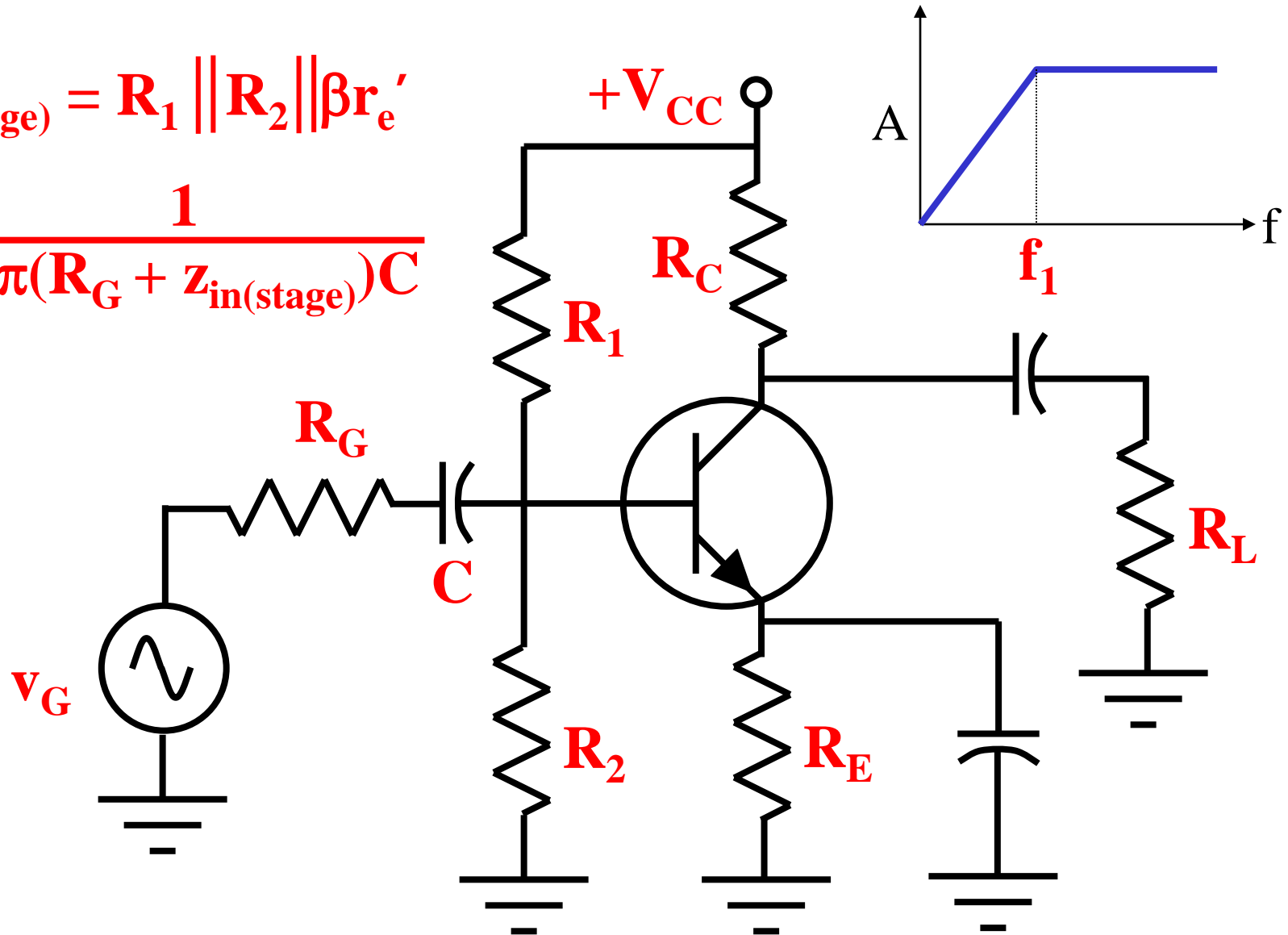
$$f_1 = \frac{1}{2\pi(R_G + Z_{\text{in(stage)})C}$$



Cutoff frequency of output coupling capacitor


$$f_1 = \frac{1}{2\pi(R_C + R_L)C}$$

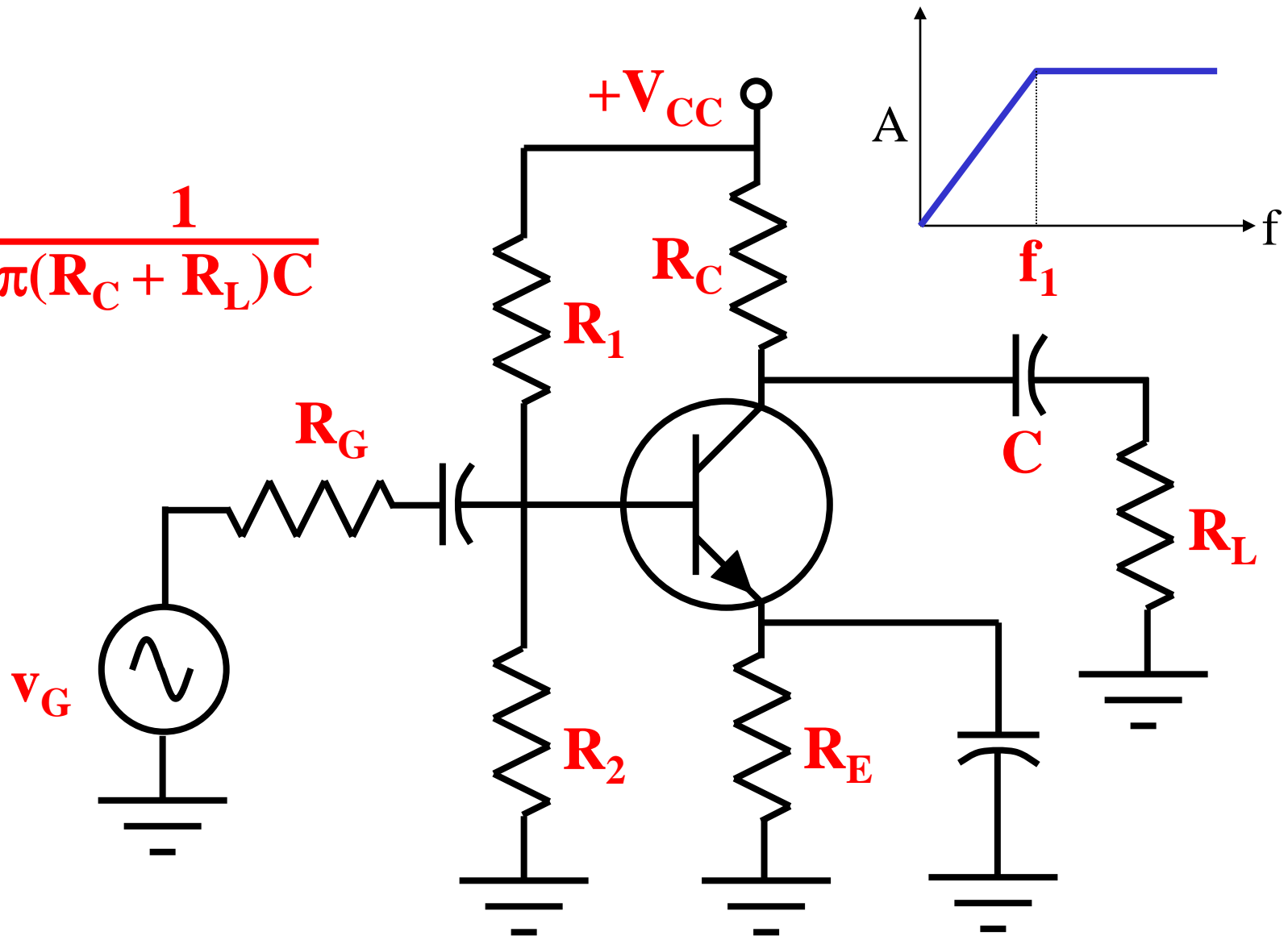

Cutoff frequency of emitter bypass capacitor

$$Z_{\text{out}} = R_E \parallel \left(r_e' + \frac{R_1 \parallel R_2 \parallel R_G}{\beta} \right)$$

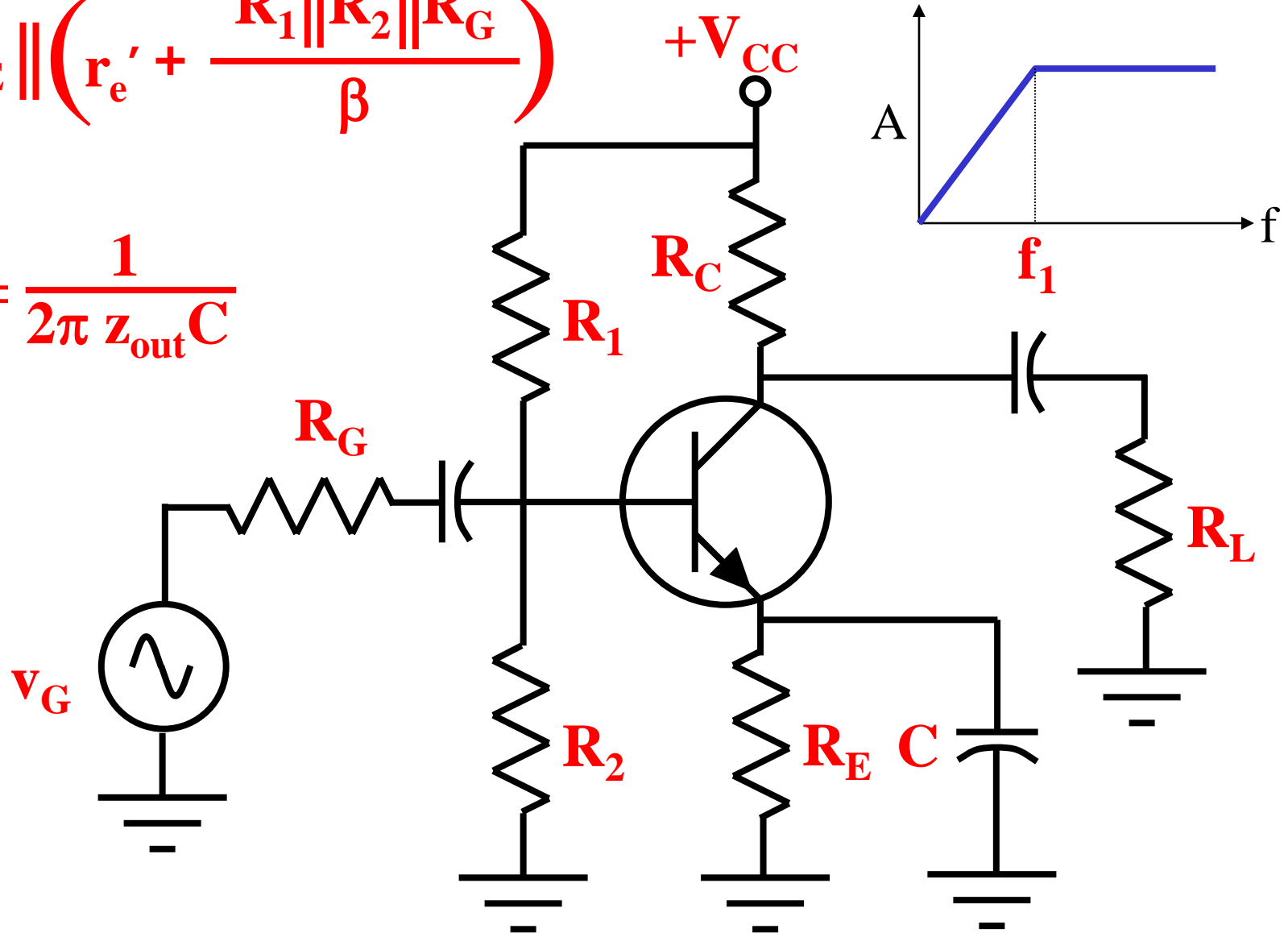
$$f_1 = \frac{1}{2\pi Z_{\text{out}} C}$$



Combined frequency effects

- The input coupling, output coupling, and emitter bypass capacitors each produce a cutoff frequency.
- One is usually dominant (the highest frequency) and produces a rolloff of 20 dB/decade as frequency *decreases*.
- When the next cutoff is reached, the gain rolloff increases to 40 dB/decade.
- When the third is reached, it becomes 60 dB/decade.

Base and collector bypass circuits

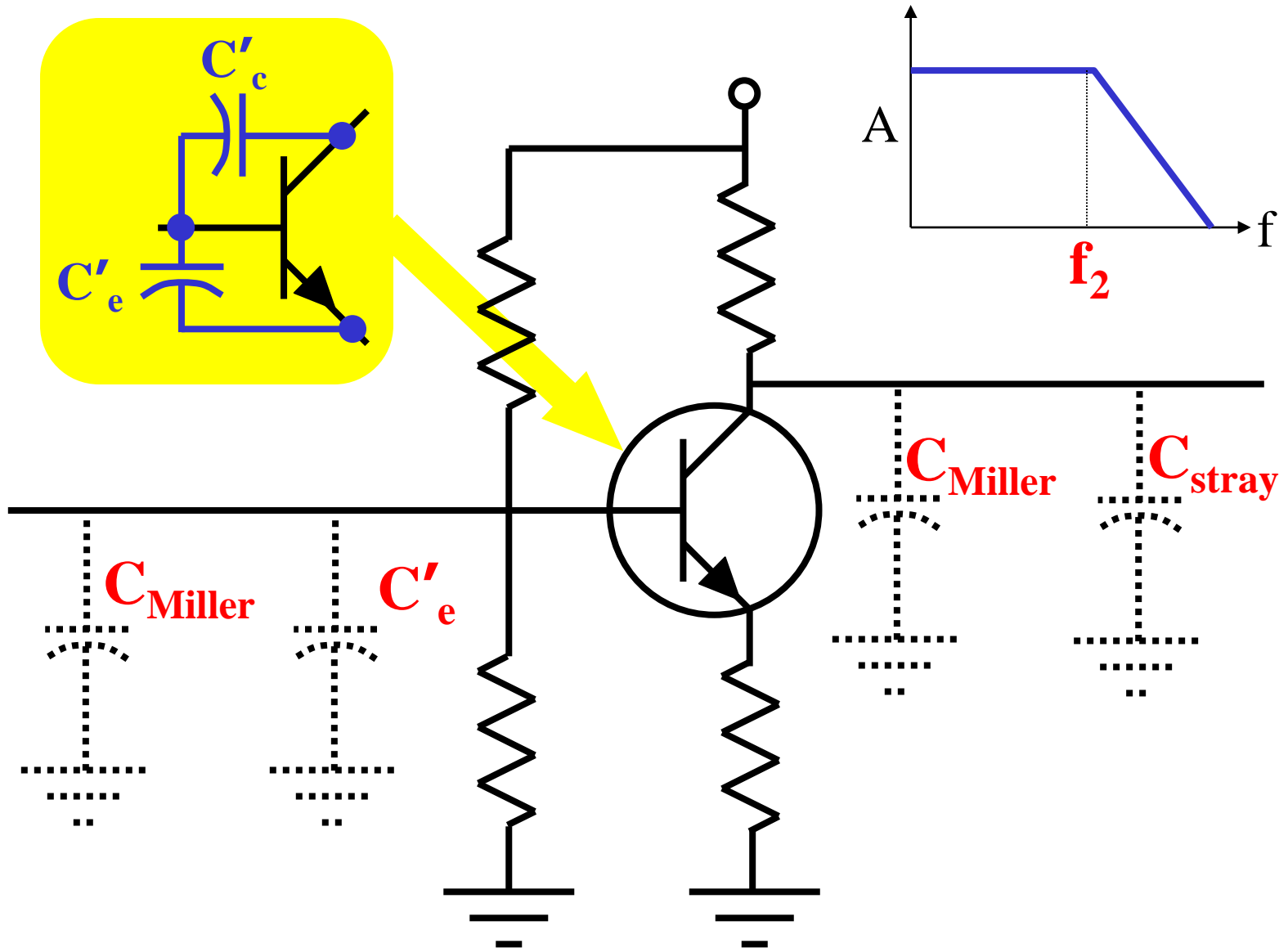

Bypass circuits

- **The base bypass circuit contains the internal base-emitter capacitance (C'_e) and the Miller capacitance due to the internal collector-base feedback capacitance (C'_c)**
- **The collector bypass circuit contains the Miller capacitance and the stray (wiring) capacitance.**