


Filter Aktif

# Elektronika





(TKE 4012)

Eka Maulana

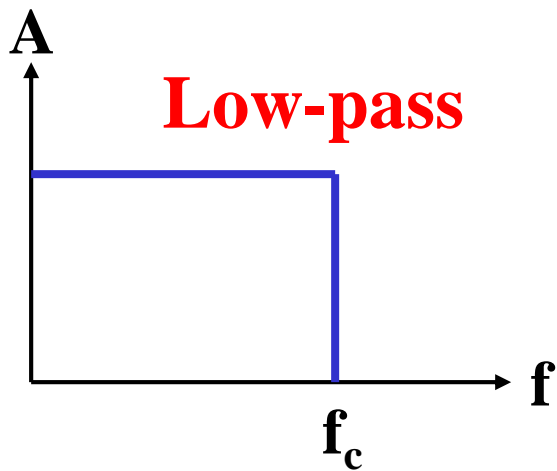[maulana.lecture.ub.ac.id](mailto:maulana.lecture.ub.ac.id)



**Ideal  
filter  
responses**

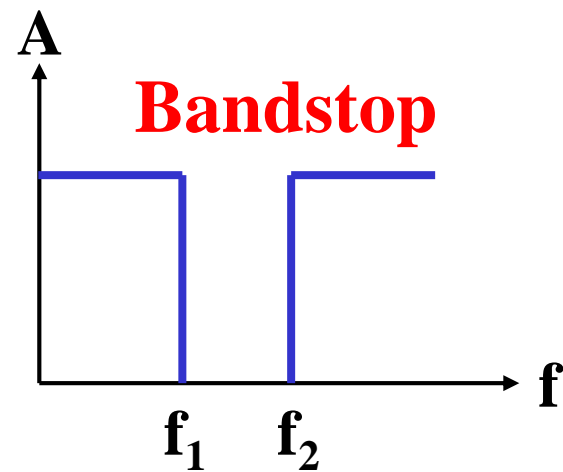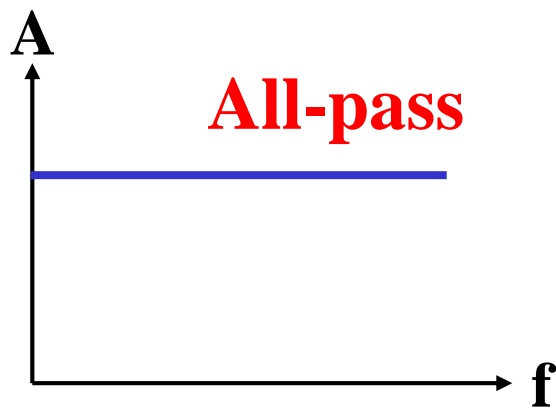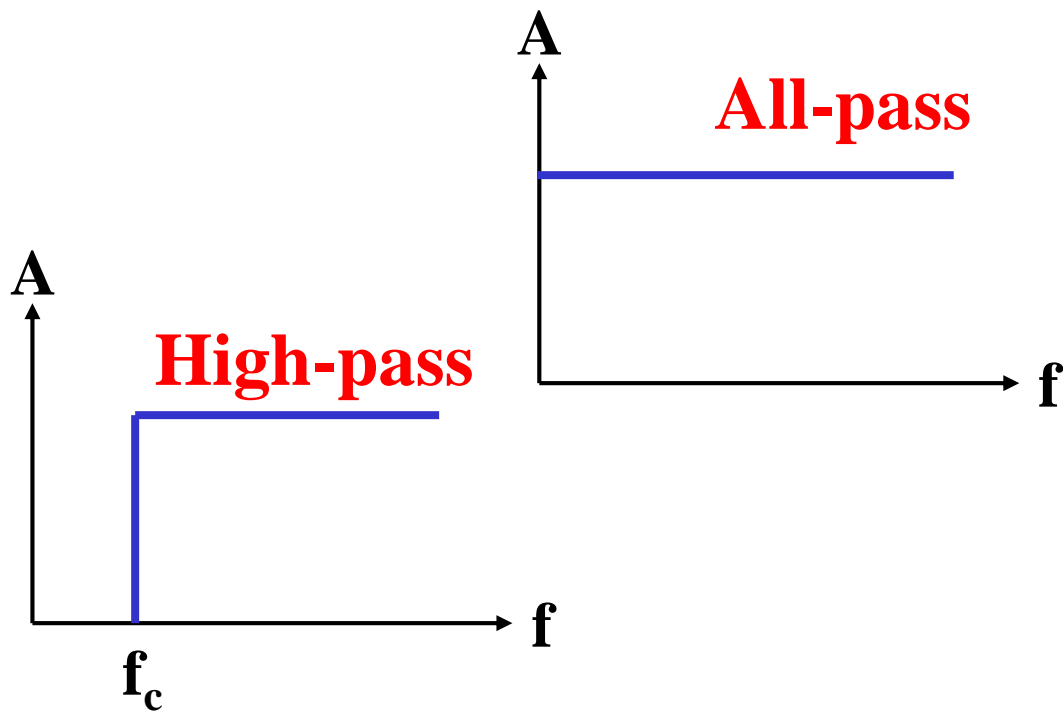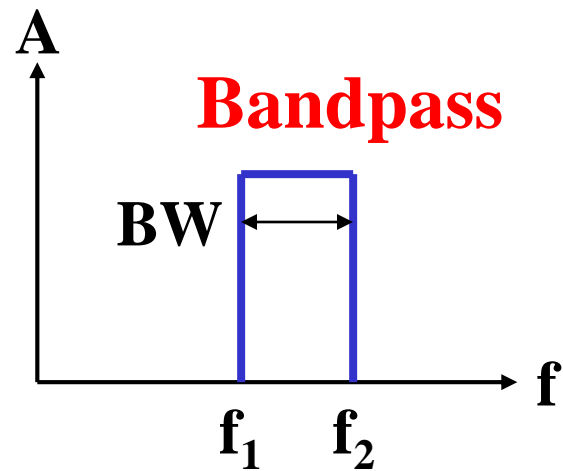

# Real filter response


- Ideal (*brickwall*) filters do not exist.
- Real filters have an approximate response.
- The attenuation of an ideal filter is  $\infty$  in the stopband.
- Real filter attenuation is  $v_{\text{out}}/v_{\text{out}(\text{mid})}$ :
  - 3 dB = 0.5
  - 12 dB = 0.25
  - 20 dB = 0.1

# The order of a filter





- In an LC type, the order is equal to the number of inductors and capacitors in the filter.
- In an RC type, the order is equal to the number of capacitors in the filter.
- In an active type, the order is approximately equal to the number of capacitors in the filter.
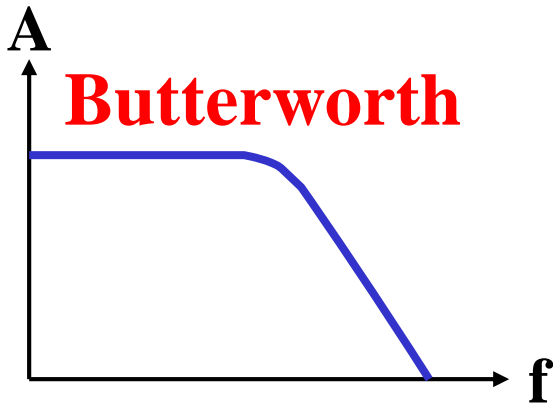
# Filter approximations


- Butterworth (maximally flat response): rolloff =  $20n$  dB/decade where  $n$  is the order of the filter
- Chebyshev (equal ripple response): the number of ripples =  $n/2$
- Inverse Chebyshev (rippled stopband).
- Elliptic (optimum transition)
- Bessel (linear phase shift)







**Real  
low-pass  
filter  
responses**

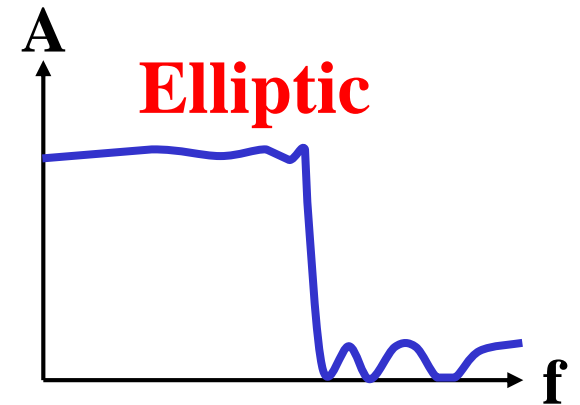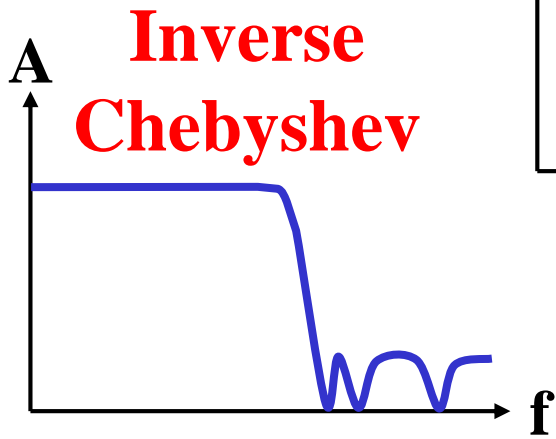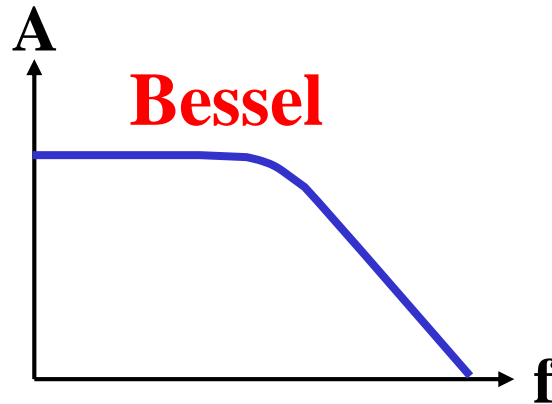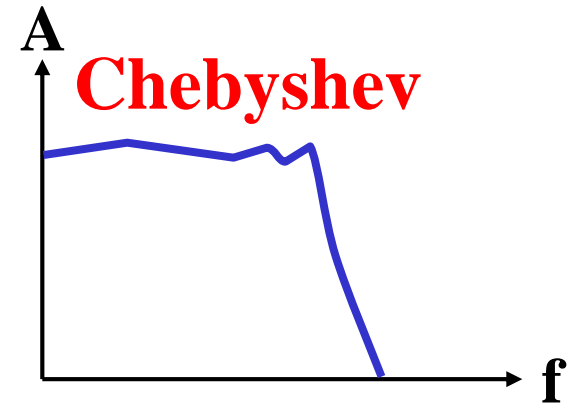

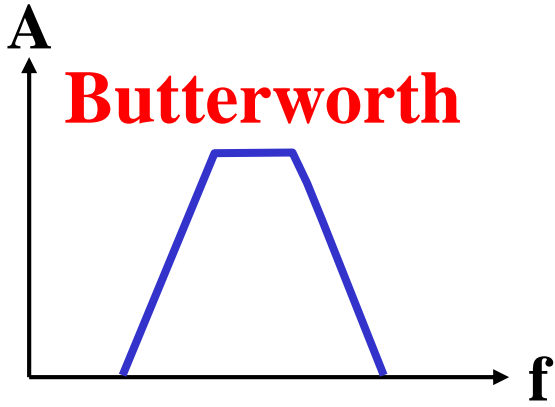
**Note: monotonic filters have no ripple in the stopband.**



**Real  
bandpass  
filter  
responses**

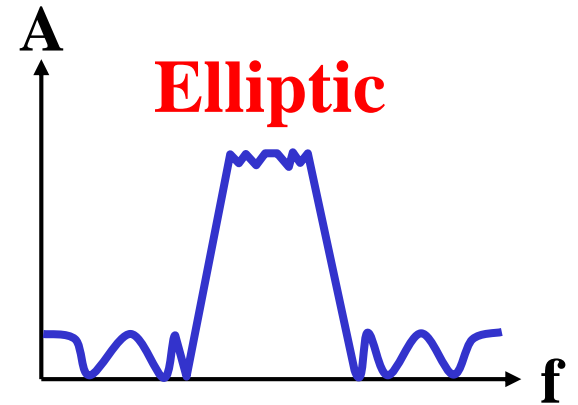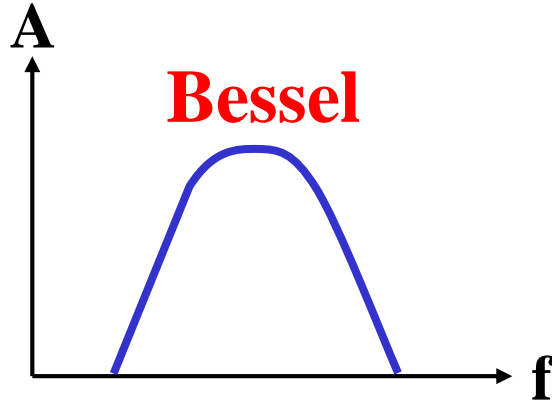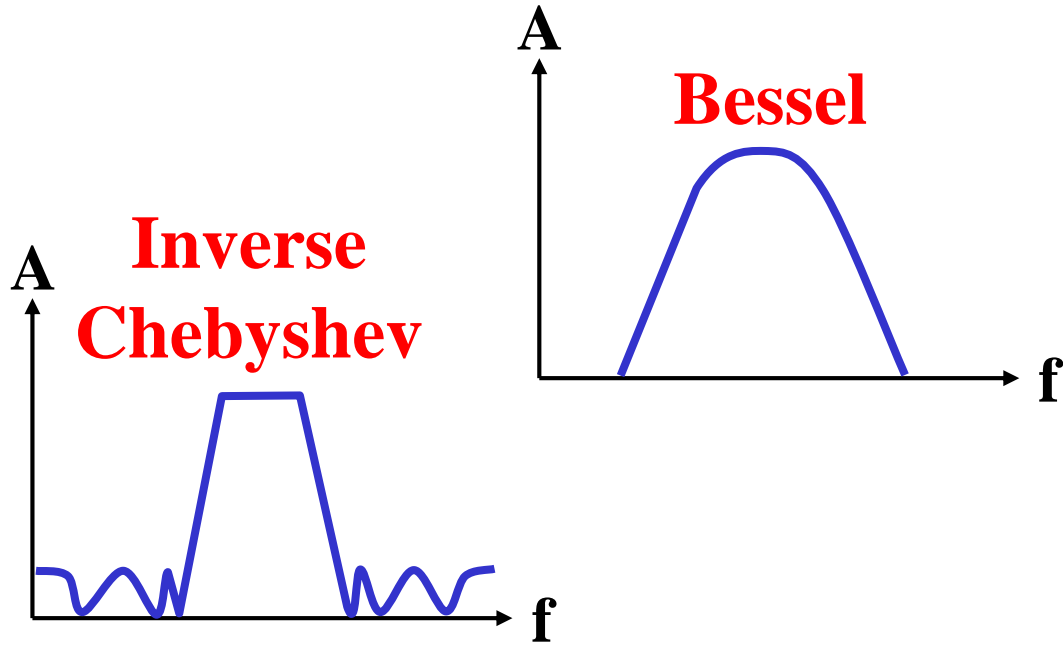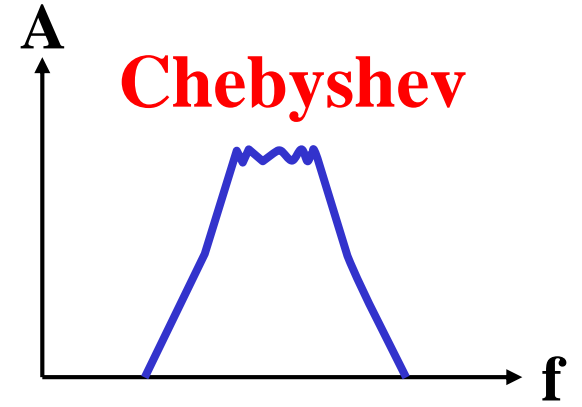

# A second-order low-pass LC filter

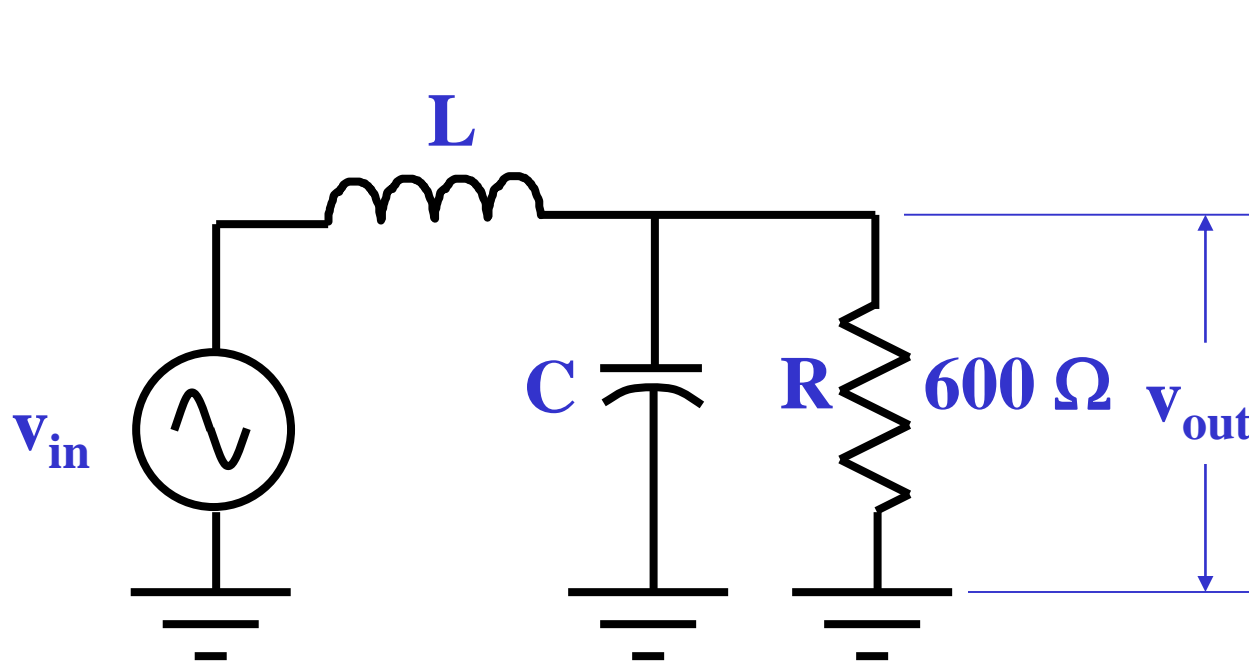


$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$Q = \frac{R}{X_L}$$

<b>L</b>	<b>C</b>	<b>f<sub>R</sub></b>	<b>Q</b>
<b>9.55 mH</b>	<b>2.65 μF</b>	<b>1 kHz</b>	<b>10</b>
<b>47.7 mH</b>	<b>531 nF</b>	<b>1 kHz</b>	<b>2</b>
<b>135 mH</b>	<b>187 nF</b>	<b>1 kHz</b>	<b>0.707</b>


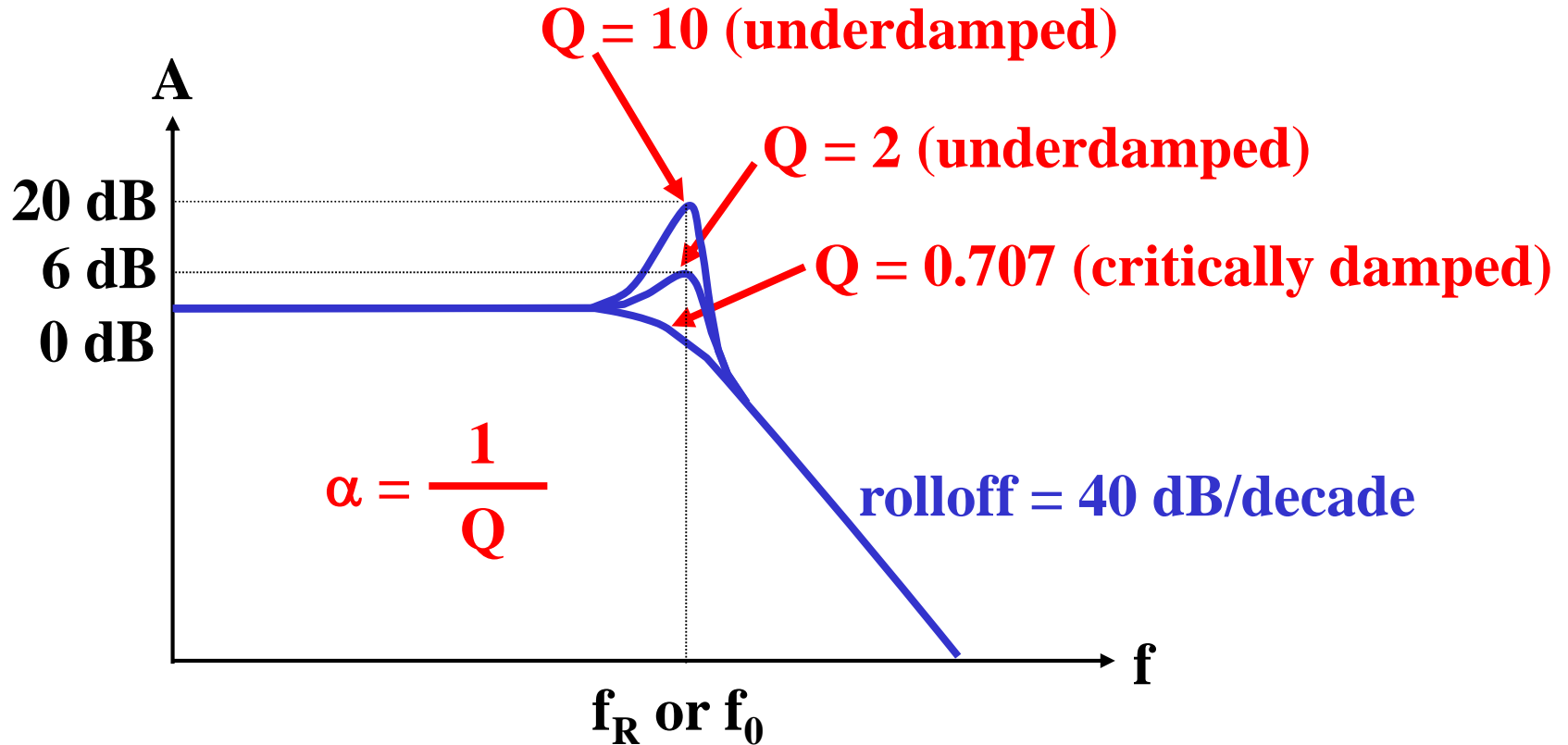
# The effect of Q on second-order response




**The Butterworth response is critically damped.**

**The Bessel response is overdamped ( $Q = 0.577 \dots$  not graphed).**

**The damping factor is  $\alpha$ .**
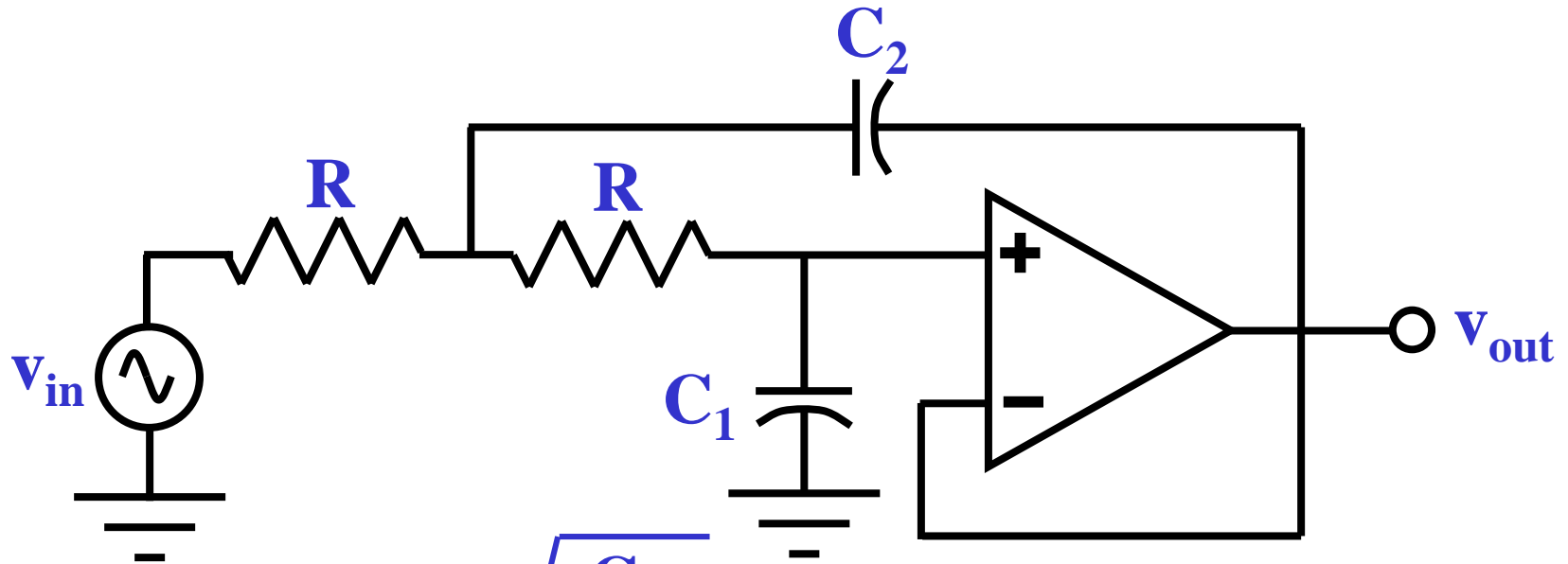
# Sallen-Key second-order low-pass filter



$$Q = 0.5 \sqrt{\frac{C_2}{C_1}}$$

$$A_v = 1$$

$$f_p = \frac{1}{2\pi R \sqrt{C_1 C_2}} = \text{pole frequency}$$


# Second-order responses

- **Butterworth:  $Q = 0.707$ ;  $K_c = 1$**
- **Bessel:  $Q = 0.577$ ;  $K_c = 0.786$**
- **Cutoff frequency:  $f_c = K_c f_p$**
- **Peaked response:  $Q > 0.707$** 
  - \*  **$f_0 = K_0 f_p$  (the peaking frequency)**
  - \*  **$f_c = K_c f_p$  (the edge frequency)**
  - \*  **$f_{3dB} = K_3 f_p$**

# Higher-order filters

- **Cascade second-order stages to obtain even-order response.**
- **Cascade second-order stages plus one first-order stage to obtain odd-order response.**
- **The dB attenuation is cumulative.**
- **Filter design can be tedious and complex.**
- **Tables and filter-design software are used.**

# Sallen-Key equal-component filter

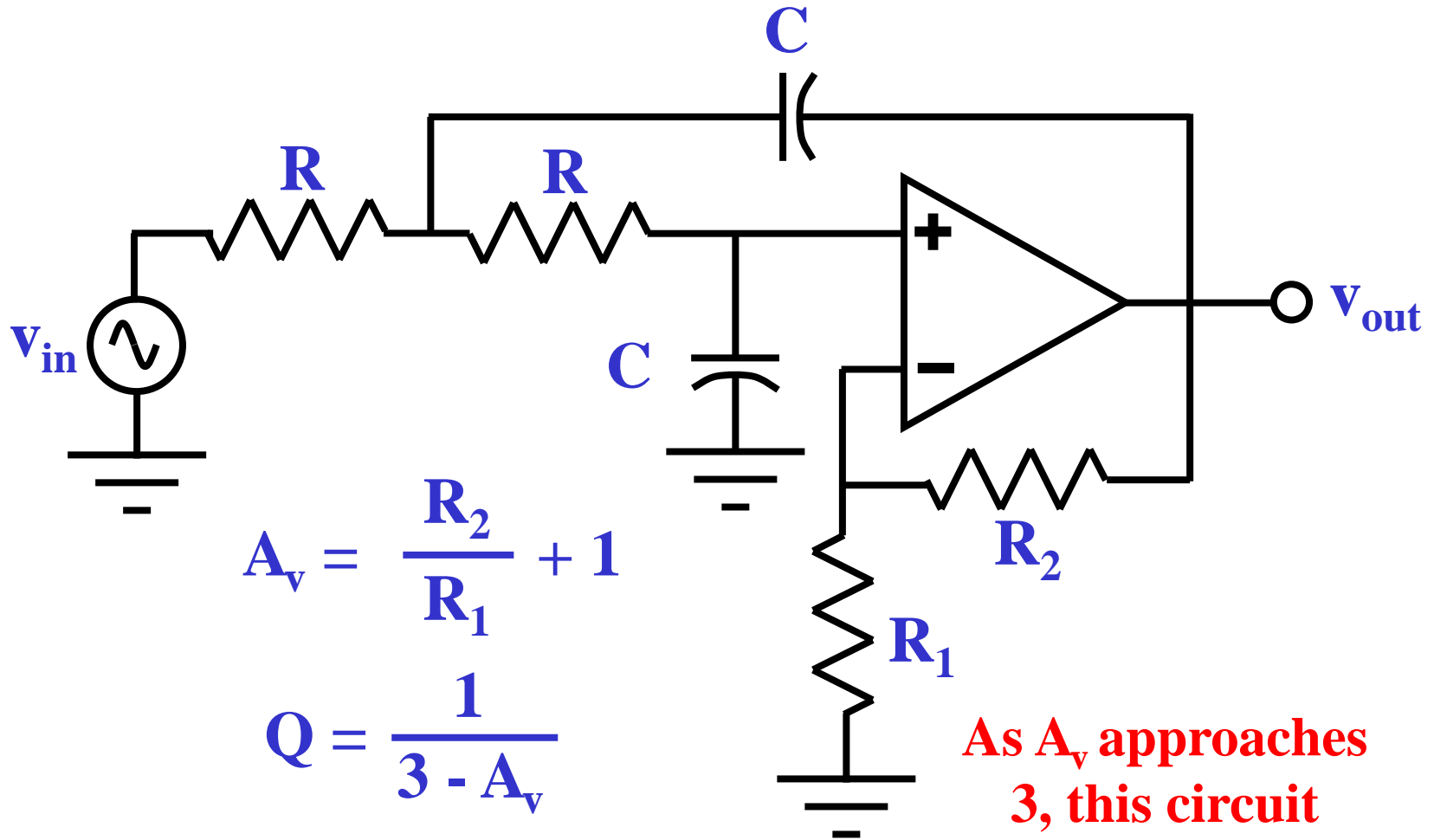


$$A_v = \frac{R_2}{R_1} + 1$$

$$Q = \frac{1}{3 - A_v}$$

$$f_p = \frac{1}{2\pi RC}$$

**As  $A_v$  approaches 3, this circuit becomes impractical.**

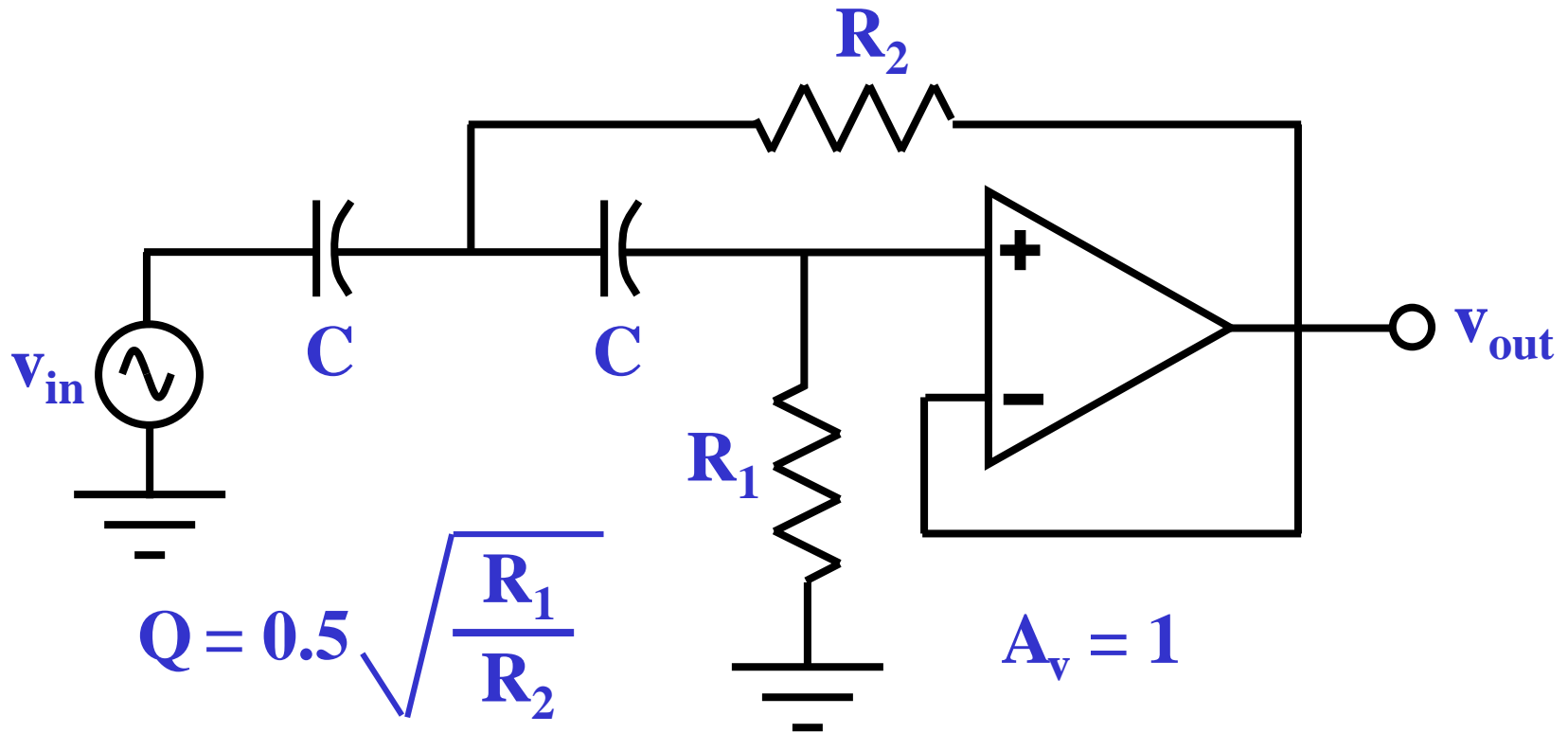
# Sallen-Key second-order high-pass filter



$$Q = 0.5 \sqrt{\frac{R_1}{R_2}}$$

$$f_p = \frac{1}{2\pi C \sqrt{R_1 R_2}}$$
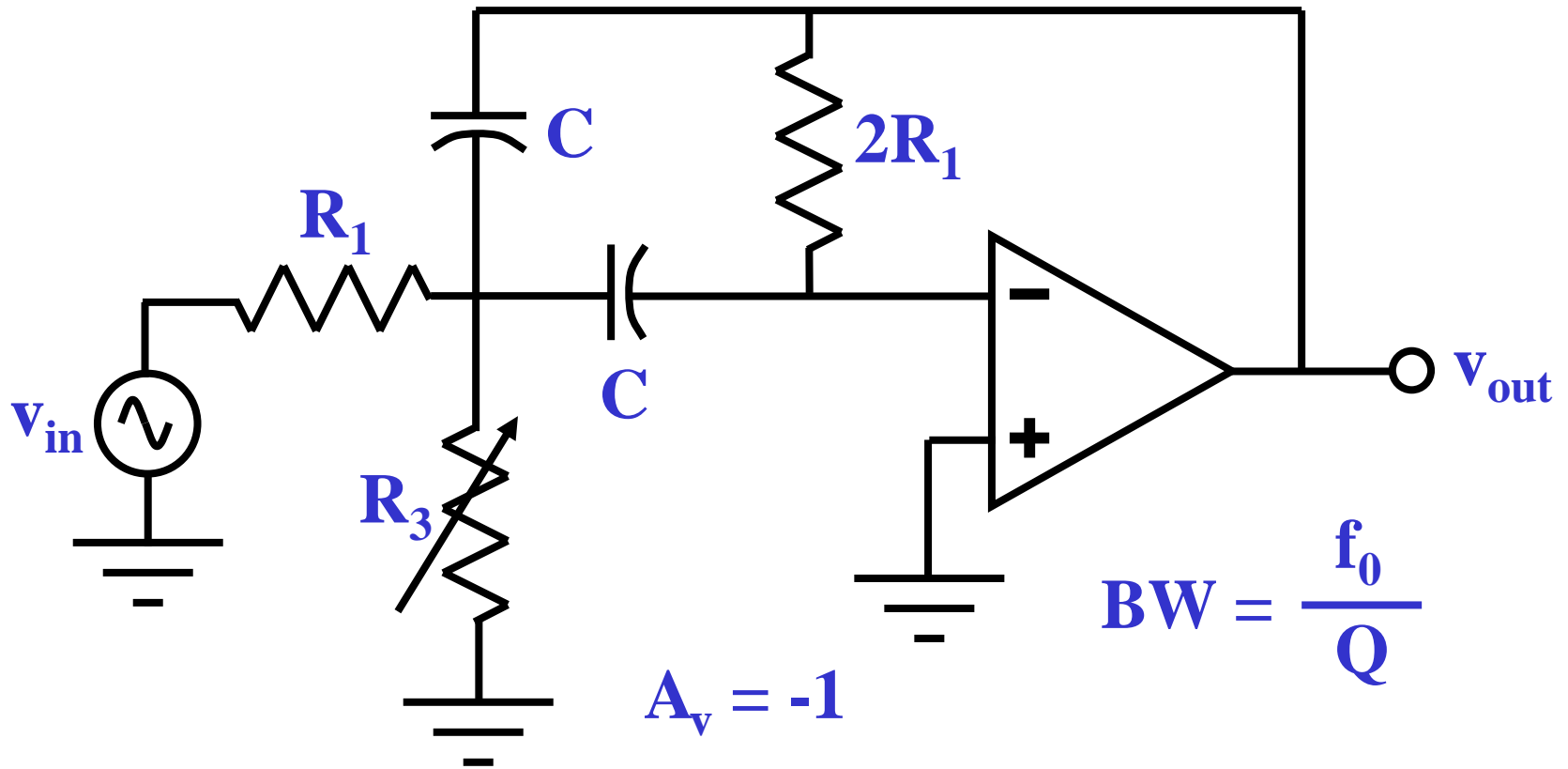
# Tunable MFB bandpass filter with constant bandwidth




$$A_v = -1$$

$$BW = \frac{f_0}{Q}$$

$$f_0 = \frac{1}{2\pi C \sqrt{2R_1(R_1 \parallel R_3)}}$$

$$Q = 0.707 \sqrt{\frac{R_1 + R_3}{R_3}}$$

# Sallen-Key second-order notch filter

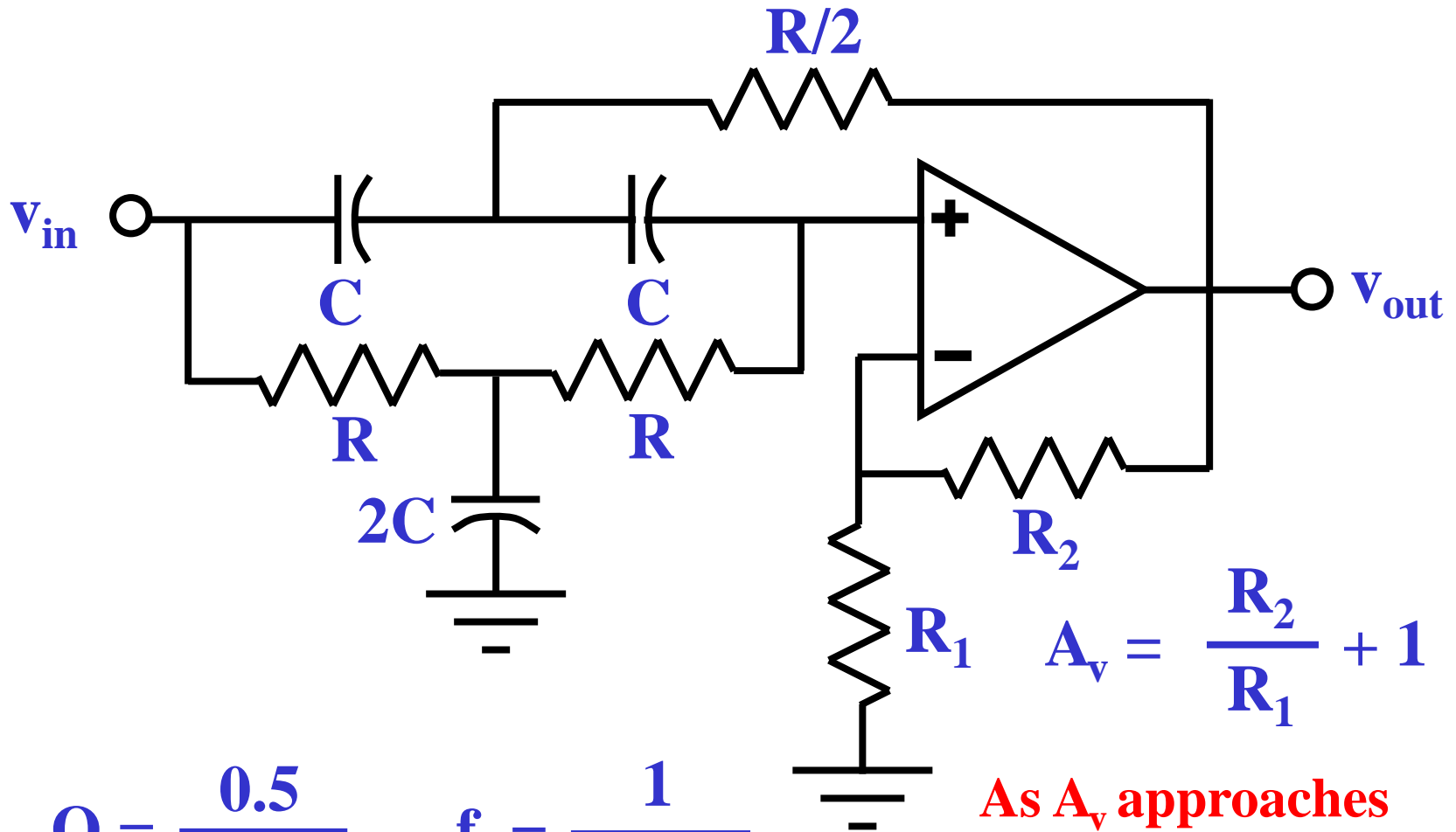


$$A_v = \frac{R_2}{R_1} + 1$$

$$Q = \frac{0.5}{2 - A_v} \quad f_0 = \frac{1}{2\pi RC}$$

As  $A_v$  approaches 2, this circuit becomes impractical.




# First-order all-pass lag filter

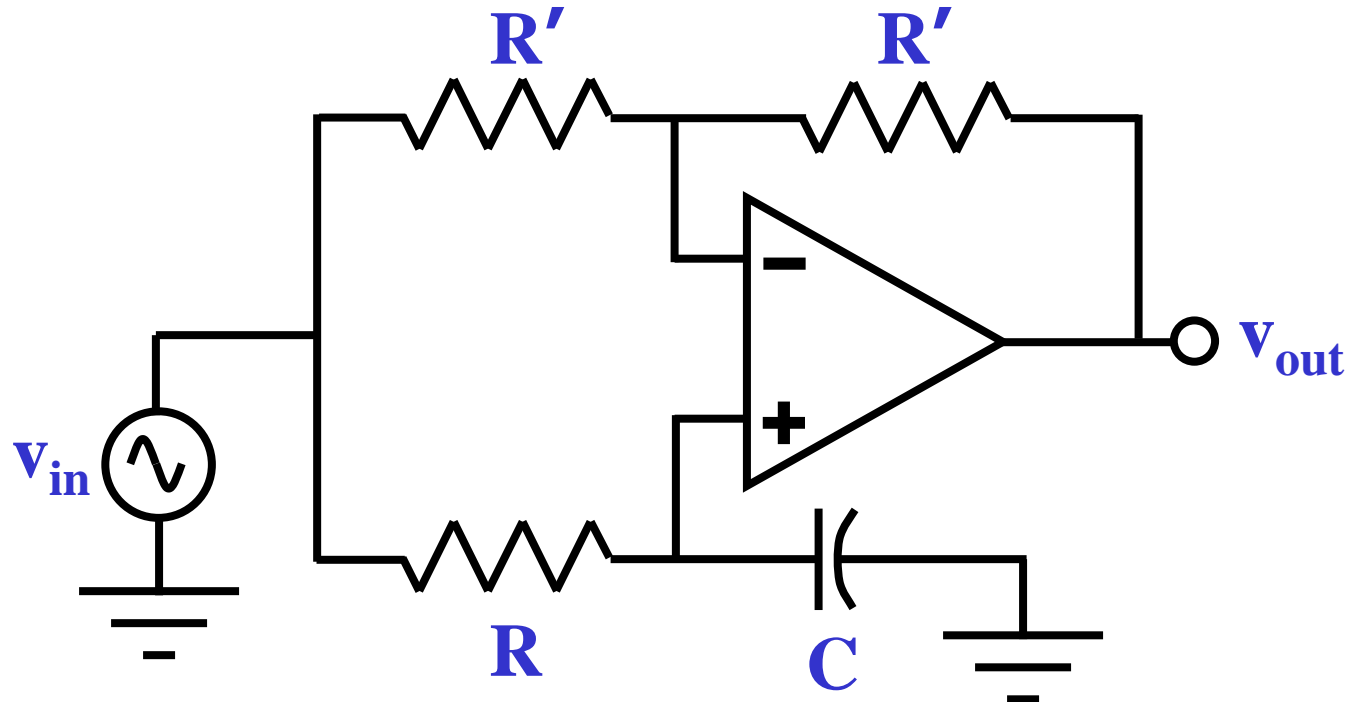

$$A_v = 1 \quad f_0 = \frac{1}{2\pi RC} \quad \phi = -2 \arctan \frac{f}{f_0}$$

# First-order all-pass lead filter

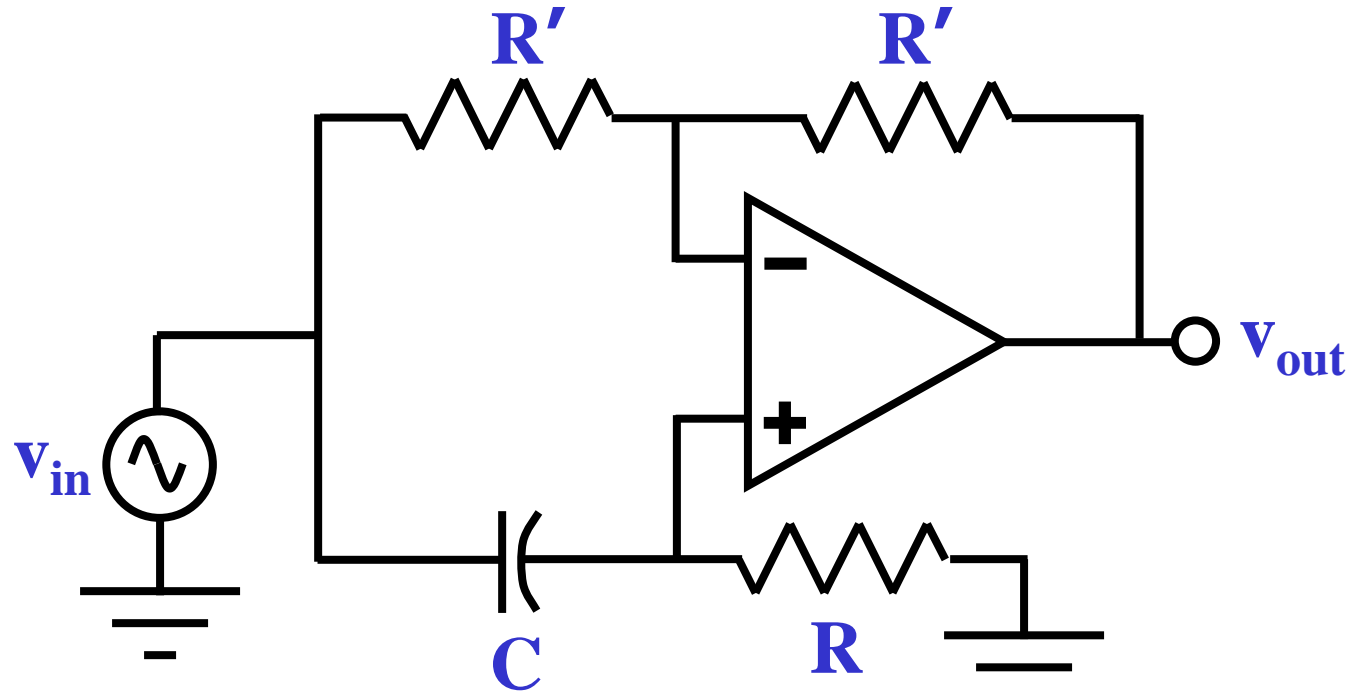

$$A_v = -1 \quad f_0 = \frac{1}{2\pi RC} \quad \phi = 2 \arctan \frac{f_0}{f}$$

# Linear phase shift

- **Required to prevent distortion of digital signals**
- **Constant delay for all frequencies in the passband**
- **Bessel design meets requirements but rolloff might not be adequate**
- **Designers sometimes use a non-Bessel design followed by an all-pass filter to correct the phase shift**

# State variable filter

